

Official-source Electricity compilation 01

Mixed-source chapter worksheet • cross-paper reuse disclosed

Total: 33 marks • Suggested time: 66 minutes

Instructions and reuse disclosure

Curated compilation of official CBSE source questions, not a CBSE-issued chapter paper. Original source labels and exact source images are retained.

Answer every selected question. Only one selected source-slot alternative appears in this paper; do not answer or count excluded alternatives.

Questions recur across this 15-paper collection. Reuse is disclosed per question in the source appendix; these are not 15 disjoint official papers.

Sections use available source marks: A MCQ; B 2 marks; C 3 marks; D 5 marks or source-marked case questions. Case marks are not inflated to five.

Section A — MCQ

Compilation questions 1-4; 4 marks. Exact source labels remain attached to each question.

Section B — 2-mark questions

Compilation questions 5-8; 8 marks. Exact source labels remain attached to each question.

Section C — 3-mark questions

Compilation questions 9-12; 12 marks. Exact source labels remain attached to each question.

Section D — 5-mark / case-based questions

Compilation questions 13-14; 9 marks. Exact source labels remain attached to each question.

Section A — MCQ

1. [1 marks] Source Q30 • 2026 First Board

30. Work done in displacing an electron between two points having potential difference of 1 V, is : 1

- | | |
|--------------------------------------|--------------------------------------|
| (A) $-1.6 \times 10^{-19} \text{ C}$ | (B) $-1.6 \times 10^{-19} \text{ J}$ |
| (C) $+1.6 \times 10^{-19} \text{ J}$ | (D) $-1.6 \times 10^{-19} \text{ V}$ |

Source/editorial note: Visually confirmed complete replacement crop: question number, wording, all options/table values, mathematical symbols and printed marks. Whitespace normalized; mathematical glyphs represented in Unicode and stacked fractions as $\frac{1}{4}$ and $\frac{V}{4}$. Page/QR/footer debris removed from text; marks retained in marks field. No supplied diagram; table retained in text and evidence. Answers not reviewed. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

2. [1 marks] Source Q6 • 2019-20

- 6 When a 4V battery is connected across an unknown resistor there is a current of 100 mA in the circuit. The value of the resistance of the resistor is:
- i) $4\ \Omega$
 - ii) $40\ \Omega$
 - iii) $400\ \Omega$
 - iv) $0.4\ \Omega$

Source/editorial note: Original spelling “resister” retained. Q6 mark is printed on the preceding page (page 3); Section A instructions and the MS both confirm 1 mark.

3. [1 marks] Source Q31 • 2026-27

31	An electrical appliance rated 1000 W is operated at 250 V. What current does it draw?	1
	A. 0.25 A	
	B. 2.5 A	
	C. 4.0 A	
	D. 10 A	

Source/editorial note: Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

4. [1 marks] Source Q19 • main

19. *Assertion (A) :* Nichrome is an alloy which is commonly used in electrical heating devices such as electric irons, toasters, etc.

Reason (R) : The resistivity of nichrome is high and its resistance decreases with increase in temperature.

For Questions number 17 to 20, two statements are given — one labelled as Assertion (A) and the other labelled as Reason (R). Select the correct answer to these questions from the codes (A), (B), (C) and (D) as given below.


- (A) Both Assertion (A) and Reason (R) are true and Reason (R) is the correct explanation of Assertion (A).
- (B) Both Assertion (A) and Reason (R) are true, but Reason (R) is **not** the correct explanation of Assertion (A).
- (C) Assertion (A) is true, but Reason (R) is false.
- (D) Assertion (A) is false, but Reason (R) is true.

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

Section B — 2-mark questions

5. [2 marks] Source Q25 B • 2024-25

B.

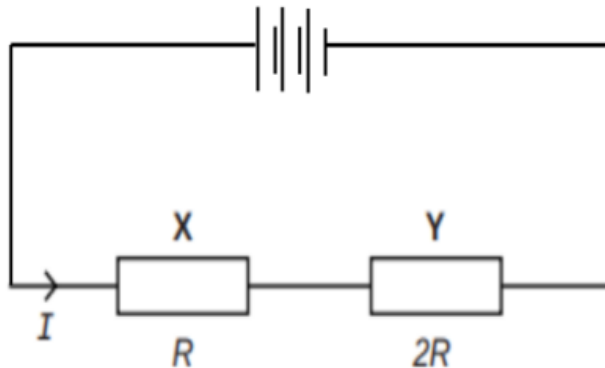

The above figure shows two resistors X and Y connected in series to a battery. The power dissipated for this combination is P_1 . When these resistors are connected in parallel to the same battery then the power dissipated is given by P_2 . Find out the ratio $\frac{P_1}{P_2}$.

Source/editorial note: Diagram supplies $X = R$ and $Y = 2R$; continuation on next page retained. Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

6. [2 marks] Source Q26 OR • 2017-18

OR

In a given ammeter, a student sees that needle indicates 17 divisions in ammeter while performing an experiment to verify Ohm's law. If ammeter has 10 divisions between 0 and 0.5A, then what is the value corresponding to 17 divisions?

Source/editorial note: Separate internal OR alternative to Q26; practical-skills question. The printed number 26 and 2-mark allocation occur on the previous page for the shared question slot.

7. [2 marks] Source Q34 VI B • 2025-26


OR

B. A copper wire has a length $L=2$ m, a cross-sectional area $A=0.5$ mm², and resistivity $\rho=1.7 \times 10^{-8}$ Ω -m. Calculate the resistance of another wire made of the same material whose length is twice the length of the wire but has the same cross-sectional area.


Source/editorial note: Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

26

2

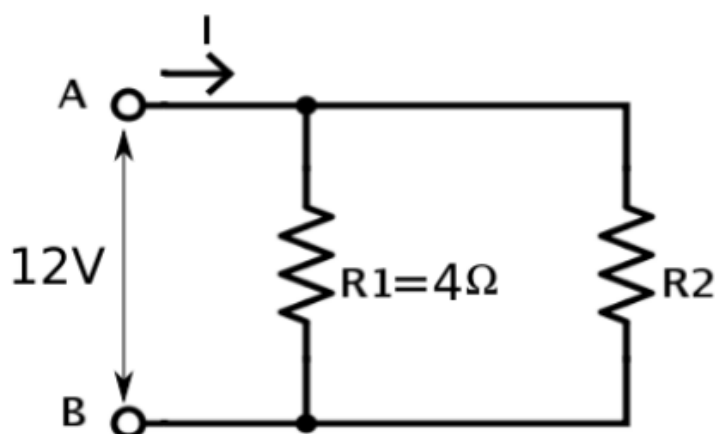

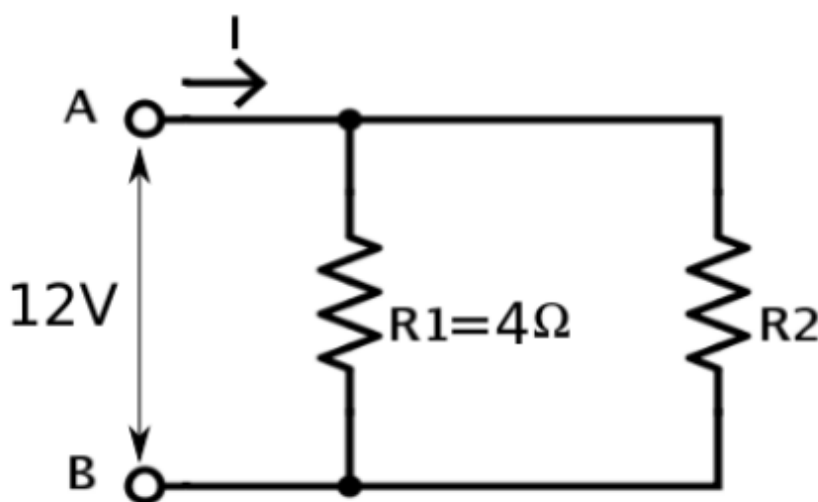A student has two resistors- 2Ω and 3Ω . She has to put one of them in place of R_2 as shown in the circuit. The current that she needs in the entire circuit is exactly 9A. Show by calculation which of the two resistors she should choose.



Section C — 3-mark questions

9. [3 marks] Source Q13 • main

- List the factors on which the resistance of a conductor in the shape of a wire depends.
- Why are metals good conductors of electricity whereas glass is a bad conductor of electricity? Give reason.
- Why are alloys commonly used in electrical heating devices? Give reason.

Source/editorial note: Occurrence mappings retained verbatim; only primary PDF/question evidence is accepted and counted. Other occurrences require their own evidence validation. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

10. [3 marks] Source Q12 • compartment

- 12.** Define the term electric power. An electric device of resistance R when connected across an electric source of voltage V draws a current I . Derive an expression for the power in terms of resistance R and voltage V . What is the power of a device of resistance $400\ \Omega$ operating at 200 V ? 3

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

11. [3 marks] Source Q12 • 2018-19

12. Two lamps, one rated 100 W at 220 V and the other 200 W at 220 V are connected (i) in series and (ii) in parallel to electric main supply of 220 V . Find the current drawn in each case. 3

Source/editorial note: Included despite mains-supply context: self-contained resistance, power and current calculation, not domestic-wiring knowledge.

12. [3 marks] Source Q37 • 2026 First Board

- 37.** The values of current I flowing in a given resistor for the corresponding values of potential difference V applied across the ends of resistor are given below in the table :

I (Amperes)	0.4	0.8	1.2	1.6	2.0
V (Volts)	1.2	2.4	3.6	4.8	6.0

Plot a graph between V and I and calculate the resistance of that resistor. 3

Source/editorial note: Visually confirmed complete replacement crop: question number, wording, all options/table values, mathematical symbols and printed marks. Whitespace normalized; mathematical glyphs represented in Unicode and stacked fractions as $I/4$ and $V/4$. Page/QR/footer debris removed from text; marks retained in marks field. No supplied diagram; table retained in text and evidence. Answers not reviewed. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

Section D — 5-mark / case-based questions

13. [5 marks] Source Q34 • main

SECTION D

- 34.** There are three resistors of $10\ \Omega$, $20\ \Omega$ and $30\ \Omega$ joined in parallel in a circuit. The potential difference across the electric circuit is 10 V .
- (a) Draw a circuit diagram for the above case.
 - (b) Find the total resistance of the combination of resistors.
 - (c) Calculate the electric current drawn from the same source. 5

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

14. [4 marks] Source Q39 OR iv • 2023-24

39	Vinita and Ahmed demonstrated a circuit that operates the two headlights and the two sidelights of a car, in their school exhibition. Based on their demonstrated circuit, answer the following questions. (i) State what happens when switch A is connected to - Position 2 - Position 3 (ii) Find the potential difference across each lamp when lit.	1+1+2
	OR (iv) Show, with calculations, which type of lamp, $4.0\ \Omega$ or $12\ \Omega$, has the higher power.	

Source/editorial note: Includes common (i), (ii) and OR (iv); 1+1+2 marks. Original scheme mislabels second line of (i) as (a). Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

Solutions and verification status

Only explicitly verified solutions are printed. A missing solution is not a claim that the question is unsolvable.

Question 1 — pyq-2026-2857cf20146cab1a7997ae98

Official answer unavailable/withheld: No independently verified official answer supplied.

Original marking scheme (see limitation above): https://www.cbse.gov.in/cbsenew/marketing-scheme/2026/X/086_SCIENCE.zip

Question 2 — cbse_sqp_2019-20_electricity_q6

ii) $40\ \Omega$. $V = IR$; $V = 4\text{ V}$; $I = 100\text{ mA} = 0.1\text{ A}$. $R = V/I = 4/0.1\ \Omega = 40\ \Omega$.

6	ii) = $40\ \Omega$. $V=IR$, $V = 4\text{ V}$, $I = 100\text{ mA} = 0.1\text{ A}$ Hence $R = V/I = 4/0.1\ \Omega = 40\ \Omega$.	1 mark
---	--	--------

Marking-scheme PDF page(s): [1]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_MS.pdf

Question 3 — SQP_2026-27_q31

C. 4.0 A

31	C. 4.0 A	1
----	-------------------	---

Marking-scheme PDF page(s): [7]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2026_27/Science-MS.pdf

Question 4 — pyq-2025-1aee07c91b9869601a83c309

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 5 — SQP_2024-25_q25_B

B. For series total resistance is $R+2R = 3R$ (0.5)

$P_1 = V^2/(3R)$. (0.5)

For parallel total Resistance is $2R/3$. (0.5)

$P_2 = V^2/(2R/3) = 3V^2/(2R)$.

$P_1/P_2 = 2/9$. (0.5)

B. For series total resistance is $R+2R = 3R$	(0.5)
$P_1 = \frac{V^2}{3R}$	(0.5)
For parallel total Resistance is $\frac{2R}{3}$.	(0.5)
$P_2 = \frac{V^2}{2R/3} = \frac{3V^2}{2R}$	
$\frac{P_1}{P_2} = \frac{2}{9}$	(0.5)

Marking-scheme PDF page(s): [3]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-MS.pdf

Question 6 — cbse_sqp_2017-18_electricity_q26_OR

1 Division = $0.5\text{ A}/10$. 17 divisions = $17/20 = 0.85\text{ A}$.

OR

An ammeter has 10 divisions between 0 to 0.5A. So,

1 Division = $0.5\text{A} / 10$

17 divisions = $17/20 = 0.85\text{A}$

Marking-scheme PDF page(s): [7]

https://cbseacademic.nic.in/web_material/SQP/CLASS_X_2017_18/Science_MS.pdf

Question 7 — SQP_2025-26_q34_VI_B

Given:

Length of the wire, $l = 2\text{ m}$

Cross-sectional area, $A = 0.5\text{ mm}^2 = 0.5 \times 10^{-6}\text{ m}^2$

Resistivity of copper, $\rho = 1.7 \times 10^{-8}\text{ }\Omega\cdot\text{m}$

The resistance R of a wire is given by the formula:

$$R = \rho l / A$$

Step 1: Calculate the initial resistance R_1 and $l = 2\text{ m}$

$$R_1 = (1.7 \times 10^{-8} \times 2) / (0.5 \times 10^{-6}) = 0.068\text{ }\Omega$$

Step 2: Calculate the new resistance R_2 and $l = 4\text{ m}$ (double length)

$$R_2 = (1.7 \times 10^{-8} \times 4) / (0.5 \times 10^{-6}) = 0.136\text{ }\Omega$$

The resistance of the wire when the length is double is $0.136\text{ }\Omega$

OR

B.

$$R = \frac{\rho \cdot l}{A}$$

Given:

- Initial length, $l = 2\text{ m}$
- Cross-sectional area, $A = 0.5\text{ mm}^2 = 0.5 \times 10^{-6}\text{ m}^2$
- Resistivity of copper, $\rho = 1.7 \times 10^{-8}\text{ }\Omega \cdot \text{m}$

Step 1: Calculate the initial resistance R_1 and $l = 2\text{ m}$

$$R_1 = \frac{\rho \cdot l}{A} = \frac{1.7 \times 10^{-8}\text{ }\Omega \cdot \text{m} \times 2\text{ m}}{0.5 \times 10^{-6}\text{ m}^2}$$

$$R_1 = \frac{3.4 \times 10^{-8}}{0.5 \times 10^{-6}}\text{ }\Omega = 0.068\text{ }\Omega$$

Step 2: Calculate the new resistance R_2 and $l = 4\text{ m}$ (double length)

$$R_2 = \frac{\rho \cdot (2l)}{A} = 2 \times R_1 = 2 \times 0.068\text{ }\Omega = 0.136\text{ }\Omega$$

The resistance of the wire when the length is double is $0.136\text{ }\Omega$

Marking-scheme PDF page(s): [8]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-MS.pdf

Question 8 — sqp_2020-21_q26

The overall current needed = 9 A and the voltage is 12 V. By Ohm's law, $R = 12/9 = 4/3 \Omega$. R_1 and R_2 are in parallel, so $R = R_1 R_2 / (R_1 + R_2) = 4R_2 / (4 + R_2) = 4/3$. Hence $R_2 = 2 \Omega$.

26	The overall current needed = 9A. The voltage is 12V Hence by Ohm's Law $V=IR$, The resistance for the entire circuit = $12/9 = 4/3 \Omega = R$ R_1 and R_2 are in parallel. Hence, $R=(R_1 R_2)/(R_1 + R_2) = 4R_2/(4+R_2) = 4/3$ $R_2 = 2\Omega$	2
----	---	---

Marking-scheme PDF page(s): [4]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2020_21/Science-MS.pdf

Question 9 — pyq-2018-910a1f81e814c508e7ea459d

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 10 — pyq-2022-4f106d54aeecf637b6b663fc

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 11 — cbse_sqp_2018-19_electricity_q12

$R_1 = V^2/P_1 = 484 \Omega$; $R_2 = V^2/P_2 = 242 \Omega$. In series: $R_s = 726 \Omega$, $I_s = 220/726 = 10/33 \text{ A} = 0.30 \text{ A}$. In parallel: $R_p = 484/3 \Omega$, $I_p = 220 \times 3/484 = 30/22 \text{ A} = 1.36 \text{ A}$.

$$12. R_1 = \frac{V^2}{P_1} = \frac{220 \times 220}{100} = 484 \Omega$$

3

$$R_2 = \frac{V^2}{P_2} = \frac{220 \times 220}{200} = 242 \Omega$$

In series:

$$R_s = R_1 + R_2 = 484 + 242 = 726 \Omega$$

$$\therefore I_s = \frac{V}{R_s} = \frac{220}{726} = \frac{10}{33} \text{ A} = 0.30 \text{ A}$$

In parallel:

$$\begin{aligned} \frac{1}{R_p} &= \frac{1}{R_1} + \frac{1}{R_2} \\ &= \frac{1}{484} + \frac{1}{242} \end{aligned}$$

$$R_p = \frac{484}{3} \Omega$$

$$I_p = \frac{V}{R_p} = \frac{220 \times 3}{484} = \frac{30}{22} \text{ A} = 1.36 \text{ A}$$

Marking-scheme PDF page(s): [4]

https://cbseacademic.nic.in/web_material/SQP/CLASS_X_2018_19/X_Science_MS_2018-19.pdf

Question 12 — pyq-2026-5a70b3f10750c4ea0ef7dba2

Official answer unavailable/withheld: No independently verified official answer supplied.

Original marking scheme (see limitation above): https://www.cbse.gov.in/cbsenew/marketing-scheme/2026/X/086_SCIENCE.zip

Question 13 — pyq-2023-84af9d4edc02297aecab4a0f

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 14 — SQP_2023-24_q39_OR_iv

(i) 12 Ω lamps (only) on.

(a) 4 Ω lamps (only) on [0.5+0.5]

(ii) 12 V for both sets of lamps and all of them are in parallel. [1]

OR

$$P = V^2/R$$

All lamps are in parallel and hence same V for all lamps.

$$\text{For } 4 \Omega \text{ lamps} \rightarrow P = (12 \times 12)/4 = 36 \text{ W}$$

$$\text{For } 12 \Omega \text{ lamps} \rightarrow P = (12 \times 12)/12 = 12 \text{ W}$$

Hence 4 Ω lamps will have higher power. [0.5 x 4]

39	(i) 12 Ω lamps (only) on. (a) 4 Ω lamps (only) on [0.5+0.5] (ii) 12 V for both sets of lamps and all of them are in parallel. [1] OR $P = V^2/R$ All lamps are in parallel and hence same V for all lamps. For 4 Ω lamps $\rightarrow P = \frac{12 \times 12}{4} = 36 \text{ W}$ For 12 Ω lamps $\rightarrow P = \frac{12 \times 12}{12} = 12 \text{ W}$ Hence 4 Ω lamps will have higher power. [0.5 x 4]	4
----	---	---

Marking-scheme PDF page(s): [6]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-MS.pdf

Per-question source appendix

Original CBSE questions/images remain attributed to their source. Compilation selection and numbering are editorial. The full Science source PDFs may include unrelated chapters; only selected Electricity crops form this worksheet.

1. pyq-2026-2857cf20146cab1a7997ae98

CBSE Class X Science 2026 First Board 31(B)-Science for V.I. | PYQ | Year/session: 2026 / 2026 First Board | Paper code: 31/B | Source question: 30 | Original section: Section C (Physics) | Selected marks: 1 | PDF pages (one-based): 21

<https://www.cbse.gov.in/cbsenew/question-paper/2026/X/Science.zip>

Also used in: official-11

2. cbse_sqp_2019-20_electricity_q6

Class-X Science-086 SAMPLE QUESTION PAPER 2019-20 | SQP | Year/session: 2019-20 / 2019-20 | Paper code: Not recorded | Source question: 6 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 4

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_SQP.pdf

Also used in: official-06, official-07, official-10, official-15

3. SQP_2026-27_q31

CBSE Class X Science (086) Sample Question Paper 2026-27 (English) | SQP | Year/session: 2026-27 / 2026-27 | Paper code: Not recorded | Source question: 31 | Original section: Section – C | Selected marks: 1 | PDF pages (one-based): 11

https://cbseacademic.nic.in/web_material/SQP/ClassX_2026_27/Science-SQP.pdf

Also used in: official-05, official-08, official-11, official-12, official-15

4. pyq-2025-1aee07c91b9869601a83c309

CBSE — Class X Science — 2025 — main — 31/2/1 | PYQ | Year/session: 2025 / main | Paper code: 31/2/1 | Source question: 19 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 13, 11

https://www.cbse.gov.in/cbsenew/question-paper/2025/X/086_Science.zip

Also used in: official-07, official-10

5. SQP_2024-25_q25_B

CBSE Class X Science (086) Sample Question Paper 2024-25 (English) | SQP | Year/session: 2024-25 / 2024-25 | Paper code: Not recorded | Source question: 25 B | Original section: Section-B | Selected marks: 2 | PDF pages (one-based): 6, 7

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-SQP.pdf

Also used in: official-10, official-13

6. cbse_sqp_2017-18_electricity_q26_OR

Sample Question Paper 2017-18 — Science — Class – X | SQP | Year/session: 2017-18 / 2017-18 | Paper code: Not recorded | Source question: 26 OR | Original section: SECTION – B | Selected marks: 2 | PDF pages (one-based): 4

https://cbseacademic.nic.in/web_material/SQP/CLASS_X_2017_18/Science_SQP.pdf

Also used in: official-09, official-13

7. SQP_2025-26_q34_VI_B

CBSE Class X Science (086) Sample Question Paper 2025-26 (English) | SQP | Year/session: 2025-26 / 2025-26 | Paper code: Not recorded | Source question: 34 VI B | Original section: Section – C | Selected marks: 2 | PDF pages (one-based): 12

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-SQP.pdf

Also used in: official-09, official-13

8. sqp_2020-21_q26

CBSE Class X Science (086) Sample Question Paper 2020-21 | SQP | Year/session: 2020-21 / 2020-21 | Paper code: Not recorded | Source question: 26 | Original section: Section B | Selected marks: 2 | PDF pages (one-based): 12

https://cbseacademic.nic.in/web_material/SQP/ClassX_2020_21/Science-SQP.pdf

Also used in: official-10

9. pyq-2018-910a1f81e814c508e7ea459d

CBSE — Class X Science — 2018 — 31/1 — main | PYQ | Year/session: 2018 / main | Paper code: 31/1 | Source question: 13 | Original section: Section – A | Selected marks: 3 | PDF pages (one-based): 6

https://www.cbse.gov.in/curric~1/qpms2018/qp_10/Science.zip

Also used in: official-06, official-10

10. pyq-2022-4f106d54aeecf637b6b663fc

CBSE — Class X Science — 2022 — compartment — 31/6/1 | PYQ | Year/session: 2022 / compartment | Paper code: 31/6/1 | Source question: 12 | Original section: SECTION B | Selected marks: 3 | PDF pages (one-based): 11

<https://www.cbse.gov.in/cbsenew/question-paper/2022-COMPTT/X/SCIENCE.zip>

Also used in: official-07, official-13

11. cbse_sqp_2018-19_electricity_q12

Class-X Science-086 SAMPLE QUESTION PAPER-19 | SQP | Year/session: 2018-19 / 2018-19 | Paper code: Not recorded | Source question: 12 | Original section: SECTION C | Selected marks: 3 | PDF pages (one-based): 2

https://cbseacademic.nic.in/web_material/SQP/CLASS_X_2018_19/X_Science_SQP_2018-19.pdf

Also used in: official-05

12. pyq-2026-5a70b3f10750c4ea0ef7dba2

CBSE Class X Science 2026 First Board 31-2-3 | PYQ | Year/session: 2026 / 2026 First Board | Paper code: 31/2/3 | Source question: 37 | Original section: Section C (Physics) | Selected marks: 3 | PDF pages (one-based): 27

<https://www.cbse.gov.in/cbsenew/question-paper/2026/X/Science.zip>

No cross-paper reuse.

13. pyq-2023-84af9d4edc02297aecab4a0f

CBSE — Class X Science — 2023 — main — 31/5/2 | PYQ | Year/session: 2023 / main | Paper code: 31/5/2 | Source question: 34 | Original section: SECTION D | Selected marks: 5 | PDF pages (one-based): 19

<https://www.cbse.gov.in/cbsenew/question-paper/2023/X/SCIENCE.zip>

Also used in: official-05, official-09, official-10, official-13

14. SQP_2023-24_q39_OR_iv

CBSE Class X Science (086) Sample Question Paper 2023-24 (English) | SQP | Year/session: 2023-24 / 2023-24 | Paper code: Not recorded | Source question: 39 OR iv | Original section: Section-E | Selected marks: 4 | PDF pages (one-based): 8

https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-SQP.pdf

Also used in: official-08, official-11, official-12, official-15