

Official-source Electricity compilation 02

Mixed-source chapter worksheet • cross-paper reuse disclosed

Total: 35 marks • Suggested time: 70 minutes

Instructions and reuse disclosure

Curated compilation of official CBSE source questions, not a CBSE-issued chapter paper. Original source labels and exact source images are retained.

Answer every selected question. Only one selected source-slot alternative appears in this paper; do not answer or count excluded alternatives.

Questions recur across this 15-paper collection. Reuse is disclosed per question in the source appendix; these are not 15 disjoint official papers.

Sections use available source marks: A MCQ; B 2 marks; C 3 marks; D 5 marks or source-marked case questions. Case marks are not inflated to five.

Section A — MCQ

Compilation questions 1-4; 4 marks. Exact source labels remain attached to each question.

Section B — 2-mark questions

Compilation questions 5-8; 8 marks. Exact source labels remain attached to each question.

Section C — 3-mark questions

Compilation questions 9-11; 9 marks. Exact source labels remain attached to each question.

Section D — 5-mark / case-based questions

Compilation questions 12-14; 14 marks. Exact source labels remain attached to each question.

Section A — MCQ

1. [1 marks] Source Q15 • compartment

15. The resistance of a wire does **not** depend on its :

- (a) Length
- (b) Area of cross-section
- (c) Shape
- (d) Material

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.


2. [1 marks] Source Q14 • main


14. An electric iron of resistance $20\ \Omega$ draws a current of 5 A . The heat developed in the iron in 30 seconds is :

- (A) 15000 J (B) 6000 J
(C) 1500 J (D) 3000 J

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

3. [1 marks] Source Q15 • 2022-23

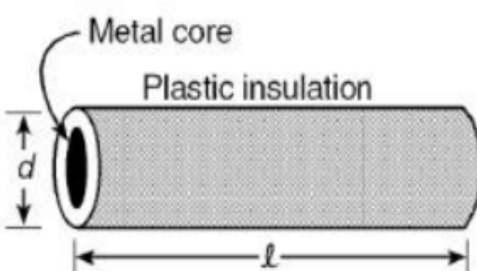15	 Plastic insulation surrounds a wire having diameter d and length l as shown above. A decrease in the resistance of the wire would be produced by an increase in the (a) length l of the wire (b) diameter d of the wire (c) temperature of the wire (d) thickness of the plastic insulation	1
----	--	---

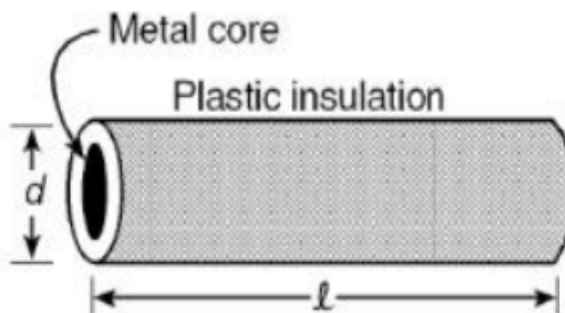


4. [1 marks] Source Q7 • 2019-20

7	Unit of electric power may also be expressed as: i) volt-ampere ii) kilowatt-hour iii) watt-second iv) joule-second	1
---	---	---

Section B — 2-mark questions

5. [2 marks] Source Q34 B • 2025-26

B.

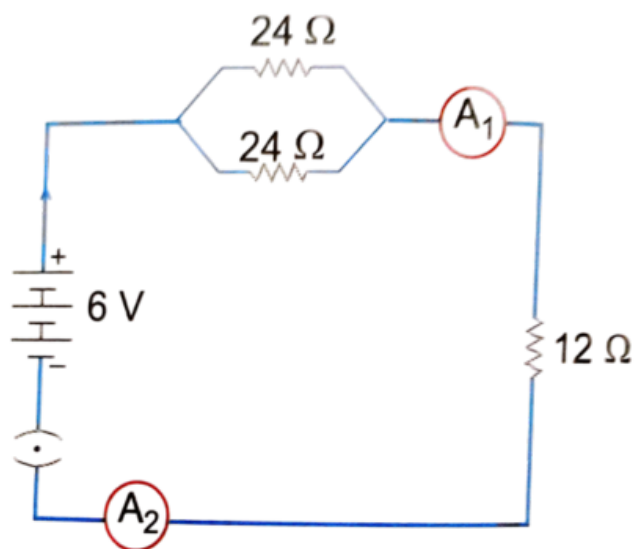

Study the circuit and find out-

- (i) Current in 12 ohm resistor
- (ii) Difference in the readings of ammeter A_1 and A_2 if any

Source/editorial note: Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

6. [2 marks] Source Q26 • main

- 26.** An electric kettle is rated 230 V; 1000 W. Calculate the resistance of its heating element when in operation.

2

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

7. [2 marks] Source Q34 B • 2026-27

Or

B.


- I. Define resistivity.
- II. Justify with an example why resistivity is an intrinsic property of a material.

Source/editorial note: Original MS “thick-nesses” retained; comparison implicitly at fixed temperature. Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

8. [2 marks] Source Q26 • 2018-19

26. The current flowing through a resistor connected in an electrical circuit and the potential difference developed across its ends are shown in the given ammeter and voltmeter. Find the least count of the voltmeter and ammeter .What is the voltage and the current across the given resistor?

2

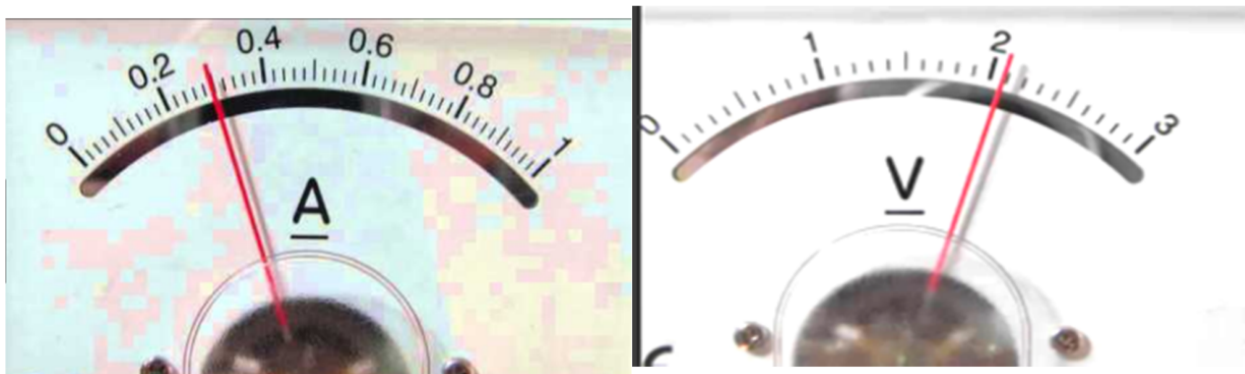

Source/editorial note: Practical-skills question. Official SQP layout error: the ammeter/voltmeter image appears beside chemistry Q22 near the top of the SAME PDF page 5, not alongside Q26. The matching meters and MS establish the intended association. Evidence array puts Q26 text first and displaced diagram second. No image was redrawn.

Section C — 3-mark questions

9. [3 marks] Source Q31 • compartment

- 31.** (a) Write mathematical expression for Joule's law of heating.
- (b) Calculate the amount of heat generated while transferring 72000 coulomb of charge in two hours through a potential difference of 220 V.


1+2

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.


10. [3 marks] Source Q12 • 2021-22

12

3

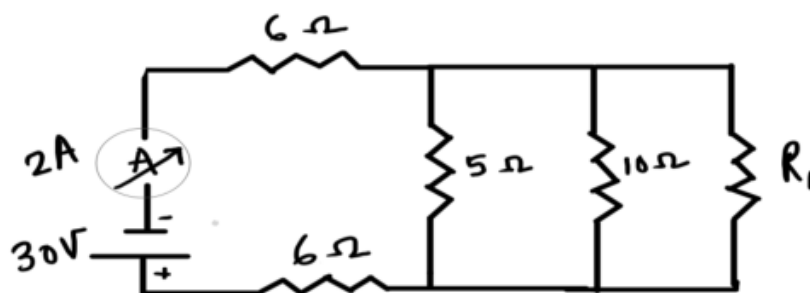

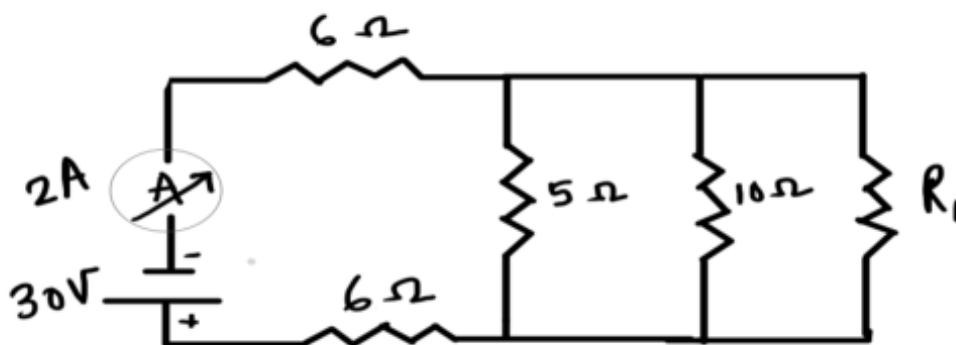
In the above circuit, if the current reading in the ammeter A is 2A, what would be the value of R_1 ?



Source/editorial note: Main and OR are separate three-mark alternatives sharing a single three-mark exam slot. MS incorrectly calls the 5 Ω, 10 Ω and R₁ block “in series”, although its reciprocal formula and source circuit show parallel; MS also prints Req = 15 A instead of 15 Ω. These source errors are explicitly corrected in answer.

11. [3 marks] Source Q35 • 2026 First Board

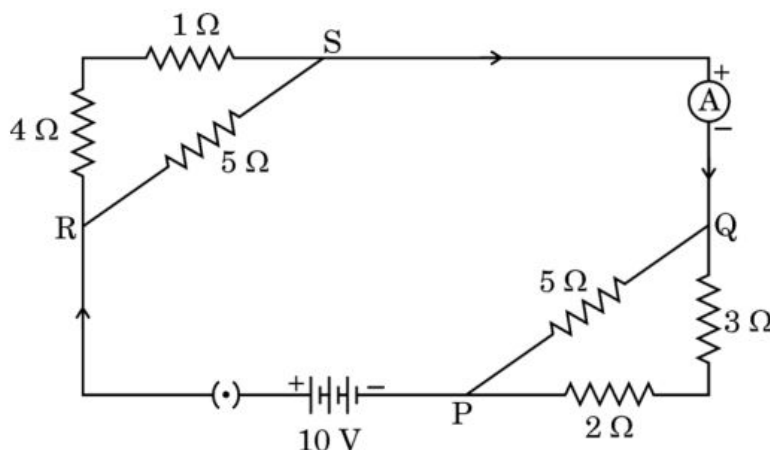35. Consider the given electric circuit :



Calculate the following :

3

- Total resistance of the circuit
- The electric current drawn from the battery
- Potential difference between points P and Q

Source/editorial note: Question text, numbering, printed marks, subparts/internal choices, diagram labels and complete crop boundaries visually checked against saved original-PDF replacement crops, using JPEG quality 80 and maximum dimension 900 px. Whitespace normalized; original wording retained. No MCQ options in this question. Page furniture is not question text. Answer and marking scheme not verified. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

Section D — 5-mark / case-based questions

12. [5 marks] Source Q36 VI B • 2024-25

OR

B.

- State Joules law of heating and write its mathematical expression.
- Two resistors of resistances 2Ω and 4Ω are connected in
 - series
 - parallel
 with a battery of given potential difference. Compute the ratio of total quantity of heat produced in the combination in the two cases if the total voltage and time are kept the same for both.

Source/editorial note: Total 5 marks from Q36 scheme heading; this alternative has no explicit subpart mark breakdown. Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.


13. [4 marks] Source Q39 iii • 2023-24

39	The diagram shows a 12V battery on the left. The positive terminal is at the top. A wire goes from the positive terminal to a junction. From this junction, a wire goes to the top of the first 4.0 Ω lamp. Another wire goes from this junction to a switch labeled 'A'. The switch 'A' has three positions: 1 (top), 2 (middle), and 3 (bottom). Position 1 is connected to the top of the second 4.0 Ω lamp. Position 2 is connected to the top of the first 12 Ω lamp. Position 3 is connected to the top of the second 12 Ω lamp. All four lamps are connected to a common bottom wire that returns to the negative terminal of the battery. Vinita and Ahmed demonstrated a circuit that operates the two headlights and the two sidelights of a car, in their school exhibition. Based on their demonstrated circuit, answer the following questions. - State what happens when switch A is connected to - Position 2 - Position 3 - Find the potential difference across each lamp when lit. - Calculate the current - in each 12 Ω lamp when lit. - In each 4 Ω lamp when lit.	1+1+2
----	--	-------

Source/editorial note: Includes common (i), (ii) and main (iii); 1+1+2 marks. Original scheme mislabels second line of (i) as (a). Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

14. [5 marks] Source Q36 • 2022-23

36	The diagram above is a schematic diagram of a household circuit. The house shown in the above diagram has 5 usable spaces where electrical connections are made. For this house, the mains have a voltage of 220 V and the net current coming from the mains is 22A. - What is the mode of connection to all the spaces in the house from the mains? - The spaces 5 and 4 have the same resistance and spaces 3 and 2 have respective resistances of 20Ω and 30Ω. Space 1 has a resistance double that of space 5. What is the net resistance for space 5. - What is the current in space 3? - What should be placed between the main connection and the rest of the house's electrical appliances to save them from accidental high electric current?	5
----	---	---

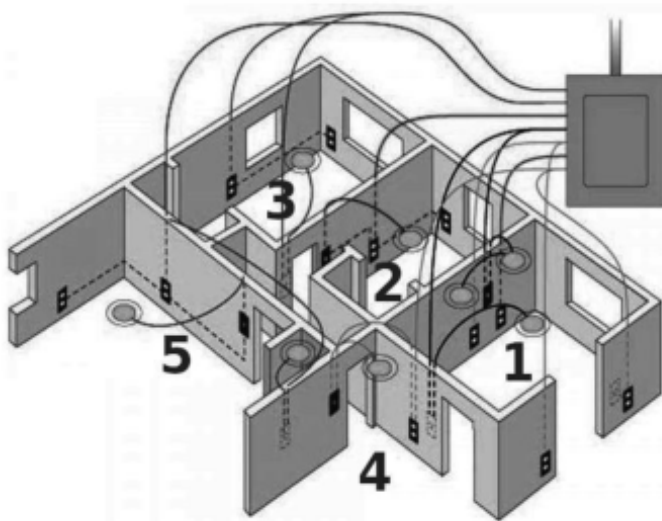

Source/editorial note: Full Q36(a-d) retained after NCERT-based chapter audit: parallel circuits and resistances are Electricity, and protective fuse function is explicitly NCERT Electricity section 11.7.1 (printed p190). Printed parent total = 5 marks. Official MS p6 supplies (a) and (b), but omits (c) and (d). Do not infer subpart mark allocations for those omissions. Answer (c)=11 A is independently derived, not an official MS answer. Answer (d) is not supplied here as an official answer. Official answer unavailable/withheld for an identified error, omission or incomplete verification: Official MS omits c,d; independent c derivation labelled; complete answer not verified. Consult the linked original marking scheme with this limitation in mind.

Solutions and verification status

Only explicitly verified solutions are printed. A missing solution is not a claim that the question is unsolvable.

Question 1 — pyq-2023-dc74f0e84e53633b06097022

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 2 — pyq-2024-a415e02467405f8b9fbacfc3

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 3 — sqp_2022-23_q15

(b) diameter d of the wire

15.	(b) diameter d of the wire	1
-----	----------------------------	---

Marking-scheme PDF page(s): [1]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-MS.pdf

Question 4 — cbse_sqp_2019-20_electricity_q7

i) volt-ampere. Power = Voltage × Current.

7	i) volt-ampere Power = Voltage x Current.	1 mark
---	--	--------

Marking-scheme PDF page(s): [1]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_MS.pdf

Question 5 — SQP_2025-26_q34_B

B.

(i) $\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{24} + \frac{1}{24} = \frac{2}{24}$

$R_P = 12 \text{ ohms}$

$R_T = R_P + 12 = 24 \text{ ohms}$

$I = \frac{V}{R} = \frac{6}{24} = 0.25 \text{ A}$

(ii) Same readings of A_1 and A_2

	B. (i) $\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{24} + \frac{1}{24} = \frac{2}{24}$ $R_P = 12 \text{ ohms}$ $R_T = R_P + 12 = 24 \text{ ohms}$ $I = \frac{V}{R} = \frac{6}{24} = 0.25 \text{ A}$ (ii) Same readings of A_1 and A_2	
--	---	--

Marking-scheme PDF page(s): [7]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-MS.pdf

Question 6 — pyq-2025-50a1900d91ebeada79f31c34

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 7 — SQP_2026-27_q34_B

B.

I. Definition: The resistivity (ρ) of a material is defined as the resistance of a wire having unit cross-sectional area and unit length

$R = \rho L/A$, where R is resistance of a wire of length L and cross-sectional area A (1)

II. Intrinsic property justification: Resistivity depends only on material (not on dimensions).

Example: Two copper wires of different lengths and thick-nesses yield the same ρ when computed using $R \cdot A/L$. (1)

B.

I. Definition: The resistivity (ρ) of a material is defined as the resistance of a wire having unit cross-sectional area and unit length
 $R = \frac{\rho L}{A}$, where R is resistance of a wire of length L and cross-sectional area A (1)

II. Intrinsic property justification: Resistivity depends only on material (not on dimensions). Example: Two copper wires of different lengths and thick-nesses yield the same ρ when computed using $R \cdot A/L$. (1)

Marking-scheme PDF page(s): [7]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2026_27/Science-MS.pdf

Question 8 — cbse_sqp_2018-19_electricity_q26

LC of ammeter = $0.2/10 \text{ A} = 0.02 \text{ A}$. LC of Voltmeter = $1/10 = 0.1 \text{ V}$. Current = $15 \times 0.02 \text{ A} = 0.3 \text{ A}$. Potential difference = $21 \times 0.1 \text{ V} = 2.1 \text{ V}$.

$$26. \text{ LC of ammeter} = \frac{0.2}{10} \text{ A} = 0.02 \text{ A}$$

2

$$\text{LC of Voltmeter} = \frac{1}{10} = 0.1 \text{ V}$$

$$\text{Current} = 15 \times 0.02 \text{ A} = 0.3 \text{ A}$$

$$\text{Potential difference} = 21 \times 0.1 \text{ V} = 2.1 \text{ V}$$

Marking-scheme PDF page(s): [7]

https://cbseacademic.nic.in/web_material/SQP/CLASS_X_2018_19/X_Science_MS_2018-19.pdf

Question 9 — pyq-2025-179b945e5fe9505f3715ef55

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 10 — sqp_2021-22_term2_q12_main

$R_1 = 30 \Omega$. The parallel block has $1/R_p = 1/5 + 1/10 + 1/R_1$, so $R_p = 10R_1/(3R_1 + 10)$. The two 6Ω resistors are in series with that block. $R_{eq} = 30/2 = 15 \Omega$, hence $12 + 10R_1/(3R_1 + 10) = 15$ and $R_1 = 30 \Omega$.

12

5 ohm, 10 ohm and R_1 are in series

$$1/R_p = 1/5 + 1/10 + 1/R_1$$

$$1/R_p = (2+1)/10 + 1/R_1$$

$$= 3/10 + 1/R_1$$

$$1/R_p = (3R_1 + 10)/10R_1$$

$$R_p = 10R_1 / (3R_1 + 10)$$

Now, 6 ohm, 6 ohm and R_p are in series

Thus,

$$R_{eq} = 12 + 10R_1 / (3R_1 + 10) \text{ ----- (1)} \quad (1 \text{ mark})$$

$$V = I R_{eq}$$

From the circuit

$$R_{eq} = 30/2 = 15 \text{ A ----- (2)} \quad (1 \text{ mark})$$


Equating (1) and (2)

$$12 + 10R_1 / (3R_1 + 10) = 15$$

$$10R_1 / (3R_1 + 10) = 3$$

$$10R_1 = (9R_1 + 30)$$

$$\text{Thus, } R_1 = 30 \text{ ohm.} \quad (1 \text{ mark})$$

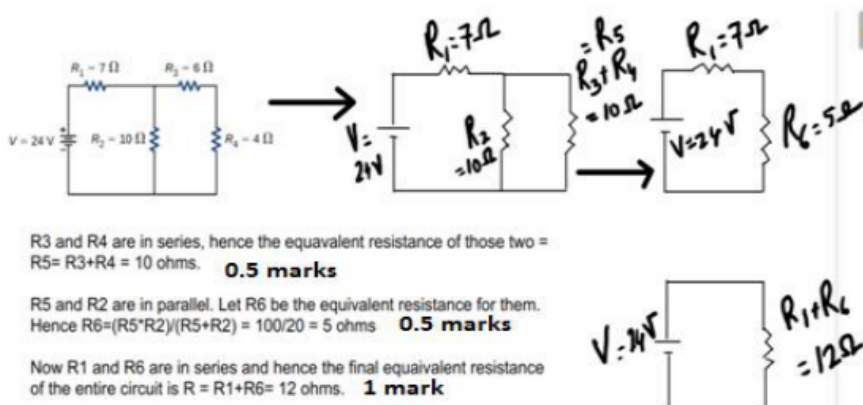OR


R_3 and R_4 are in series, hence the equivalent resistance of those two = $R_5 = R_3 + R_4 = 10 \text{ ohms}$. **0.5 marks**

R_5 and R_2 are in parallel. Let R_6 be the equivalent resistance for them. Hence $R_6 = (R_5 \cdot R_2) / (R_5 + R_2) = 100/20 = 5 \text{ ohms}$ **0.5 marks**

Now R_1 and R_6 are in series and hence the final equivalent resistance of the entire circuit is $R = R_1 + R_6 = 12 \text{ ohms}$. **1 mark**

By Ohm's Law we know that $V = IR$, hence $I = V/R$.

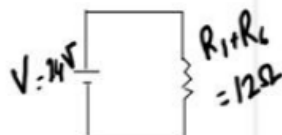Hence the current in the circuit is $24/12 \text{ A} = 2 \text{ A}$ (Final Answer) **1 mark**



(0.5+0.5+1+1)

3

Marking-scheme PDF page(s): [4]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2021_22/Science-MS_Term2.pdf

Question 11 — pyq-2026-cf1c5280affd78bfb04001a2

Official answer unavailable/withheld: No independently verified official answer supplied.

Original marking scheme (see limitation above): https://www.cbse.gov.in/cbsenew/marking-scheme/2026/X/086_SCIENCE.zip

Question 12 — SQP_2024-25_q36_VI_B

B.

(i) Joule's Law of Heating states that the amount of heat produced in a conductor is directly proportional to the square of the electric current passing through it, the resistance of the conductor, and the time for which the current flows. Mathematically, it can be expressed as

$$H = I^2 R t$$

H is the heat produced (in joules),

I is the electric current (in amperes),

R is the resistance of the conductor (in ohms),

t is the time for which the current flows (in seconds).

(ii) Let the equivalent resistance in series be denoted by R_s and that for parallel be denoted by R_p . Total voltage of the circuit is given by V in both cases and the time is denoted by t .

$$R_s = 2 + 4 = 6\Omega$$

$$1/R_p = 1/2 + 1/4 = 3/4, R_p = 4/3$$

$$H_s = (V^2/R_s)t, H_p = (V^2/R_p)t$$

$$H_s/H_p = R_p/R_s = 2/9$$

OR

B.

- (i) Joule's Law of Heating states that the amount of heat produced in a conductor is directly proportional to the square of the electric current passing through it, the resistance of the conductor, and the time for which the current flows. Mathematically, it can be expressed as

$$H = I^2 R t$$

- H is the heat produced (in joules),
- I is the electric current (in amperes),
- R is the resistance of the conductor (in ohms),
- t is the time for which the current flows (in seconds).

- (ii) Let the equivalent resistance in series be denoted by R_s and that for parallel be denoted by R_p . Total voltage of the circuit is given by V in both cases and the time is denoted by t .

- $R_s = 2 + 4 = 6\Omega$
- $\frac{1}{R_p} = \frac{1}{2} + \frac{1}{4} = \frac{3}{4}, R_p = \frac{4}{3}$
- $H_s = \frac{V^2}{R_s}t, H_p = \frac{V^2}{R_p}t$
- $\frac{H_s}{H_p} = \frac{R_p}{R_s} = \frac{2}{9}$

Marking-scheme PDF page(s): [10]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-MS.pdf

Question 13 — SQP_2023-24_q39_iii

(i) 12 Ω lamps (only) on.

(a) 4 Ω lamps (only) on [0.5+0.5]

(ii) 12 V for both sets of lamps and all of them are in parallel. [1]

(iii) 12 Ω lamps are on when the wire is connected to position 2. Voltage across both 12 Ω lamps = 12 V. $V=IR$ (Ohm's law). $I = V/R = 12/12 = 1A$. [1]

4 Ω lamps are on when the wire is connected to position 3. Voltage across both 4 Ω lamps = 12 V. $V=IR$ (Ohm's law). $I = V/R = 12/4 = 3A$. [1]

39	(i) 12 Ω lamps (only) on. (a) 4 Ω lamps (only) on (ii) 12 V for both sets of lamps and all of them are in parallel. (iii) 12 Ω lamps are on when the wire is connected to position 2. Voltage across both 12 Ω lamps = 12 V. $V=IR$ (Ohm's law). $I = \frac{V}{R} = \frac{12}{12} = 1\text{A}.$ 4 Ω lamps are on when the wire is connected to position 3. Voltage across both 4 Ω lamps = 12 V. $V=IR$ (Ohm's law). $I = \frac{V}{R} = \frac{12}{4} = 3\text{A}.$	[0.5+0.5] [1] [1] [1]	4
----	---	---	---

Marking-scheme PDF page(s): [6]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-MS.pdf

Question 14 — sqp_2022-23_q36

Official answer unavailable/withheld: Official MS omits c,d; independent c derivation labelled; complete answer not verified.

Original marking scheme (see limitation above): https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-MS.pdf

Per-question source appendix

Original CBSE questions/images remain attributed to their source. Compilation selection and numbering are editorial. The full Science source PDFs may include unrelated chapters; only selected Electricity crops form this worksheet.

1. pyq-2023-dc74f0e84e53633b06097022

CBSE — Class X Science — 2023 — compartment | PYQ | Year/session: 2023 / compartment | Paper code: Not recorded | Source question: 15 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 11

<https://www.cbse.gov.in/cbsenew/question-paper/2023-COMPTT/X/Science.zip>

Also used in: official-03, official-06, official-09, official-11, official-14

2. pyq-2024-a415e02467405f8b9fbacfc3

CBSE — Class X Science — 2024 — main — 31/4/1 | PYQ | Year/session: 2024 / main | Paper code: 31/4/1 | Source question: 14 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 7

<https://www.cbse.gov.in/cbsenew/question-paper/2024/X/SCIENCE.zip>

Also used in: official-06, official-07, official-09, official-12, official-15

3. sqp_2022-23_q15

CBSE Class X Science (086) Sample Question Paper 2022-23 | SQP | Year/session: 2022-23 / 2022-23 | Paper code: Not recorded | Source question: 15 | Original section: Section A | Selected marks: 1 | PDF pages (one-based): 5

https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-SQP.pdf

Also used in: official-04, official-08, official-10, official-12, official-14

4. cbse_sqp_2019-20_electricity_q7

Class-X Science-086 SAMPLE QUESTION PAPER 2019-20 | SQP | Year/session: 2019-20 / 2019-20 | Paper code: Not recorded | Source question: 7 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 4

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_SQP.pdf

Also used in: official-04, official-08, official-12, official-14

5. SQP_2025-26_q34_B

CBSE Class X Science (086) Sample Question Paper 2025-26 (English) | SQP | Year/session: 2025-26 / 2025-26 | Paper code: Not recorded | Source question: 34 B | Original section: Section – C | Selected marks: 2 | PDF pages (one-based): 12

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-SQP.pdf

Also used in: official-07, official-15

6. pyq-2025-50a1900d91ebada79f31c34

CBSE — Class X Science — 2025 — main — 31/3/1 | PYQ | Year/session: 2025 / main | Paper code: 31/3/1 | Source question: 26 | Original section: SECTION B | Selected marks: 2 | PDF pages (one-based): 13

https://www.cbse.gov.in/cbsenew/question-paper/2025/X/086_Science.zip

Also used in: official-11, official-12

7. SQP_2026-27_q34_B

CBSE Class X Science (086) Sample Question Paper 2026-27 (English) | SQP | Year/session: 2026-27 / 2026-27 | Paper code: Not recorded | Source question: 34 B | Original section: Section – C | Selected marks: 2 | PDF pages (one-based): 12

https://cbseacademic.nic.in/web_material/SQP/ClassX_2026_27/Science-SQP.pdf

Also used in: official-06, official-14

8. cbse_sqp_2018-19_electricity_q26

Class-X Science-086 SAMPLE QUESTION PAPER-19 | SQP | Year/session: 2018-19 / 2018-19 | Paper code: Not recorded | Source question: 26 | Original section: SECTION E | Selected marks: 2 | PDF pages (one-based): 5

https://cbseacademic.nic.in/web_material/SQP/CLASS_X_2018_19/X_Science_SQP_2018-19.pdf

Also used in: official-10, official-15

9. pyq-2025-179b945e5fe9505f3715ef55

CBSE — Class X Science — 2025 — compartment — 31/S/3 | PYQ | Year/session: 2025 / compartment | Paper code: 31/S/3 | Source question: 31 | Original section: SECTION C | Selected marks: 3 | PDF pages (one-based): 15

<https://www.cbse.gov.in/cbsenew/question-paper/2025-COMPTT/X/Science.zip>

Also used in: official-05, official-11

10. sqp_2021-22_term2_q12_main

CBSE Class X Science (086) Sample Question Paper 2021-22 — Term 2 | SQP | Year/session: 2021-22 / 2021-22 | Paper code: Not recorded | Source question: 12 | Original section: Section B | Selected marks: 3 | PDF pages (one-based): 4

https://cbseacademic.nic.in/web_material/SQP/ClassX_2021_22/Science-SQP_Term2.pdf

Also used in: official-12

11. pyq-2026-cf1c5280affd78bfb04001a2

CBSE Class X Science 2026 First Board 31-3-3 | PYQ | Year/session: 2026 / 2026 First Board | Paper code: 31/3/3 | Source question: 35 | Original section: Section C (Physics) | Selected marks: 3 | PDF pages (one-based): 25

<https://www.cbse.gov.in/cbsenew/question-paper/2026/X/Science.zip>

No cross-paper reuse.

12. SQP_2024-25_q36_VI_B

CBSE Class X Science (086) Sample Question Paper 2024-25 (English) | SQP | Year/session: 2024-25 / 2024-25 | Paper code: Not recorded | Source question: 36 VI B | Original section: Section-D | Selected marks: 5 | PDF pages (one-based): 13

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-SQP.pdf

No cross-paper reuse.

13. SQP_2023-24_q39_iii

CBSE Class X Science (086) Sample Question Paper 2023-24 (English) | SQP | Year/session: 2023-24 / 2023-24 | Paper code: Not recorded | Source question: 39 iii | Original section: Section-E | Selected marks: 4 | PDF pages (one-based): 8

https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-SQP.pdf

Also used in: official-07, official-10, official-14

14. sqp_2022-23_q36

CBSE Class X Science (086) Sample Question Paper 2022-23 | SQP | Year/session: 2022-23 / 2022-23 | Paper code: Not recorded | Source question: 36 | Original section: Section D | Selected marks: 5 | PDF pages (one-based): 9

https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-SQP.pdf

Also used in: official-11