

Official-source Electricity compilation 04

Mixed-source chapter worksheet • cross-paper reuse disclosed

Total: 34 marks • Suggested time: 68 minutes

Instructions and reuse disclosure

Curated compilation of official CBSE source questions, not a CBSE-issued chapter paper. Original source labels and exact source images are retained.

Answer every selected question. Only one selected source-slot alternative appears in this paper; do not answer or count excluded alternatives.

Questions recur across this 15-paper collection. Reuse is disclosed per question in the source appendix; these are not 15 disjoint official papers.

Sections use available source marks: A MCQ; B 2 marks; C 3 marks; D 5 marks or source-marked case questions. Case marks are not inflated to five.

Section A — MCQ

Compilation questions 1-4; 4 marks. Exact source labels remain attached to each question.

Section B — 2-mark questions

Compilation questions 5-8; 8 marks. Exact source labels remain attached to each question.

Section C — 3-mark questions

Compilation questions 9-12; 12 marks. Exact source labels remain attached to each question.

Section D — 5-mark / case-based questions

Compilation questions 13-14; 10 marks. Exact source labels remain attached to each question.

Section A — MCQ

1. [1 marks] Source Q31 • 2026 First Board

31. In an electric circuit carrying current I , a $2\ \Omega$ resistor is replaced by an $8\ \Omega$ resistor without changing the connected (ideal) battery. Then : I

- (A) current becomes $\frac{I}{4}$ and potential difference $\frac{V}{4}$
- (B) current becomes $\frac{I}{4}$ and potential difference remains V
- (C) current becomes $4I$ and potential difference remains V
- (D) current becomes $4I$ and potential difference $\frac{V}{4}$

31/3/2

Page 23 of 31


P.T.O.

Source/editorial note: Visually confirmed complete replacement crop: question number, wording, all options/table values, mathematical symbols and printed marks. Whitespace normalized; mathematical glyphs represented in Unicode and stacked fractions as $I/4$ and $V/4$. Page/QR/footer debris removed from text; marks retained in marks field. No supplied diagram; table retained in text and evidence. Answers not reviewed. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

2. [1 marks] Source Q15 • 2022-23


15

1

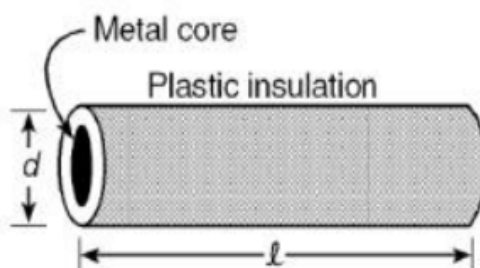

Plastic insulation surrounds a wire having diameter d and length l as shown above. A decrease in the resistance of the wire would be produced by an increase in the

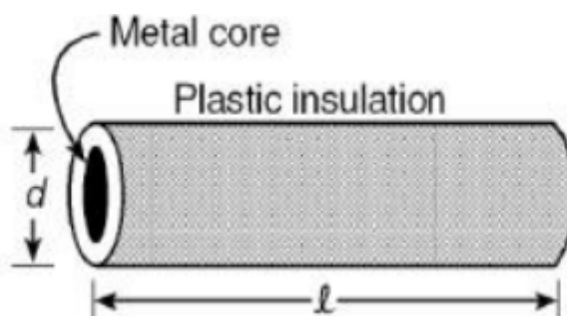- (a) length l of the wire
- (b) diameter d of the wire
- (c) temperature of the wire
- (d) thickness of the plastic insulation



3. [1 marks] Source Q13 • main

- 13.** A wire of length ' l ' is gradually stretched so that its length increases to $3l$.
If its original resistance is R , then its new resistance will be :

- | | |
|----------|-----------|
| (A) $3R$ | (B) $6R$ |
| (C) $9R$ | (D) $27R$ |

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

4. [1 marks] Source Q7 • 2019-20

- | | | |
|---|--|---|
| 7 | Unit of electric power may also be expressed as: | 1 |
| | i) volt-ampere | |
| | ii) kilowatt-hour | |
| | iii) watt-second | |
| | iv) joule-second | |

Section B — 2-mark questions

5. [2 marks] Source Q27 • main


The range of a milliammeter is 0-500 mA. There are 20 divisions between 0 and 100 mA mark on its scale. During an experiment a student observes ammeter's pointer at 3rd graduation mark after zero mark when the key is off and the pointer at 15th graduation mark after 300 mA mark when the key is inserted into the plug. Find (i) the least count, (ii) the zero error with proper sign and (iii) the value of current drawn from the battery.

Source/editorial note: Occurrence mappings retained verbatim; only primary PDF/question evidence is accepted and counted. Other occurrences require their own evidence validation. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

6. [2 marks] Source Q25 • main

25. V – I graph for two conducting wires A and B are as shown. If both wires are of the same length and same diameter, which of the two is made of a material of high resistivity ? Give reasons to justify your answer.

2

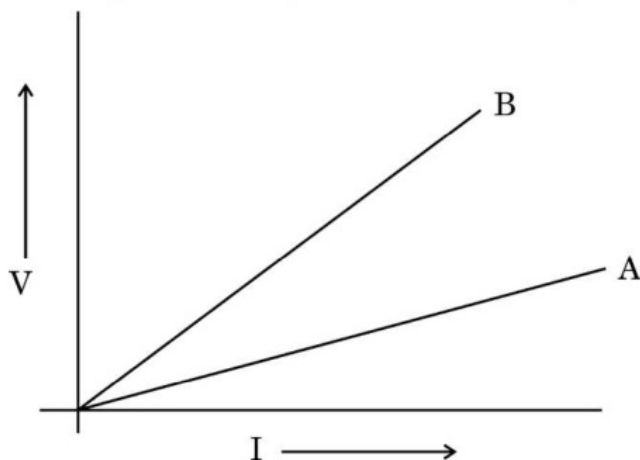

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.


7. [2 marks] Source Q25 A • 2024-25

25

Attempt either option A or B.

2

A.

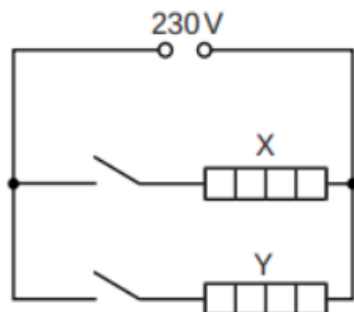

The electric circuit (above figure) in a clothes dryer contains two heaters X and Y in parallel. The above figure shows the circuit connected to a 230 V power supply. When both switches are closed, the current in X is 3.5 A.

Analyse the circuit given above and answer the following questions.

- Calculate the power developed in heater X.
- If the resistance of X is double that of Y calculate the current in heater Y.

Source/editorial note: Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

8. [2 marks] Source Q26 • 2017-18

26	The values of current I flowing in a given resistor for the corresponding values of potential difference V across the resistor are given below:					2
	I (ampere)	0.5	1.0	2.0	3.0	4.0
	V (volt)	1.6	3.4	6.7	10.2	13.2

Plot a graph between V and I and calculate the resistance of the resistor.

Source/editorial note: Practical-skills question; continues from SQP page 3 to page 4. OR alternative stored separately. Official MS states 3.2Ω and does not supply the plotted graph; data ratios are approximate (about $3.2\text{--}3.4 \Omega$). The official worked slope uses graph coordinates not listed in the table; preserved rather than silently corrected. Official answer unavailable/withheld for an identified error, omission or incomplete verification: Official slope solution captured, but required plotted graph absent from official MS; not a complete publishable model answer. Consult the linked original marking scheme with this limitation in mind.

Section C — 3-mark questions

9. [3 marks] Source Q10 • main

- 10.** (a) Calculate the resistance of a metal wire of length 2 m and area of cross-section $1.55 \times 10^{-6} \text{ m}^2$.

(Resistivity of the metal is $2.8 \times 10^{-8} \Omega \text{ m}$)


- (b) Why are alloys preferred over pure metals to make the heating elements of electrical heating devices ?

2+1


Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

10. [3 marks] Source Q12 • 2021-22

OR

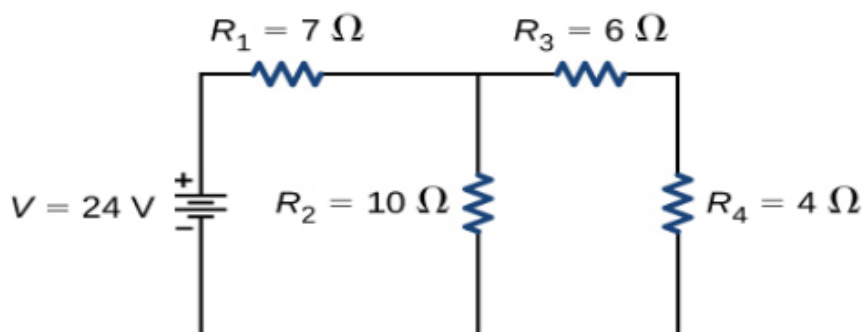

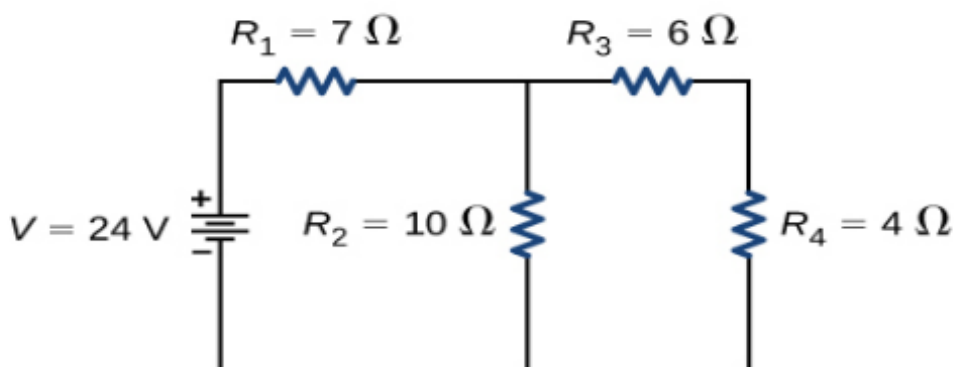Calculate the total resistance of the circuit and find the total current in the circuit.



Source/editorial note: OR alternative with its own complete circuit and stem. Official solution is an embedded image on MS p.4 and was visually transcribed. Main and OR share three exam marks.

11. [3 marks] Source Q32 • 2023-24

32	(i) State the law that explains the heating effect of current with respect to the measurable properties in an electrical circuit. (ii) List the factors on which the resistance of a conductor depends.	2+1
----	---	-----


Source/editorial note: Official MS prints $H = I^2Rt$ (digit 1, visually verified), evidently a typo for $H = I^2Rt$. Printed typo preserved in answer. Marks 2+1. Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence. Official answer unavailable/withheld for an identified error, omission or incomplete verification: Official answer retains erroneous digit 1 in $H = I^2Rt$; correct formula explained in notes. Consult the linked original marking scheme with this limitation in mind.

12. [3 marks] Source Q11 • main

11. (a) Three resistors R_1 , R_2 and R_3 are connected in parallel and the combination is connected to a battery, an ammeter, a voltmeter and a key. Draw suitable circuit diagram to show the arrangement of these circuit components along with the direction of current flowing.

- (b) Calculate the equivalent resistance of the following network :

3

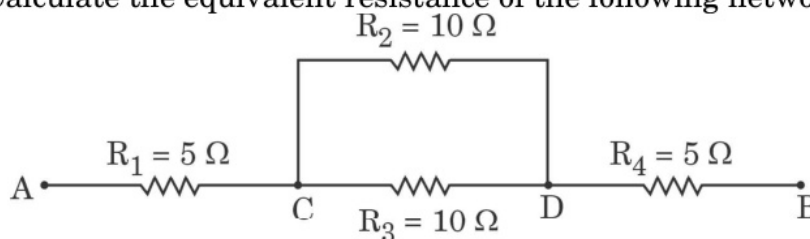

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

Section D — 5-mark / case-based questions

13. [5 marks] Source Q39 VI B • 2025-26

OR

B. Two resistors, $R_1=6\ \Omega$ and $R_2=12\ \Omega$, are connected in parallel to a 24V battery. The circuit operates for 5 minutes.

- Calculate the total heat generated in both resistors.
- If each resistor has a power rating of 100 W, determine whether it is safe to use these resistors in the circuit.

Source/editorial note: Total 5 marks from scheme; no subpart mark allocation printed. Original “Heat generate” and “both resistor” retained. Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

14. [5 marks] Source Q36 • compartment

36. (a) (i) Write the relation between the electrical resistivity ‘ ρ ’ and the resistance ‘ R ’ of a cylindrical conductor of length ‘ l ’ and area of cross-section ‘ A ’. Use this relationship to determine the SI unit of ‘ ρ ’.
- (ii) Find the electrical resistivity of the material of a wire of length 120 cm and diameter 0.4 mm. The resistance of this wire is $3\ \Omega$.

5

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

Solutions and verification status

Only explicitly verified solutions are printed. A missing solution is not a claim that the question is unsolvable.

Question 1 — pyq-2026-a53ce36a0fd993043d965609

Official answer unavailable/withheld: No independently verified official answer supplied.

Original marking scheme (see limitation above): https://www.cbse.gov.in/cbsenew/marketing-scheme/2026/X/086_SCIENCE.zip

Question 2 — sqp_2022-23_q15

(b) diameter d of the wire

15.	(b) diameter d of the wire	1
-----	----------------------------	---

Marking-scheme PDF page(s): [1]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-MS.pdf

Question 3 — pyq-2025-89ec80e87c4adf229cc3e824

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 4 — cbse_sqp_2019-20_electricity_q7

i) volt-ampere. Power = Voltage × Current.

7	i) volt-ampere Power = Voltage x Current.	1 mark
---	--	--------

Marking-scheme PDF page(s): [1]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_MS.pdf

Question 5 — pyq-2018-7253f82c5332b612f2b92314

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 6 — pyq-2023-246eac3017f0793c27bba6a6

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 7 — SQP_2024-25_q25_A

A. $P = VI$ (1)

$= 230 \times 3.5 = 805 \text{ W}$

$I \propto 1/R$, so half the resistance means double the current.

Therefore, current in Y = 7.0 A. (1)

25	<u>Student to attempt either A or B.</u>	
	A. $P = VI$	(1)
	$= 230 \times 3.5 = 805 \text{ W}$	
	$I \propto \frac{1}{R}$, so half the resistance means double the current.	
	Therefore, current in Y = 7.0 A.	(1)

Marking-scheme PDF page(s): [3]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-MS.pdf

Question 8 — cbse_sqp_2017-18_electricity_q26

Official answer unavailable/withheld: Official slope solution captured, but required plotted graph absent from official MS; not a complete publishable model answer.

Original marking scheme (see limitation above): https://cbseacademic.nic.in/web_material/SQP/CLASS_X_2017_18/Science_MS.pdf

Question 9 — pyq-2022-cfec2ef8067dd02793a5ebf2

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 10 — sqp_2021-22_term2_q12_OR

R3 and R4 are in series: $R_5 = 6 + 4 = 10 \Omega$. R5 and R2 are in parallel: $R_6 = (10 \times 10)/(10 + 10) = 5 \Omega$. R1 and R6 are in series: total resistance = $7 + 5 = 12 \Omega$. With $V = 24 \text{ V}$, $I = V/R = 24/12 = 2 \text{ A}$.

12	5 ohm, 10 ohm and R_1 are in series $1/R_p = 1/5 + 1/10 + 1/R_1$ $1/R_p = (2+1)/10 + 1/R_1$ $= 3/10 + 1/R_1$ $1/R_p = (3 R_1 + 10)/10 R_1$ $R_p = 10 R_1 / (3 R_1 + 10)$ Now, 6 ohm, 6 ohm and R_p are in series Thus, $R_{eq} = 12 + 10 R_1 / (3 R_1 + 10) \text{ ----- (1)}$ (1 mark) $V = I R_{eq}$ From the circuit $R_{eq} = 30/2 = 15 \text{ A ----- (2)}$ (1 mark) Equating (1) and (2) $12 + 10 R_1 / (3 R_1 + 10) = 15$ $10 R_1 / (3 R_1 + 10) = 3$ $10 R_1 = (9 R_1 + 30)$ Thus, $R_1 = 30 \text{ ohm}$. (1 mark) OR R3 and R4 are in series, hence the equivalent resistance of those two = $R_5 = R_3 + R_4 = 10 \text{ ohms}$. 0.5 marks R5 and R2 are in parallel. Let R_6 be the equivalent resistance for them. Hence $R_6 = (R_5 \times R_2)/(R_5 + R_2) = 100/20 = 5 \text{ ohms}$ 0.5 marks Now R_1 and R_6 are in series and hence the final equivalent resistance of the entire circuit is $R = R_1 + R_6 = 12 \text{ ohms}$. 1 mark By Ohm's Law we know that $V = IR$, hence $I = V/R$. Hence the current in the circuit is $24/12 \text{ A} = 2 \text{ A}$ (Final Answer) 1 mark (0.5+0.5+1+1)	3
----	---	---

Question 11 — SQP_2023-24_q32

Official answer unavailable/withheld: Official answer retains erroneous digit 1 in $H = I^2 R t$; correct formula explained in notes.

Original marking scheme (see limitation above): https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-M S.pdf

Question 12 — pyq-2022-9fe4ca3895577ede74461fc1

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 13 — SQP_2025-26_q39_VI_B

B.

Given data:

Resistor $R_1 = 6 \Omega$

Resistor $R_2 = 12 \Omega$

Voltage $V = 24 \text{ V}$

Time $t = 5 \text{ Minutes} = 5 \times 60 = 300 \text{ seconds}$

Step 1: Calculate the Current through each Resistor

Since the resistors are connected in parallel, the voltage across each resistor is the same as the battery voltage, $V = 24 \text{ V}$.

Using Ohm's Law,

Current through R_1 : $I_1 = V/R_1 = 24/6 = 4 \text{ A}$

Current through R_2 : $I_2 = V/R_2 = 24/12 = 2 \text{ A}$

Step 2: Calculate the Heat Generated in Each Resistor

Using Joule's Law of Heating, $H = I^2 R t$:

Heat generate in R_1 : $H_1 = 4^2 \times 6 \times 300 = 28800 \text{ J}$

Heat generate in R_2 : $H_2 = 2^2 \times 12 \times 300 = 14400 \text{ J}$

Total Heat Generated H : $H = H_1 + H_2 = 28800 + 14400 = 43200 \text{ J}$

So, the total heat generated in both resistor is 43200 J.

Step 3 : Determine if each Resistor is safe

The power dissipated by each resistor can be calculated using $P = V \times I$

Power dissipated by R_1 : $P_1 = 24 \times 4 = 96 \text{ W}$

Power dissipated by R_2 : $P_2 = 24 \times 2 = 48 \text{ W}$

Given that the power rating of each resistor is 100 W:

R_1 is operating at 96 W, which is within the 100 W limit. Hence, it is safe.

R_2 is operating at 48 W, which is also within the 100 W limit. Hence, it is safe.

B.

Given data:

- Resistor $R_1 = 6 \Omega$
- Resistor $R_2 = 12 \Omega$
- Voltage $V = 24 \text{ V}$
- Time $t = 5 \text{ Minutes} = 5 \times 60 = 300 \text{ seconds}$

Step 1: Calculate the Current through each Resistor

Since the resistors are connected in parallel, the voltage across each resistor is the same as the battery voltage, $V = 24 \text{ V}$.

Using Ohm's Law, $I = \frac{V}{R}$:

Current through R_1

$$I_1 = \frac{V}{R_1} = \frac{24 \text{ V}}{6 \Omega} = 4 \text{ A}$$

Current through R_2 :

$$I_2 = \frac{V}{R_2} = \frac{24 \text{ V}}{12 \Omega} = 2 \text{ A}$$

Step 2: Calculate the Heat Generated in Each Resistor

Using Joule's Law of Heating, $H = I^2 R t$:

- Heat generate in R_1 :

$$H_1 = I_1^2 \times R_1 \times t = (4 \text{ A})^2 \times 6 \Omega \times 300 \text{ s}$$

$$H_1 = 16 \times 6 \times 300 = 28800 \text{ J}$$

- Heat generate in R_2 :

$$H_2 = I_2^2 \times R_2 \times t = (2 \text{ A})^2 \times 12 \Omega \times 300 \text{ s}$$

$$H_2 = 4 \times 12 \times 300 = 14400 \text{ J}$$

- Total Heat Generated H :

$$H_{\text{total}} = H_1 + H_2 = 28800 \text{ J} + 14400 \text{ J} = 43200 \text{ J}$$

So, the total heat generated in both resistor is **43200 J**.

Step 3 : Determine if each Resistor is safe

The power dissipated by each resistor can be calculated using $P = V \times I$

- Power dissipated by R_1 :

$$P_1 = V \times I_1 = 24 \text{ V} \times 4 \text{ A} = 96 \text{ W}$$

- Power dissipated by R_2 :

$$P_2 = V \times I_2 = 24 \text{ V} \times 2 \text{ A} = 48 \text{ W}$$

Given that the power rating of each resistor is 100 W:

- R_1 is operating at 96 W, which is within the 100 W limit. Hence, it is safe.
- R_2 is operating at 48 W, which is also within the 100 W limit. Hence, it is safe.

Question 14 — pyq-2024-17a293a3889e84f2b1aa8c67

Official answer unavailable/withheld: No independently verified official answer supplied.

Per-question source appendix

Original CBSE questions/images remain attributed to their source. Compilation selection and numbering are editorial. The full Science source PDFs may include unrelated chapters; only selected Electricity crops form this worksheet.

1. pyq-2026-a53ce36a0fd993043d965609

CBSE Class X Science 2026 First Board 31-3-2 | PYQ | Year/session: 2026 / 2026 First Board | Paper code: 31/3/2 | Source question: 31 | Original section: Section C (Physics) | Selected marks: 1 | PDF pages (one-based): 23

<https://www.cbse.gov.in/cbsenew/question-paper/2026/X/Science.zip>

Also used in: official-08, official-14

2. sqp_2022-23_q15

CBSE Class X Science (086) Sample Question Paper 2022-23 | SQP | Year/session: 2022-23 / 2022-23 | Paper code: Not recorded | Source question: 15 | Original section: Section A | Selected marks: 1 | PDF pages (one-based): 5

https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-SQP.pdf

Also used in: official-02, official-08, official-10, official-12, official-14

3. pyq-2025-89ec80e87c4adf229cc3e824

CBSE — Class X Science — 2025 — main — 31/3/1 | PYQ | Year/session: 2025 / main | Paper code: 31/3/1 | Source question: 13 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 9

https://www.cbse.gov.in/cbsenew/question-paper/2025/X/086_Science.zip

Also used in: official-03, official-13

4. cbse_sqp_2019-20_electricity_q7

Class-X Science-086 SAMPLE QUESTION PAPER 2019-20 | SQP | Year/session: 2019-20 / 2019-20 | Paper code: Not recorded | Source question: 7 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 4

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_SQP.pdf

Also used in: official-02, official-08, official-12, official-14

5. pyq-2018-7253f82c5332b612f2b92314

CBSE — Class X Science — 2018 — 31/B — main | PYQ | Year/session: 2018 / main | Paper code: 31/B | Source question: 27 | Original section: SECTION-B | Selected marks: 2 | PDF pages (one-based): 15

https://www.cbse.gov.in/curric~1/qpms2018/qp_10/Science.zip

Also used in: official-07, official-12

6. pyq-2023-246eac3017f0793c27bba6a6

CBSE — Class X Science — 2023 — main — 31/2/1 | PYQ | Year/session: 2023 / main | Paper code: 31/2/1 | Source question: 25 | Original section: SECTION B | Selected marks: 2 | PDF pages (one-based): 15

<https://www.cbse.gov.in/cbsenew/question-paper/2023/X/SCIENCE.zip>

Also used in: official-07, official-08, official-11, official-14

7. SQP_2024-25_q25_A

CBSE Class X Science (086) Sample Question Paper 2024-25 (English) | SQP | Year/session: 2024-25 / 2024-25 | Paper code: Not recorded | Source question: 25 A | Original section: Section-B | Selected marks: 2 | PDF pages (one-based): 6

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-SQP.pdf

Also used in: official-09, official-14

8. cbse_sqp_2017-18_electricity_q26

Sample Question Paper 2017-18 — Science — Class - X | SQP | Year/session: 2017-18 / 2017-18 | Paper code: Not recorded | Source question: 26 | Original section: SECTION - B | Selected marks: 2 | PDF pages (one-based): 3, 4

https://cbseacademic.nic.in/web_material/SQP/CLASS_X_2017_18/Science_SQP.pdf

Also used in: official-10, official-15

9. pyq-2022-cfec2ef8067dd02793a5ebf2

CBSE — Class X Science — 2022 — main — 31/1/2 | PYQ | Year/session: 2022 / main | Paper code: 31/1/2 | Source question: 10 | Original section: SECTION B | Selected marks: 3 | PDF pages (one-based): 7

<https://www.cbse.gov.in/cbsenew/question-paper/2022/X/Scince.zip>

Also used in: official-06, official-12

10. sqp_2021-22_term2_q12_OR

CBSE Class X Science (086) Sample Question Paper 2021-22 — Term 2 | SQP | Year/session: 2021-22 / 2021-22 | Paper code: Not recorded | Source question: 12 | Original section: Section B | Selected marks: 3 | PDF pages (one-based): 4

https://cbseacademic.nic.in/web_material/SQP/ClassX_2021_22/Science-SQP_Term2.pdf

Also used in: official-07, official-14

11. SQP_2023-24_q32

CBSE Class X Science (086) Sample Question Paper 2023-24 (English) | SQP | Year/session: 2023-24 / 2023-24 | Paper code: Not recorded | Source question: 32 | Original section: Section-C | Selected marks: 3 | PDF pages (one-based): 5

https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-SQP.pdf

Also used in: official-09, official-13

12. pyq-2022-9fe4ca3895577ede74461fc1

CBSE — Class X Science — 2022 — main — 31/1/1 | PYQ | Year/session: 2022 / main | Paper code: 31/1/1 | Source question: 11 | Original section: SECTION B | Selected marks: 3 | PDF pages (one-based): 7

<https://www.cbse.gov.in/cbsenew/question-paper/2022/X/Scince.zip>

Also used in: official-07, official-10

13. SQP_2025-26_q39_VI_B

CBSE Class X Science (086) Sample Question Paper 2025-26 (English) | SQP | Year/session: 2025-26 / 2025-26 | Paper code: Not recorded | Source question: 39 VI B | Original section: Section - C | Selected marks: 5 | PDF pages (one-based): 15

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-SQP.pdf

No cross-paper reuse.

14. pyq-2024-17a293a3889e84f2b1aa8c67

CBSE — Class X Science — 2024 — compartment — 31/S/1 | PYQ | Year/session: 2024 / compartment | Paper code: 31/S/1 | Source question: 36 | Original section: SECTION D | Selected marks: 5 | PDF pages (one-based): 23

<https://www.cbse.gov.in/cbsenew/question-paper/2024-COMPTT/X/SCIENCE.zip>

Also used in: official-03, official-06, official-13, official-15