

Official-source Electricity compilation 07

Mixed-source chapter worksheet • cross-paper reuse disclosed

Total: 33 marks • Suggested time: 66 minutes

Instructions and reuse disclosure

Curated compilation of official CBSE source questions, not a CBSE-issued chapter paper. Original source labels and exact source images are retained.

Answer every selected question. Only one selected source-slot alternative appears in this paper; do not answer or count excluded alternatives.

Questions recur across this 15-paper collection. Reuse is disclosed per question in the source appendix; these are not 15 disjoint official papers.

Sections use available source marks: A MCQ; B 2 marks; C 3 marks; D 5 marks or source-marked case questions. Case marks are not inflated to five.

Section A — MCQ

Compilation questions 1-4; 4 marks. Exact source labels remain attached to each question.

Section B — 2-mark questions

Compilation questions 5-8; 8 marks. Exact source labels remain attached to each question.

Section C — 3-mark questions

Compilation questions 9-12; 12 marks. Exact source labels remain attached to each question.

Section D — 5-mark / case-based questions

Compilation questions 13-14; 9 marks. Exact source labels remain attached to each question.

Section A — MCQ

1. [1 marks] Source Q30 • 2026 First Board

- 30.** The correct way to connect an ammeter and a voltmeter in an electric circuit is : 1
- (A) Ammeter in parallel and voltmeter in series
 - (B) Ammeter and voltmeter both in parallel
 - (C) Ammeter in series and voltmeter in parallel
 - (D) Ammeter and voltmeter both in series

Source/editorial note: Visually confirmed complete replacement crop: question number, wording, all options/table values, mathematical symbols and printed marks. Whitespace normalized; mathematical glyphs represented in Unicode and stacked fractions as $\frac{1}{4}$ and $\frac{V}{4}$. Page/QR/footer debris removed from text; marks retained in marks field. No supplied diagram; table retained in text and evidence. Answers not reviewed. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

2. [1 marks] Source Q19 • main

19. *Assertion (A)* : Nichrome is an alloy which is commonly used in electrical heating devices such as electric irons, toasters, etc.

Reason (R) : The resistivity of nichrome is high and its resistance decreases with increase in temperature.

For Questions number 17 to 20, two statements are given — one labelled as Assertion (A) and the other labelled as Reason (R). Select the correct answer to these questions from the codes (A), (B), (C) and (D) as given below.

- (A) Both Assertion (A) and Reason (R) are true and Reason (R) is the correct explanation of Assertion (A).
- (B) Both Assertion (A) and Reason (R) are true, but Reason (R) is **not** the correct explanation of Assertion (A).
- (C) Assertion (A) is true, but Reason (R) is false.
- (D) Assertion (A) is false, but Reason (R) is true.

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

3. [1 marks] Source Q14 • main

14. An electric iron of resistance $20\ \Omega$ draws a current of 5 A. The heat developed in the iron in 30 seconds is :

- (A) 15000 J
- (B) 6000 J
- (C) 1500 J
- (D) 3000 J

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

4. [1 marks] Source Q6 • 2019-20

6 When a 4V battery is connected across an unknown resistor there is a current of 100 mA in the circuit. The value of the resistance of the resistor is:

- i) $4\ \Omega$
- ii) $40\ \Omega$
- iii) $400\ \Omega$
- iv) $0.4\ \Omega$

Source/editorial note: Original spelling “resister” retained. Q6 mark is printed on the preceding page (page 3); Section A instructions and the MS both confirm 1 mark.

Section B — 2-mark questions


5. [2 marks] Source Q27 • main

The range of a milliammeter is 0-500 mA. There are 20 divisions between 0 and 100 mA mark on its scale. During an experiment a student observes ammeter's pointer at 3rd graduation mark after zero mark when the key is off and the pointer at 15th graduation mark after 300 mA mark when the key is inserted into the plug. Find (i) the least count, (ii) the zero error with proper sign and (iii) the value of current drawn from the battery.

Source/editorial note: Occurrence mappings retained verbatim; only primary PDF/question evidence is accepted and counted. Other occurrences require their own evidence validation. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

6. [2 marks] Source Q25 • main

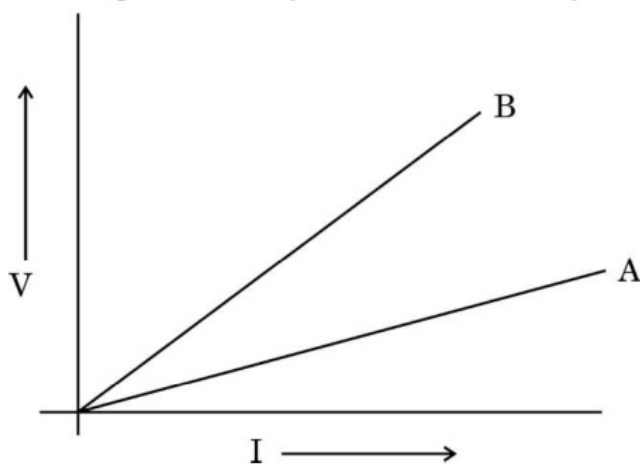
- 25.** V – I graph for two conducting wires A and B are as shown. If both wires are of the same length and same diameter, which of the two is made of a material of high resistivity ? Give reasons to justify your answer. 2



Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

7. [2 marks] Source Q34 B • 2025-26

B.

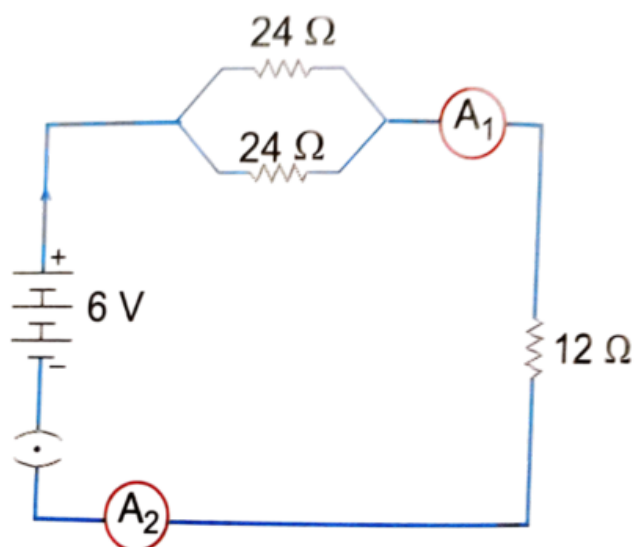

Study the circuit and find out-

- (i) Current in 12 ohm resistor
- (ii) Difference in the readings of ammeter A_1 and A_2 if any

Source/editorial note: Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

8. [2 marks] Source Q34 A • 2026-27

34

Attempt either option A or B.

2

A.

- I. State Joule's Law of heating.
- II. What happens to the heat produced in a conductor if the resistance is doubled while keeping other variables constant?

Source/editorial note: Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

Section C — 3-mark questions

9. [3 marks] Source Q12 • compartment


- 12.** Define the term electric power. An electric device of resistance R when connected across an electric source of voltage V draws a current I . Derive an expression for the power in terms of resistance R and voltage V . What is the power of a device of resistance $400\ \Omega$ operating at 200 V ?

3


Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

10. [3 marks] Source Q12 • 2021-22

OR

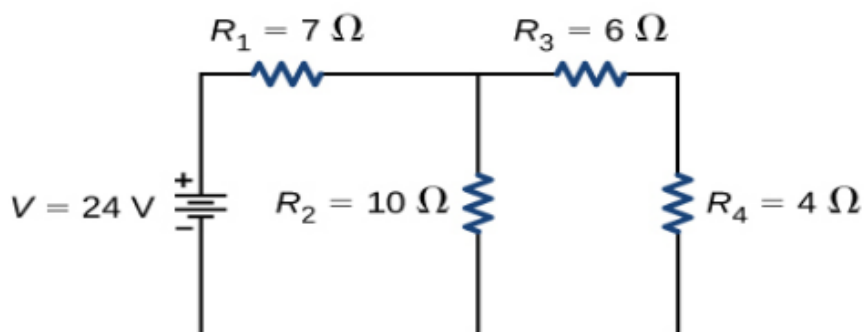

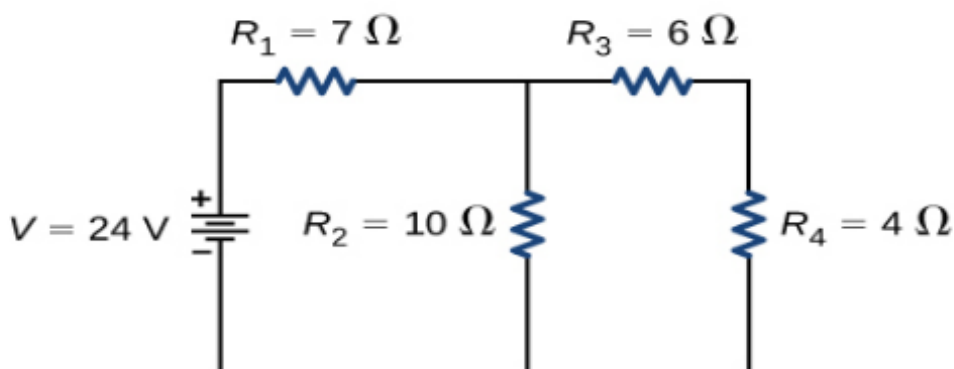Calculate the total resistance of the circuit and find the total current in the circuit.




Source/editorial note: OR alternative with its own complete circuit and stem. Official solution is an embedded image on MS p.4 and was visually transcribed. Main and OR share three exam marks.

11. [3 marks] Source Q11 • main

11. (a) Three resistors R_1 , R_2 and R_3 are connected in parallel and the combination is connected to a battery, an ammeter, a voltmeter and a key. Draw suitable circuit diagram to show the arrangement of these circuit components along with the direction of current flowing.

- (b) Calculate the equivalent resistance of the following network :

3

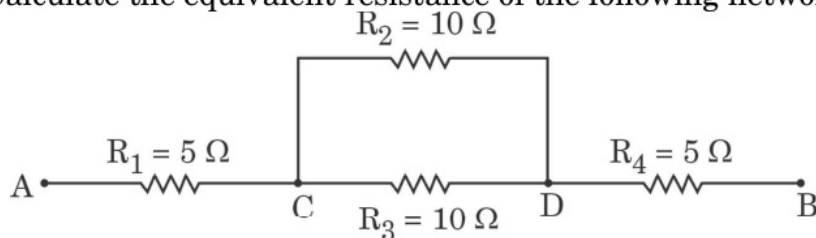

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

12. [3 marks] Source Q36 • 2026 First Board

- 36.** (a) Name a device which is used to :
- Maintain a constant potential difference in a circuit.
 - Change the electric current in an electric circuit.
- (b) When the potential difference between the terminals of an electric heater is 110 V, a current of 5 A flows through it. What will be the value of current flowing through it when the potential difference is increased to 220 V ?


3

Source/editorial note: Question text, numbering, printed marks, subparts/internal choices, diagram labels and complete crop boundaries visually checked against saved original-PDF replacement crops, using JPEG quality 80 and maximum dimension 900 px. Whitespace normalized; original wording retained. No MCQ options in this question. Page furniture is not question text. Answer and marking scheme not verified. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

Section D — 5-mark / case-based questions

13. [5 marks] Source Q36 B • 2024-25

B.

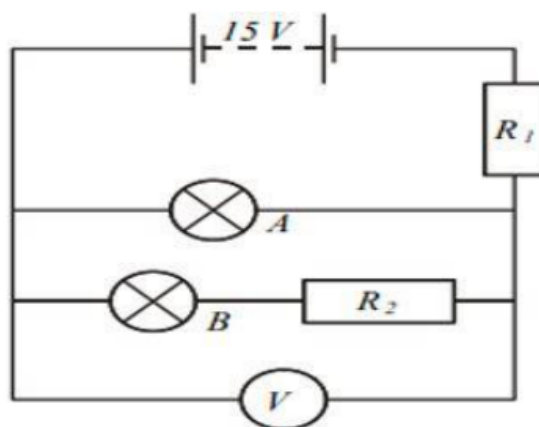

As shown in the figure above A and B are two lamps. Lamp A is rated at 12 V, 24W. Lamp B is rated at 6.0 V. When lamp B operates at its rated voltage, the current in it is 3.0 A. The values of R_1 and R_2 are chosen so that both lamps operate at their rated voltages.

Based on the information given, answer the following.

- Calculate the current in Lamp A.
- State and give reason for the reading of the Voltmeter.
- Calculate the resistance of R_2 .
- Find the value of the resistance R_1 .

Source/editorial note: Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

14. [4 marks] Source Q39 iii • 2023-24

39	The diagram shows a 12V battery on the left. The positive terminal is at the top. A wire goes from the positive terminal to a switch labeled 'A'. The switch has three positions: 1 (top), 2 (middle), and 3 (bottom). Position 1 is connected to the top of the first 4.0 Ω lamp. Position 2 is connected to the top of the second 4.0 Ω lamp. Position 3 is connected to the top of the first 12 Ω lamp. The bottom terminals of all four lamps are connected to a common wire that returns to the negative terminal of the battery. Vinita and Ahmed demonstrated a circuit that operates the two headlights and the two sidelights of a car, in their school exhibition. Based on their demonstrated circuit, answer the following questions. - State what happens when switch A is connected to - Position 2 - Position 3 - Find the potential difference across each lamp when lit. - Calculate the current - in each $12\ \Omega$ lamp when lit. - In each $4\ \Omega$ lamp when lit.	1+1+2
----	---	-------

Source/editorial note: Includes common (i), (ii) and main (iii); 1+1+2 marks. Original scheme mislabels second line of (i) as (a). Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

Solutions and verification status

Only explicitly verified solutions are printed. A missing solution is not a claim that the question is unsolvable.

Question 1 — pyq-2026-8f6db37837565412c602b458

Official answer unavailable/withheld: No independently verified official answer supplied.

Original marking scheme (see limitation above): https://www.cbse.gov.in/cbsenew/marketing-scheme/2026/X/086_SCIENCE.zip

Question 2 — pyq-2025-1aee07c91b9869601a83c309

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 3 — pyq-2024-a415e02467405f8b9fbacfc3

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 4 — cbse_sqp_2019-20_electricity_q6

ii) $40\ \Omega$. $V = IR$; $V = 4\text{ V}$; $I = 100\text{ mA} = 0.1\text{ A}$. $R = V/I = 4/0.1\ \Omega = 40\ \Omega$.

6	ii) $40\ \Omega$. $V=IR$, $V = 4\text{ V}$, $I = 100\text{ mA} = 0.1\text{ A}$ Hence $R = V/I = 4/0.1\ \Omega = 40\ \Omega$.	1 mark
---	--	--------

Marking-scheme PDF page(s): [1]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_MS.pdf

Question 5 — pyq-2018-7253f82c5332b612f2b92314

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 6 — pyq-2023-246eac3017f0793c27bba6a6

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 7 — SQP_2025-26_q34_B

B.

(i) $1/R_P = 1/R_1 + 1/R_2 = 1/24 + 1/24 = 2/24$

$R_P = 12\text{ ohms}$

$R_T = R_P + 12 = 24\text{ ohms}$

$I = V/R = 6/24 = 0.25\text{ A}$

(ii) Same readings of A_1 and A_2

B.

(i)

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{24} + \frac{1}{24} = \frac{2}{24}$$

$$R_p = 12 \text{ ohms}$$

$$R_T = R_p + 12 = 24 \text{ ohms}$$

$$I = \frac{V}{R} = \frac{6}{24} = 0.25 \text{ A}$$

(ii) Same readings of A_1 and A_2

Marking-scheme PDF page(s): [7]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-MS.pdf

Question 8 — SQP_2026-27_q34_A

A.

I. Joule's law of heating: The heat produced in a resistor is

(i) directly proportional to the square of current for a given resistance,

(ii) directly proportional to resistance for a given current, and

(iii) directly proportional to the time for which the current flows through the resistor.

$$H = I^2 R t,$$

where 'I' is current and 'R' is resistance. (1)

II. If resistance is doubled: For the same current I, heat H becomes

$$H = I^2 (2R) t = 2I^2 R t = 2H,$$

i.e. heat doubles. (1)

34

Student to attempt either A or B.

2

A.

I. Joule's law of heating: The heat produced in a resistor is

(i) directly proportional to the square of current for a given resistance,

(ii) directly proportional to resistance for a given current, and

(iii) directly proportional to the time for which the current flows through the resistor.

$$H = I^2 R t,$$

where 'I' is current and 'R' is resistance. (1)

II. If resistance is doubled: For the same current I, heat H becomes

$$H = I^2 (2R) t = 2I^2 R t = 2H,$$

i.e. heat doubles. (1)

Marking-scheme PDF page(s): [7]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2026_27/Science-MS.pdf

Question 9 — pyq-2022-4f106d54aeecf637b6b663fc

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 10 — sqp_2021-22_term2_q12_OR

R3 and R4 are in series: $R_5 = 6 + 4 = 10 \Omega$. R5 and R2 are in parallel: $R_6 = (10 \times 10)/(10 + 10) = 5 \Omega$. R1 and R6 are in series: total resistance = $7 + 5 = 12 \Omega$. With $V = 24 \text{ V}$, $I = V/R = 24/12 = 2 \text{ A}$.

12	5 ohm, 10 ohm and R_1 are in series $1/R_p = 1/5 + 1/10 + 1/R_1$ $1/R_p = (2+1)/10 + 1/R_1$ $= 3/10 + 1/R_1$ $1/R_p = (3 R_1 + 10)/10 R_1$ $R_p = 10 R_1 / (3 R_1 + 10)$ Now, 6 ohm, 6 ohm and R_p are in series Thus, $R_{eq} = 12 + 10 R_1 / (3 R_1 + 10) \text{ ----- (1)} \quad (1 \text{ mark})$ $V = I R_{eq}$ From the circuit $R_{eq} = 30/2 = 15 \text{ A ----- (2)} \quad (1 \text{ mark})$ Equating (1) and (2) $12 + 10 R_1 / (3 R_1 + 10) = 15$ $10 R_1 / (3 R_1 + 10) = 3$ $10 R_1 = (9 R_1 + 30)$ Thus, $R_1 = 30 \text{ ohm}$. (1 mark) OR R3 and R4 are in series, hence the equivalent resistance of those two = $R_5 = R_3 + R_4 = 10 \text{ ohms}$. 0.5 marks R5 and R2 are in parallel. Let R_6 be the equivalent resistance for them. Hence $R_6 = (R_5 \times R_2)/(R_5 + R_2) = 100/20 = 5 \text{ ohms}$ 0.5 marks Now R_1 and R_6 are in series and hence the final equivalent resistance of the entire circuit is $R = R_1 + R_6 = 12 \text{ ohms}$. 1 mark By Ohm's Law we know that $V = IR$, hence $I = V/R$. Hence the current in the circuit is $24/12 \text{ A} = 2 \text{ A}$ (Final Answer) 1 mark (0.5+0.5+1+1)	3
----	--	---

Marking-scheme PDF page(s): [4]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2021_22/Science-MS_Term2.pdf

Question 11 — pyq-2022-9fe4ca3895577ede74461fc1

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 12 — pyq-2026-32c755bd7a305a8fe9cf5451

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 13 — SQP_2024-25_q36_B

B.

(i) Use of $P = IV$ (0.5)

$$I = P \div V = 24 \text{ W} \div 12\text{V}$$

Current in lamp A - 2 A (0.5)

(ii) Voltmeter reading = 12 V (0.5)

Lamp A and Lamp B are in parallel.

Hence p.d. across the arm containing A = p.d. across arm containing B

= 12 V (from a) (0.5)

(iii) p.d. across R_2 + p.d. across B = 12 V. (0.5)

p.d. across B = 6 V (given)

Hence p.d. across R_2 = 12 V - 6 V = 6V (0.5)

Current through R_2 = Current through B = 3A (given) (0.5)

Use of $R = V/I$

$$R_2 = 6\text{V}/3\text{A} = 2\Omega \text{ (0.5)}$$

(iv) Current through R_1 = Total Current = 3A+2A = 5A

p.d. across R_1 = 15V - 12 V = 3V (0.5)

$$R_1 = 3\text{V}/5\text{A} = 0.6 \Omega \text{ (0.5)}$$

B.

(i) Use of $P = IV$ (0.5)

$$I = P \div V = 24 \text{ W} \div 12\text{V}$$

Current in lamp A - 2 A (0.5)

(ii) Voltmeter reading = 12 V (0.5)

Lamp A and Lamp B are in parallel.

Hence p.d. across the arm containing A = p.d. across arm containing B

= 12 V (from a) (0.5)

(iii) p.d. across R_2 + p.d. across B = 12 V. (0.5)

p.d. across B = 6 V (given)

Hence p.d. across R_2 = 12 V - 6 V = 6V (0.5)

Current through R_2 = Current through B = 3A (given) (0.5)

Use of $R = V/I$

$$R_2 = 6\text{V}/3\text{A} = 2\Omega \text{ (0.5)}$$

(iv) Current through R_1 = Total Current = 3A+2A = 5A

p.d. across R_1 = 15V - 12 V = 3V (0.5)

$$R_1 = 3\text{V}/5\text{A} = 0.6 \Omega \text{ (0.5)}$$

Marking-scheme PDF page(s): [9]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-MS.pdf

Question 14 — SQP_2023-24_q39_iii

(i) 12 Ω lamps (only) on.

(a) 4 Ω lamps (only) on [0.5+0.5]

(ii) 12 V for both sets of lamps and all of them are in parallel. [1]

(iii) 12 Ω lamps are on when the wire is connected to position 2. Voltage across both 12 Ω lamps = 12 V. $V=IR$ (Ohm's law). $I = V/R = 12/12 = 1\text{A}$. [1]

4 Ω lamps are on when the wire is connected to position 3. Voltage across both 4 Ω lamps = 12 V. $V=IR$ (Ohm's law). $I = V/R = 12/4 = 3\text{A}$. [1]

39	(i) 12 Ω lamps (only) on. (a) 4 Ω lamps (only) on [0.5+0.5] (ii) 12 V for both sets of lamps and all of them are in parallel. [1] (iii) 12 Ω lamps are on when the wire is connected to position 2. Voltage across both 12 Ω lamps = 12 V. V=IR (Ohm's law). $I = \frac{V}{R} = \frac{12}{12} = 1\text{A}.$ [1] 4 Ω lamps are on when the wire is connected to position 3. Voltage across both 4 Ω lamps = 12 V. V=IR (Ohm's law). $I = \frac{V}{R} = \frac{12}{4} = 3\text{A}.$ [1]	4
----	---	---

Marking-scheme PDF page(s): [6]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-MS.pdf

Per-question source appendix

Original CBSE questions/images remain attributed to their source. Compilation selection and numbering are editorial. The full Science source PDFs may include unrelated chapters; only selected Electricity crops form this worksheet.

1. pyq-2026-8f6db37837565412c602b458

CBSE Class X Science 2026 First Board 31-3-1 | PYQ | Year/session: 2026 / 2026 First Board | Paper code: 31/3/1 | Source question: 30 | Original section: Section C (Physics) | Selected marks: 1 | PDF pages (one-based): 23

<https://www.cbse.gov.in/cbsenew/question-paper/2026/X/Science.zip>

Also used in: official-10

2. pyq-2025-1aee07c91b9869601a83c309

CBSE — Class X Science — 2025 — main — 31/2/1 | PYQ | Year/session: 2025 / main | Paper code: 31/2/1 | Source question: 19 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 13, 11

https://www.cbse.gov.in/cbsenew/question-paper/2025/X/086_Science.zip

Also used in: official-01, official-10

3. pyq-2024-a415e02467405f8b9fbacfc3

CBSE — Class X Science — 2024 — main — 31/4/1 | PYQ | Year/session: 2024 / main | Paper code: 31/4/1 | Source question: 14 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 7

<https://www.cbse.gov.in/cbsenew/question-paper/2024/X/SCIENCE.zip>

Also used in: official-02, official-06, official-09, official-12, official-15

4. cbse_sqp_2019-20_electricity_q6

Class-X Science-086 SAMPLE QUESTION PAPER 2019-20 | SQP | Year/session: 2019-20 / 2019-20 | Paper code: Not recorded | Source question: 6 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 4

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_SQP.pdf

Also used in: official-01, official-06, official-10, official-15

5. pyq-2018-7253f82c5332b612f2b92314

CBSE — Class X Science — 2018 — 31/B — main | PYQ | Year/session: 2018 / main | Paper code: 31/B | Source question: 27 | Original section: SECTION-B | Selected marks: 2 | PDF pages (one-based): 15

https://www.cbse.gov.in/curric~1/qpms2018/qp_10/Science.zip

Also used in: official-04, official-12

6. pyq-2023-246eac3017f0793c27bba6a6

CBSE — Class X Science — 2023 — main — 31/2/1 | PYQ | Year/session: 2023 / main | Paper code: 31/2/1 | Source question: 25 | Original section: SECTION B | Selected marks: 2 | PDF pages (one-based): 15

<https://www.cbse.gov.in/cbsenew/question-paper/2023/X/SCIENCE.zip>

Also used in: official-04, official-08, official-11, official-14

7. SQP_2025-26_q34_B

CBSE Class X Science (086) Sample Question Paper 2025-26 (English) | SQP | Year/session: 2025-26 / 2025-26 | Paper code: Not recorded | Source question: 34 B | Original section: Section - C | Selected marks: 2 | PDF pages (one-based): 12

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-SQP.pdf

Also used in: official-02, official-15

8. SQP_2026-27_q34_A

CBSE Class X Science (086) Sample Question Paper 2026-27 (English) | SQP | Year/session: 2026-27 / 2026-27 | Paper code: Not recorded | Source question: 34 A | Original section: Section – C | Selected marks: 2 | PDF pages (one-based): 12

https://cbseacademic.nic.in/web_material/SQP/ClassX_2026_27/Science-SQP.pdf

Also used in: official-03

9. pyq-2022-4f106d54aeecf637b6b663fc

CBSE — Class X Science — 2022 — compartment — 31/6/1 | PYQ | Year/session: 2022 / compartment | Paper code: 31/6/1 | Source question: 12 | Original section: SECTION B | Selected marks: 3 | PDF pages (one-based): 11

<https://www.cbse.gov.in/cbsenew/question-paper/2022-COMPTT/X/SCIENCE.zip>

Also used in: official-01, official-13

10. sqp_2021-22_term2_q12_OR

CBSE Class X Science (086) Sample Question Paper 2021-22 — Term 2 | SQP | Year/session: 2021-22 / 2021-22 | Paper code: Not recorded | Source question: 12 | Original section: Section B | Selected marks: 3 | PDF pages (one-based): 4

https://cbseacademic.nic.in/web_material/SQP/ClassX_2021_22/Science-SQP_Term2.pdf

Also used in: official-04, official-14

11. pyq-2022-9fe4ca3895577ede74461fc1

CBSE — Class X Science — 2022 — main — 31/1/1 | PYQ | Year/session: 2022 / main | Paper code: 31/1/1 | Source question: 11 | Original section: SECTION B | Selected marks: 3 | PDF pages (one-based): 7

<https://www.cbse.gov.in/cbsenew/question-paper/2022/X/Scince.zip>

Also used in: official-04, official-10

12. pyq-2026-32c755bd7a305a8fe9cf5451

CBSE Class X Science 2026 First Board 31-3-1 | PYQ | Year/session: 2026 / 2026 First Board | Paper code: 31/3/1 | Source question: 36 | Original section: Section C (Physics) | Selected marks: 3 | PDF pages (one-based): 27

<https://www.cbse.gov.in/cbsenew/question-paper/2026/X/Science.zip>

No cross-paper reuse.

13. SQP_2024-25_q36_B

CBSE Class X Science (086) Sample Question Paper 2024-25 (English) | SQP | Year/session: 2024-25 / 2024-25 | Paper code: Not recorded | Source question: 36 B | Original section: Section-D | Selected marks: 5 | PDF pages (one-based): 13

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-SQP.pdf

Also used in: official-15

14. SQP_2023-24_q39_iii

CBSE Class X Science (086) Sample Question Paper 2023-24 (English) | SQP | Year/session: 2023-24 / 2023-24 | Paper code: Not recorded | Source question: 39 iii | Original section: Section-E | Selected marks: 4 | PDF pages (one-based): 8

https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-SQP.pdf

Also used in: official-02, official-10, official-14