

Official-source Electricity compilation 09

Mixed-source chapter worksheet • cross-paper reuse disclosed

Total: 35 marks • Suggested time: 70 minutes

Instructions and reuse disclosure

Curated compilation of official CBSE source questions, not a CBSE-issued chapter paper. Original source labels and exact source images are retained.

Answer every selected question. Only one selected source-slot alternative appears in this paper; do not answer or count excluded alternatives.

Questions recur across this 15-paper collection. Reuse is disclosed per question in the source appendix; these are not 15 disjoint official papers.

Sections use available source marks: A MCQ; B 2 marks; C 3 marks; D 5 marks or source-marked case questions. Case marks are not inflated to five.

Section A — MCQ

Compilation questions 1-4; 4 marks. Exact source labels remain attached to each question.

Section B — 2-mark questions

Compilation questions 5-8; 8 marks. Exact source labels remain attached to each question.

Section C — 3-mark questions

Compilation questions 9-11; 9 marks. Exact source labels remain attached to each question.

Section D — 5-mark / case-based questions

Compilation questions 12-14; 14 marks. Exact source labels remain attached to each question.

Section A — MCQ

1. [1 marks] Source Q14 • 2019-20

14 **Assertion:** A fuse wire is always connected in parallel with the mainline. 1

Reason: If a current larger than the specified value flows through the circuit, fuse wire melts.

For question numbers 13 and 14, two statements are given- one labeled *Assertion* (A) and the other labeled *Reason* (R). Select the correct answer to these questions from the codes (i), (ii), (iii) and (iv) as given below

- i) Both A and R are true and R is correct explanation of the assertion.
- ii) Both A and R are true but R is not the correct explanation of the assertion.
- iii) A is true but R is false.
- iv) A is false but R is true.

13 **Assertion:** Following are the structural isomers of butane. 1

Source/editorial note: Fuse series placement and melting from excess current are explicitly NCERT Electricity section 11.7.1 (printed p190, PDF p20). Included after independent audit overturned the batch reviewer's domestic-circuit exclusion. Shared assertion-reason choices occur on preceding PDF page 5.

2. [1 marks] Source Q14 • main

14. An electric iron of resistance $20\ \Omega$ draws a current of 5 A. The heat developed in the iron in 30 seconds is :

- | | |
|-------------|------------|
| (A) 15000 J | (B) 6000 J |
| (C) 1500 J | (D) 3000 J |

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

3. [1 marks] Source Q15 • compartment

15. The resistance of a wire does ***not*** depend on its :

- (a) Length
- (b) Area of cross-section
- (c) Shape
- (d) Material

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

4. [1 marks] Source Q13 • 2022-23

13	A complete circuit is left on for several minutes, causing the connecting copper wire to become hot. As the temperature of the wire increases, the electrical resistance of the wire (a) decreases. (b) remains the same. (c) increases. (d) increases for some time and then decreases .	1
----	--	---

Section B — 2-mark questions

5. [2 marks] Source Q27 • main

The values of current (I) flowing through a given resistor of resistance (R), for the corresponding values of potential difference (V) across the resistor are as given below :

V (volts)	0.5	1.0	1.5	2.0	2.5	3.0	4.0	5.0
I (amperes)	0.1	0.2	0.3	0.4	0.5	0.6	0.8	1.0

Plot a graph between current (I) and potential difference (V) and determine the resistance (R) of the resistor.

Source/editorial note: Occurrence mappings retained verbatim; only primary PDF/question evidence is accepted and counted. Other occurrences require their own evidence validation. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

6. [2 marks] Source Q34 VI B • 2025-26

	OR	
	B. A copper wire has a length $L=2$ m, a cross-sectional area $A=0.5 \text{ mm}^2$, and resistivity $\rho=1.7 \times 10^{-8} \Omega\text{-m}$. Calculate the resistance of another wire made of the same material whose length is twice the length of the wire but has the same cross-sectional area.	

Source/editorial note: Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.


7. [2 marks] Source Q25 A • 2024-25

25

Attempt either option A or B.

2

A.

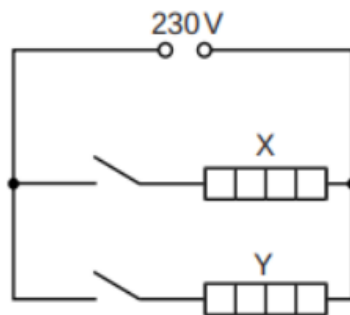

The electric circuit (above figure) in a clothes dryer contains two heaters X and Y in parallel. The above figure shows the circuit connected to a 230 V power supply. When both switches are closed, the current in X is 3.5 A.

Analyse the circuit given above and answer the following questions.

- Calculate the power developed in heater X.
- If the resistance of X is double that of Y calculate the current in heater Y.

Source/editorial note: Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

8. [2 marks] Source Q26 OR • 2017-18

OR


In a given ammeter, a student sees that needle indicates 17 divisions in ammeter while performing an experiment to verify Ohm's law. If ammeter has 10 divisions between 0 and 0.5A, then what is the value corresponding to 17 divisions?

Source/editorial note: Separate internal OR alternative to Q26; practical-skills question. The printed number 26 and 2-mark allocation occur on the previous page for the shared question slot.

Section C — 3-mark questions

9. [3 marks] Source Q36 • 2026 First Board

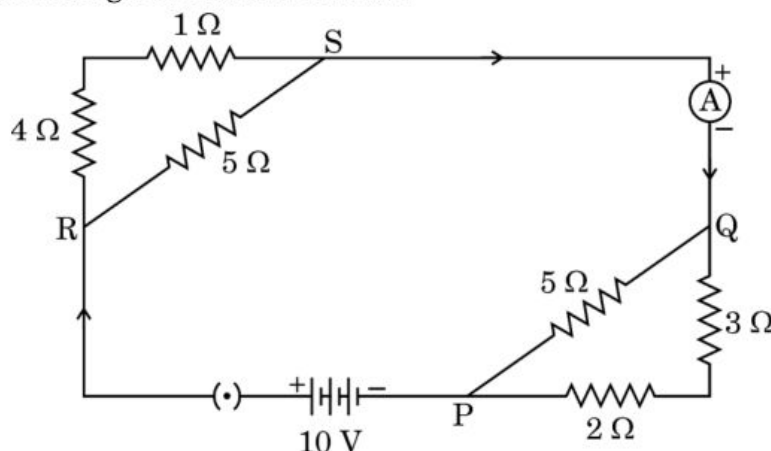36. Consider the given electric circuit :



Calculate the following :


3

- Total resistance of the circuit
- The electric current drawn from the battery
- Potential difference between points P and Q

Source/editorial note: Question text, numbering, printed marks, subparts/internal choices, diagram labels and complete crop boundaries visually checked against saved original-PDF replacement crops, using JPEG quality 80 and maximum dimension 900 px. Whitespace normalized; original wording retained. No MCQ options in this question. Page furniture is not question text. Answer and marking scheme not verified. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

10. [3 marks] Source Q37 main • 2026-27

37

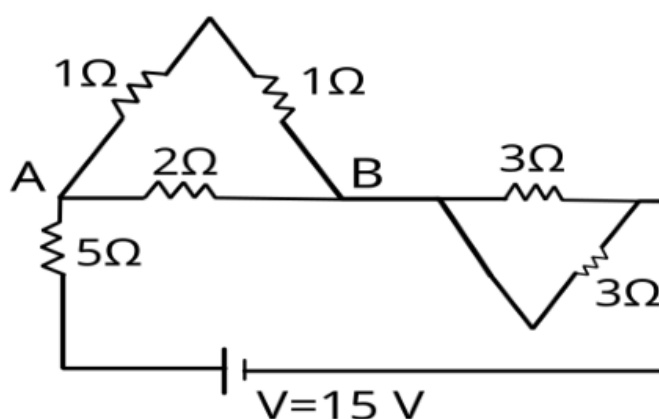

3

The figure shows a circuit with a 15 V battery connected to several resistors. Using the given circuit diagram:

- Find the total current supplied by the battery.
- Calculate the potential difference between points A and B.

Source/editorial note: Original and reduced circuit diagrams are preserved in answer evidence. Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

11. [3 marks] Source Q32 • 2023-24

32	(i) State the law that explains the heating effect of current with respect to the measurable properties in an electrical circuit. (ii) List the factors on which the resistance of a conductor depends.	2+1
----	--	-----

Source/editorial note: Official MS prints $H = I^2 R t$ (digit 1, visually verified), evidently a typo for $H = I^2 R t$. Printed typo preserved in answer. Marks 2+1. Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence. Official answer unavailable/withheld for an identified error, omission or incomplete verification: Official answer retains erroneous digit 1 in $H = I^2 R t$; correct formula explained in notes. Consult the linked original marking scheme with this limitation in mind.

Section D — 5-mark / case-based questions

12. [4 marks] Source Q39 • main


- 39.** As shown in the diagram, an electric circuit consisting of an ammeter, a voltmeter, 4 cells of 1.5 V each, a plug key with a gap XY was set up. Voltmeter and ammeter readings were recorded in the observation table for four arrangements as given below :

Arrangement No. 1 – only resistor R_1 in gap XY


Arrangement No. 2 – only resistor R_2 in gap XY

Arrangement No. 3 – Resistors R_1 and R_2 in series in gap XY

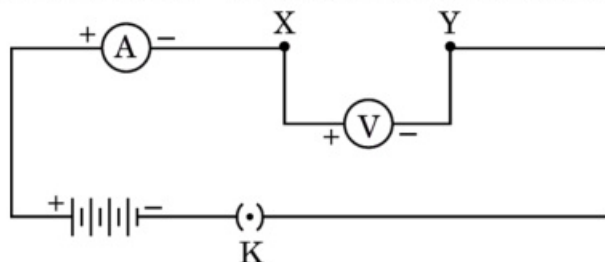Arrangement No. 4 – Resistors R_1 and R_2 in parallel in gap XY



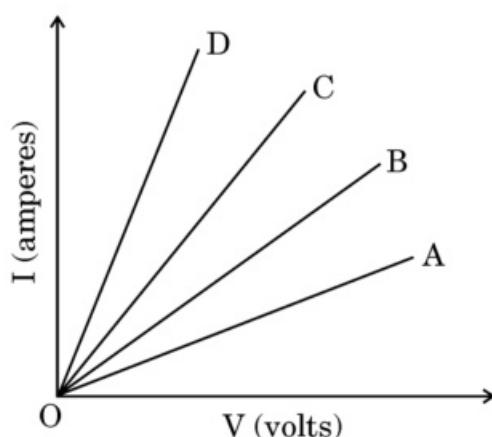Based on the observations, four V – I graphs A, B, C and D as shown in figure were drawn. Study these graphs.



- (a) Which one of the graphs represents the series combination of R_1 and R_2 ? 1
- (b) Which one of these graphs represents the parallel combination of R_1 and R_2 ? 1
- (c) (i) Show an arrangement of three resistors, each of resistance $10\ \Omega$, so that the combination has a resistance of $15\ \Omega$. Give justification for your answer. 2

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

13. [5 marks] Source Q34 • main

SECTION D

34. There are three resistors of $10\ \Omega$, $20\ \Omega$ and $30\ \Omega$ joined in parallel in a circuit. The potential difference across the electric circuit is $10\ \text{V}$.

- (a) Draw a circuit diagram for the above case.
- (b) Find the total resistance of the combination of resistors.
- (c) Calculate the electric current drawn from the same source.

5

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

14. [5 marks] Source Q39 VI A • 2025-26

For visually impaired students

A.

- (i) Explain why in household circuits only the fuse is connected in series with all the rest of the appliances but all appliances are connected in parallel to each other.
- (ii) In a household circuit, an electric heater of power $1500\ \text{W}$ and a fan of power $500\ \text{W}$ are connected in parallel to a $220\ \text{V}$ supply. A fuse rated for $10\ \text{A}$ is connected to the circuit to protect it from excessive current.
 - (a) Calculate the total current drawn by the heater and the fan.
 - (b) Determine whether the $10\ \text{A}$ fuse is appropriate for this circuit or if it will blow.

Source/editorial note: Full alternative is included: fuse series placement and heating protection are explicitly NCERT Electricity section 11.7.1 (printed p190); appliance parallel connections are section 11.6. This overlaps domestic-circuit applications but requires no magnetic effects. Full printed total is 5; MS does not specify subpart allocations. Original source typos retained. Answer text is source transcription; source crops are authoritative.

Solutions and verification status

Only explicitly verified solutions are printed. A missing solution is not a claim that the question is unsolvable.

Question 1 — SQP-2019-20-Q14

iv) Assertion is false but reason is true.

14	iv) Assertion is false but reason is true.	1 mark
----	--	--------

Marking-scheme PDF page(s): [2]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_MS.pdf

Question 2 — pyq-2024-a415e02467405f8b9fbacfc3

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 3 — pyq-2023-dc74f0e84e53633b06097022

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 4 — sqp_2022-23_q13

(c) increases

13.	(c) increases	1
-----	---------------	---

Marking-scheme PDF page(s): [1]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-MS.pdf

Question 5 — pyq-2018-ac2b7b28762938a4a2df67a3

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 6 — SQP_2025-26_q34_VI_B

Given:

Length of the wire, $l = 2 \text{ m}$

Cross-sectional area, $A = 0.5 \text{ mm}^2 = 0.5 \times 10^{-6} \text{ m}^2$

Resistivity of copper, $\rho = 1.7 \times 10^{-8} \Omega\text{-m}$

The resistance R of a wire is given by the formula:

$$R = \rho l / A$$

Step 1: Calculate the initial resistance R_1 and $l = 2 \text{ m}$

$$R_1 = (1.7 \times 10^{-8} \times 2) / (0.5 \times 10^{-6}) = 0.068 \Omega$$

Step 2: Calculate the new resistance R_2 and $l = 4 \text{ m}$ (double length)

$$R_2 = (1.7 \times 10^{-8} \times 4) / (0.5 \times 10^{-6}) = 0.136 \Omega$$

The resistance of the wire when the length is double is 0.136Ω

OR

B.

$$R = \frac{\rho \cdot l}{A}$$

Given:

- Initial length, $l = 2 \text{ m}$
- Cross-sectional area, $A = 0.5 \text{ mm}^2 = 0.5 \times 10^{-6} \text{ m}^2$
- Resistivity of copper, $\rho = 1.7 \times 10^{-8} \Omega \cdot \text{m}$

Step 1: Calculate the initial resistance R_1 and $l = 2 \text{ m}$

$$R_1 = \frac{\rho \cdot l}{A} = \frac{1.7 \times 10^{-8} \Omega \cdot \text{m} \times 2 \text{ m}}{0.5 \times 10^{-6} \text{ m}^2}$$
$$R_1 = \frac{3.4 \times 10^{-8}}{0.5 \times 10^{-6}} \Omega = 0.068 \Omega$$

Step 2: Calculate the new resistance R_2 and $l = 4 \text{ m}$ (double length)

$$R_2 = \frac{\rho \cdot (2l)}{A} = 2 \times R_1 = 2 \times 0.068 \Omega = 0.136 \Omega$$

The resistance of the wire when the length is double is 0.136Ω

Marking-scheme PDF page(s): [8]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-MS.pdf

Question 7 — SQP_2024-25_q25_A

A. $P = VI$ (1)

$$= 230 \times 3.5 = 805 \text{ W}$$

$I \propto 1/R$, so half the resistance means double the current.

Therefore, current in Y = 7.0 A. (1)

25

Student to attempt either A or B.

A. $P = VI$

$$= 230 \times 3.5 = 805 \text{ W}$$

$I \propto \frac{1}{R}$, so half the resistance means double the current.

Therefore, current in Y = 7.0 A.

(1)

(1)

2

Marking-scheme PDF page(s): [3]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-MS.pdf

Question 8 — cbse_sqp_2017-18_electricity_q26_OR

1 Division = $0.5\text{A} / 10$. 17 divisions = $17/20 = 0.85\text{A}$.

OR

An ammeter has 10 divisions between 0 to 0.5A. So,

1 Division = $0.5\text{A} / 10$

17 divisions = $17/20 = 0.85\text{A}$

Question 9 — pyq-2026-e72c8490b3fd0c9755779864

Official answer unavailable/withheld: No independently verified official answer supplied.

Original marking scheme (see limitation above): https://www.cbse.gov.in/cbsenew/marketing-scheme/2026/X/086_SCIENCE.zip

Question 10 — SQP_2026-27_q37_main

A.

1 Ω and 1 Ω are in series and the combination is in parallel with 2 Ω

$$1/R = 1/2 + 1/2 \quad R_{AB} = 1 \Omega$$

$$1/R = 1/3 + 1/3 \quad R = 1.5 \Omega$$

5 Ω , 1 Ω and 1.5 Ω are in series: $R_s = 5 + 1 + 1.5$

$$R_s = 7.5 \Omega$$

$$V = IR$$


$$15 \text{ V} = I \times 7.5$$

$$I = 2 \text{ A (2)}$$


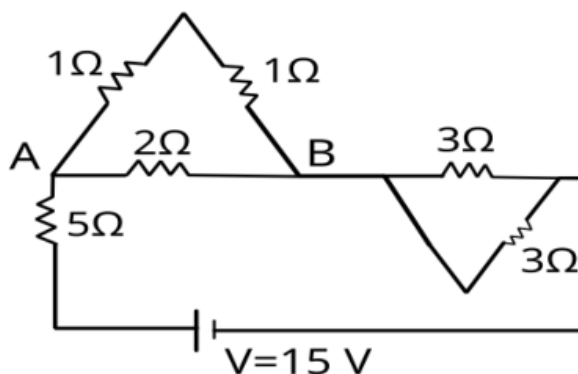
B. $R_{AB} = 1 \Omega$, net current between points A and B is 2 A

$$V_{AB} = I_{AB} \times R_{AB}$$


$$V_{AB} = 2 \times 1 = 2 \text{ V (1)}$$



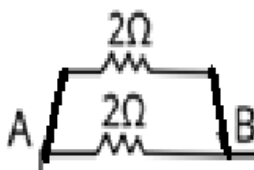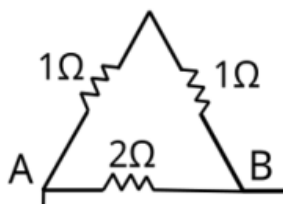1 Ω and 1 Ω are in series and the combination is in parallel with 2 Ω


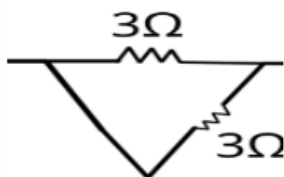
$$\frac{1}{R} = \frac{1}{2} + \frac{1}{2} \quad R_{AB} = 1 \Omega$$



$$\frac{1}{R} = \frac{1}{3} + \frac{1}{3} \quad R = 1.5 \Omega$$

5 Ω , 1 Ω and 1.5 Ω are in series: $R_s = 5 + 1 + 1.5$
 $R_s = 7.5 \Omega$

$$V = I R$$

$$15 \text{ V} = I * 7.5$$

$$I = 2 \text{ A}$$

(2)

B. $R_{AB} = 1 \Omega$, net current between points A and B is 2A

$$V_{AB} = I_{AB} * R_{AB}$$

$$V_{AB} = 2 * 1 = 2 \text{ V}$$

(1)

Marking-scheme PDF page(s): [9]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2026_27/Science-MS.pdf

Question 11 — SQP_2023-24_q32

Official answer unavailable/withheld: Official answer retains erroneous digit 1 in $H=1^2Rt$; correct formula explained in notes.

Original marking scheme (see limitation above): https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-M S.pdf

Question 12 — pyq-2025-3c907fffc20ec05c468bbbea

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 13 — pyq-2023-84af9d4edc02297aecab4a0f

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 14 — SQP_2025-26_q39_VI_A

A.

(i) In household circuits, the fuse is connected in series with all appliances to ensure that it can cut off the entire circuit in case of excessive current, preventing hazards like fires or damage. This way, any overload or short circuit causes the fuse to blow, protecting all appliances.

Appliances are connected in parallel to ensure each receives the same voltage from the mains and can operate independently. This setup allows appliances to work simultaneously and efficiently, with each drawing only the current it needs, without affecting others.

Give Data:

Power of heater, $P_{\text{heater}} = 1500 \text{ W}$

Power of Fan, $P_{\text{fan}} = 500 \text{ W}$

Supply Voltage, $V = 220 \text{ V}$

Fuse rating = 10 A

Step 1: Calculate the Current Drawn by Each Appliance

$I = P/V$

1. Current drawn by the heater: $I_{\text{heater}} = 1500/220 = 6.82 \text{ A}$ (rounded to two decimal places)

2. Current drawn by the fan: $I_{\text{fan}} = P_{\text{fan}}/V = 500 \text{ W}/220 \text{ V}$

$I_{\text{fan}} = 2.27 \text{ A}$ (rounded to two decimal places)

Step 2 : Calculate the total current in the circuit

Since the heater and fan are connected in parallel, the total current I_{total} is the sum of the currents through each appliance:

$I_{\text{total}} = I_{\text{heater}} + I_{\text{fan}} = 6.82 + 2.27 = 9.09 \text{ A}$

Step 3: Compare with the Fuse Rating

The fuse is rated for 10 A , and the total current drawn by the heater and fan together is 9.09 A .

Since $9.09 \text{ A} < 10 \text{ A}$, the fuse will not blow and is appropriate for this circuit, as the total current is within the fuse's capacity.

For visually impaired students

A.

- (i) In household circuits, the fuse is connected in series with all appliances to ensure that it can cut off the entire circuit in case of excessive current, preventing hazards like fires or damage. This way, any overload or short circuit causes the fuse to blow, protecting all appliances.

Appliances are connected in parallel to ensure each receives the same voltage from the mains and can operate independently. This setup allows appliances to work simultaneously and efficiently, with each drawing only the current it needs, without affecting others.

Give Data:

- Power of heater, $P_{\text{heater}} = 1500 \text{ W}$
- Power of Fan, $P_{\text{fan}} = 500 \text{ W}$

- Supply Voltage, $V = 220 \text{ V}$
- Fuse rating = 10 A

Step 1: Calculate the Current Drawn by Each Appliance

Using the formula = $I = \frac{P}{V}$:

1. Current drawn by the heater:

$$I_{\text{heater}} = \frac{P_{\text{heater}}}{V} = \frac{1500 \text{ W}}{220 \text{ V}}$$

$$I_{\text{heater}} = 6.82 \text{ A (rounded to two decimal places)}$$

2. Current drawn by the fan:

$$I_{\text{fan}} = \frac{P_{\text{fan}}}{V} = \frac{500 \text{ W}}{220 \text{ V}}$$

$$I_{\text{fan}} = 2.27 \text{ A (rounded to two decimal places)}$$

Step 2 : Calculate the total current in the circuit

Since the heater and fan are connected in parallel, the total current I_{total} is the sum of the currents through each appliance:

$$I_{\text{total}} = I_{\text{heater}} + I_{\text{fan}}$$

$$I_{\text{total}} = 6.82 \text{ A} + 2.27 \text{ A}$$

$$I_{\text{total}} = 9.09 \text{ A}$$

Step 3: Compare with the Fuse Rating

The fuse is rated for 10 A , and the total current drawn by the heater and fan together is 9.09 A .

Since $9.09 \text{ A} < 10 \text{ A}$, the fuse will not blow and is appropriate for this circuit, as the total current is within the fuse's capacity.

Marking-scheme PDF page(s): [13, 14]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-MS.pdf

Per-question source appendix

Original CBSE questions/images remain attributed to their source. Compilation selection and numbering are editorial. The full Science source PDFs may include unrelated chapters; only selected Electricity crops form this worksheet.

1. SQP-2019-20-Q14

Science-086 Sample Question Paper 2019-20 Class-X | SQP | Year/session: 2019-20 / 2019-20 | Paper code: Not recorded | Source question: 14 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 5, 6

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_SQP.pdf

Also used in: official-03, official-05, official-11, official-13

2. pyq-2024-a415e02467405f8b9fbacfc3

CBSE — Class X Science — 2024 — main — 31/4/1 | PYQ | Year/session: 2024 / main | Paper code: 31/4/1 | Source question: 14 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 7

<https://www.cbse.gov.in/cbsenew/question-paper/2024/X/SCIENCE.zip>

Also used in: official-02, official-06, official-07, official-12, official-15

3. pyq-2023-dc74f0e84e53633b06097022

CBSE — Class X Science — 2023 — compartment | PYQ | Year/session: 2023 / compartment | Paper code: Not recorded | Source question: 15 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 11

<https://www.cbse.gov.in/cbsenew/question-paper/2023-COMPTT/X/Science.zip>

Also used in: official-02, official-03, official-06, official-11, official-14

4. sqp_2022-23_q13

CBSE Class X Science (086) Sample Question Paper 2022-23 | SQP | Year/session: 2022-23 / 2022-23 | Paper code: Not recorded | Source question: 13 | Original section: Section A | Selected marks: 1 | PDF pages (one-based): 4

https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-SQP.pdf

Also used in: official-03, official-05, official-06, official-13, official-15

5. pyq-2018-ac2b7b28762938a4a2df67a3

CBSE — Class X Science — 2018 — 31/1 — main | PYQ | Year/session: 2018 / main | Paper code: 31/1 | Source question: 27 | Original section: Section – B | Selected marks: 2 | PDF pages (one-based): 12

https://www.cbse.gov.in/curric~1/qpms2018/qp_10/Science.zip

Also used in: official-03, official-13, official-15

6. SQP_2025-26_q34_VI_B

CBSE Class X Science (086) Sample Question Paper 2025-26 (English) | SQP | Year/session: 2025-26 / 2025-26 | Paper code: Not recorded | Source question: 34 VI B | Original section: Section – C | Selected marks: 2 | PDF pages (one-based): 12

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-SQP.pdf

Also used in: official-01, official-13

7. SQP_2024-25_q25_A

CBSE Class X Science (086) Sample Question Paper 2024-25 (English) | SQP | Year/session: 2024-25 / 2024-25 | Paper code: Not recorded | Source question: 25 A | Original section: Section-B | Selected marks: 2 | PDF pages (one-based): 6

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-SQP.pdf

Also used in: official-04, official-14

8. cbse_sqp_2017-18_electricity_q26_OR

Sample Question Paper 2017-18 — Science — Class - X | SQP | Year/session: 2017-18 / 2017-18 | Paper code: Not recorded | Source question: 26 OR | Original section: SECTION - B | Selected marks: 2 | PDF pages (one-based): 4

https://cbseacademic.nic.in/web_material/SQP/CLASS_X_2017_18/Science_SQP.pdf

Also used in: official-01, official-13

9. pyq-2026-e72c8490b3fd0c9755779864

CBSE Class X Science 2026 First Board 31-3-2 | PYQ | Year/session: 2026 / 2026 First Board | Paper code: 31/3/2 | Source question: 36 | Original section: Section C (Physics) | Selected marks: 3 | PDF pages (one-based): 27

<https://www.cbse.gov.in/cbsenew/question-paper/2026/X/Science.zip>

No cross-paper reuse.

10. SQP_2026-27_q37_main

CBSE Class X Science (086) Sample Question Paper 2026-27 (English) | SQP | Year/session: 2026-27 / 2026-27 | Paper code: Not recorded | Source question: 37 main | Original section: Section - C | Selected marks: 3 | PDF pages (one-based): 13

https://cbseacademic.nic.in/web_material/SQP/ClassX_2026_27/Science-SQP.pdf

Also used in: official-13

11. SQP_2023-24_q32

CBSE Class X Science (086) Sample Question Paper 2023-24 (English) | SQP | Year/session: 2023-24 / 2023-24 | Paper code: Not recorded | Source question: 32 | Original section: Section-C | Selected marks: 3 | PDF pages (one-based): 5

https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-SQP.pdf

Also used in: official-04, official-13

12. pyq-2025-3c907fffc20ec05c468bbbea

CBSE — Class X Science — 2025 — main — 31/3/1 | PYQ | Year/session: 2025 / main | Paper code: 31/3/1 | Source question: 39 | Original section: SECTION E | Selected marks: 4 | PDF pages (one-based): 25, 27

https://www.cbse.gov.in/cbsenew/question-paper/2025/X/086_Science.zip

Also used in: official-06, official-14

13. pyq-2023-84af9d4edc02297aecab4a0f

CBSE — Class X Science — 2023 — main — 31/5/2 | PYQ | Year/session: 2023 / main | Paper code: 31/5/2 | Source question: 34 | Original section: SECTION D | Selected marks: 5 | PDF pages (one-based): 19

<https://www.cbse.gov.in/cbsenew/question-paper/2023/X/SCIENCE.zip>

Also used in: official-01, official-05, official-10, official-13

14. SQP_2025-26_q39_VI_A

CBSE Class X Science (086) Sample Question Paper 2025-26 (English) | SQP | Year/session: 2025-26 / 2025-26 | Paper code: Not recorded | Source question: 39 VI A | Original section: Section - C | Selected marks: 5 | PDF pages (one-based): 15

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-SQP.pdf

No cross-paper reuse.