

Official-source Electricity compilation 10

Mixed-source chapter worksheet • cross-paper reuse disclosed

Total: 35 marks • Suggested time: 70 minutes

Instructions and reuse disclosure

Curated compilation of official CBSE source questions, not a CBSE-issued chapter paper. Original source labels and exact source images are retained.

Answer every selected question. Only one selected source-slot alternative appears in this paper; do not answer or count excluded alternatives.

Questions recur across this 15-paper collection. Reuse is disclosed per question in the source appendix; these are not 15 disjoint official papers.

Sections use available source marks: A MCQ; B 2 marks; C 3 marks; D 5 marks or source-marked case questions. Case marks are not inflated to five.

Section A — MCQ

Compilation questions 1-4; 4 marks. Exact source labels remain attached to each question.

Section B — 2-mark questions

Compilation questions 5-8; 8 marks. Exact source labels remain attached to each question.

Section C — 3-mark questions

Compilation questions 9-11; 9 marks. Exact source labels remain attached to each question.

Section D — 5-mark / case-based questions

Compilation questions 12-14; 14 marks. Exact source labels remain attached to each question.

Section A — MCQ

1. [1 marks] Source Q30 • 2026 First Board

- 30.** The correct way to connect an ammeter and a voltmeter in an electric circuit is : 1
- (A) Ammeter in parallel and voltmeter in series
 - (B) Ammeter and voltmeter both in parallel
 - (C) Ammeter in series and voltmeter in parallel
 - (D) Ammeter and voltmeter both in series

Source/editorial note: Visually confirmed complete replacement crop: question number, wording, all options/table values, mathematical symbols and printed marks. Whitespace normalized; mathematical glyphs represented in Unicode and stacked fractions as $\frac{1}{4}$ and $\frac{V}{4}$. Page/QR/footer debris removed from text; marks retained in marks field. No supplied diagram; table retained in text and evidence. Answers not reviewed. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

2. [1 marks] Source Q19 • main

19. *Assertion (A)* : Nichrome is an alloy which is commonly used in electrical heating devices such as electric irons, toasters, etc.

Reason (R) : The resistivity of nichrome is high and its resistance decreases with increase in temperature.

For Questions number 17 to 20, two statements are given — one labelled as Assertion (A) and the other labelled as Reason (R). Select the correct answer to these questions from the codes (A), (B), (C) and (D) as given below.

- (A) Both Assertion (A) and Reason (R) are true and Reason (R) is the correct explanation of Assertion (A).
- (B) Both Assertion (A) and Reason (R) are true, but Reason (R) is **not** the correct explanation of Assertion (A).
- (C) Assertion (A) is true, but Reason (R) is false.
- (D) Assertion (A) is false, but Reason (R) is true.

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.


3. [1 marks] Source Q6 • 2019-20


6 When a 4V battery is connected across an unknown resistor there is a current of 100 mA in the circuit. The value of the resistance of the resistor is:

- i) $4\ \Omega$
- ii) $40\ \Omega$
- iii) $400\ \Omega$
- iv) $0.4\ \Omega$

Source/editorial note: Original spelling “resister” retained. Q6 mark is printed on the preceding page (page 3); Section A instructions and the MS both confirm 1 mark.

4. [1 marks] Source Q15 • 2022-23

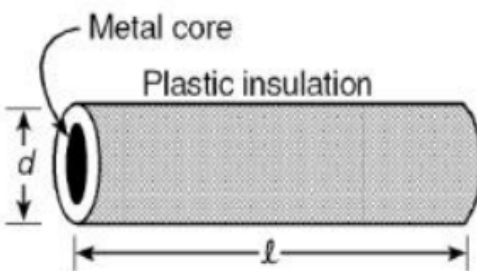15	 Plastic insulation surrounds a wire having diameter d and length l as shown above. A decrease in the resistance of the wire would be produced by an increase in the (a) length l of the wire (b) diameter d of the wire (c) temperature of the wire (d) thickness of the plastic insulation	1
----	--	---

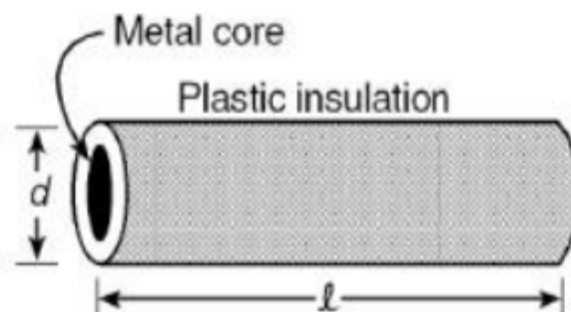

Section B — 2-mark questions

5. [2 marks] Source Q26 • 2017-18

26	The values of current I flowing in a given resistor for the corresponding values of potential difference V across the resistor are given below: <table border="1" style="width: 100%; border-collapse: collapse; margin-top: 10px;"> <tr> <td style="padding: 5px;">I (ampere)</td> <td style="padding: 5px;">0.5</td> <td style="padding: 5px;">1.0</td> <td style="padding: 5px;">2.0</td> <td style="padding: 5px;">3.0</td> <td style="padding: 5px;">4.0</td> </tr> <tr> <td style="padding: 5px;">V (volt)</td> <td style="padding: 5px;">1.6</td> <td style="padding: 5px;">3.4</td> <td style="padding: 5px;">6.7</td> <td style="padding: 5px;">10.2</td> <td style="padding: 5px;">13.2</td> </tr> </table>	I (ampere)	0.5	1.0	2.0	3.0	4.0	V (volt)	1.6	3.4	6.7	10.2	13.2	2
I (ampere)	0.5	1.0	2.0	3.0	4.0									
V (volt)	1.6	3.4	6.7	10.2	13.2									


Plot a graph between V and I and calculate the resistance of the resistor.

Source/editorial note: Practical-skills question; continues from SQP page 3 to page 4. OR alternative stored separately. Official MS states 3.2Ω and does not supply the plotted graph; data ratios are approximate (about 3.2 – 3.4Ω). The official worked slope uses graph coordinates not listed in the table; preserved rather than silently corrected. Official answer unavailable/withheld for an identified error, omission or incomplete verification: Official slope solution captured, but required plotted graph absent from official MS; not a complete publishable model answer. Consult the linked original marking scheme with this limitation in mind.

6. [2 marks] Source Q26 • 2018-19

26. The current flowing through a resistor connected in an electrical circuit and the potential difference developed across its ends are shown in the given ammeter and voltmeter. Find the least count of the voltmeter and ammeter. What is the voltage and the current across the given resistor?


2

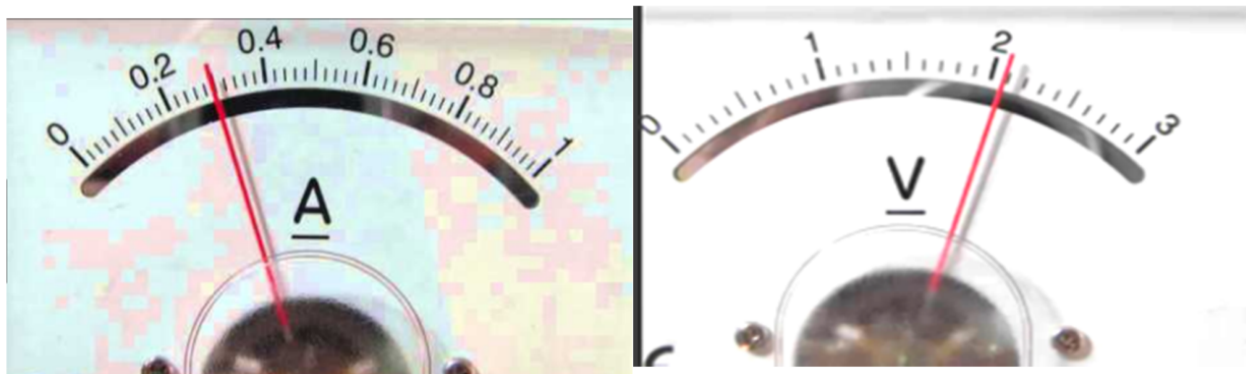

Source/editorial note: Practical-skills question. Official SQP layout error: the ammeter/voltmeter image appears beside chemistry Q22 near the top of the SAME PDF page 5, not alongside Q26. The matching meters and MS establish the intended association. Evidence array puts Q26 text first and displaced diagram second. No image was redrawn.

7. [2 marks] Source Q25 B • 2024-25

B.

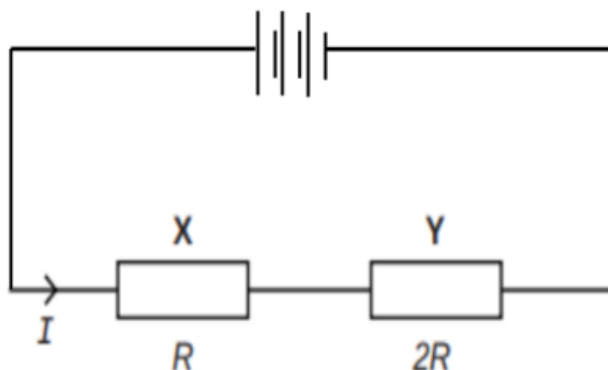


The above figure shows two resistors X and Y connected in series to a battery. The power dissipated for this combination is P_1 . When these resistors

are connected in parallel to the same battery then the power dissipated is given by P_2 . Find out the ratio $\frac{P_1}{P_2}$.


Source/editorial note: Diagram supplies $X = R$ and $Y = 2R$; continuation on next page retained. Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

26

2

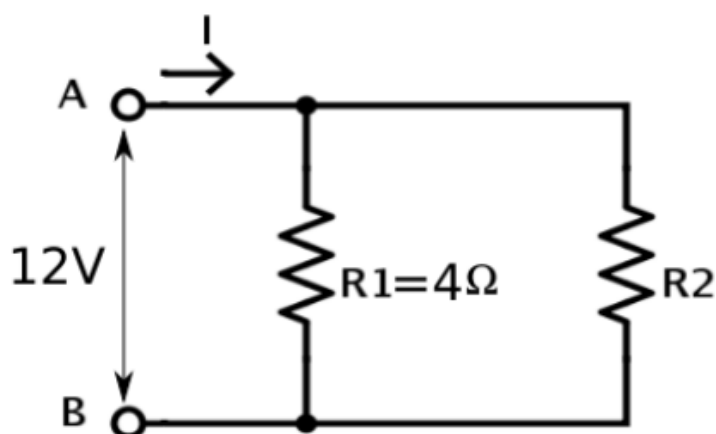

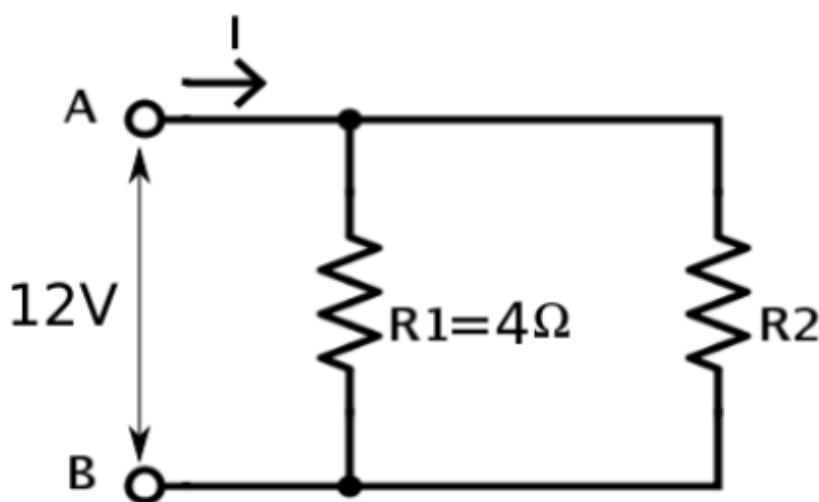A student has two resistors- 2Ω and 3Ω . She has to put one of them in place of R_2 as shown in the circuit. The current that she needs in the entire circuit is exactly 9A. Show by calculation which of the two resistors she should choose.



Section C — 3-mark questions

9. [3 marks] Source Q13 • main


- List the factors on which the resistance of a conductor in the shape of a wire depends.
- Why are metals good conductors of electricity whereas glass is a bad conductor of electricity? Give reason.
- Why are alloys commonly used in electrical heating devices? Give reason.

Source/editorial note: Occurrence mappings retained verbatim; only primary PDF/question evidence is accepted and counted. Other occurrences require their own evidence validation. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

10. [3 marks] Source Q11 • main

11. (a) Three resistors R_1 , R_2 and R_3 are connected in parallel and the combination is connected to a battery, an ammeter, a voltmeter and a key. Draw suitable circuit diagram to show the arrangement of these circuit components along with the direction of current flowing.

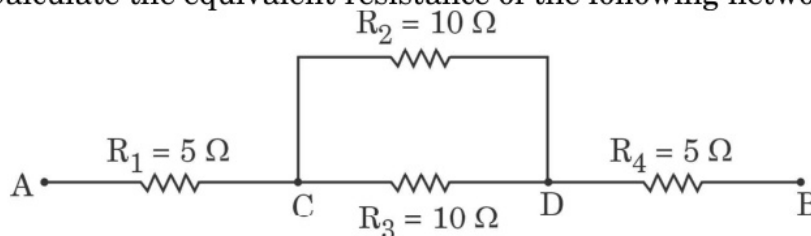- (b) Calculate the equivalent resistance of the following network : 3



Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

11. [3 marks] Source Q36 • 2025-26

36	A student needs to make a 0.12Ω resistor. She has some copper wire of 0.80 mm diameter. Resistivity of copper is $1.8 \times 10^{-8} \Omega \text{m}$ (i) Determine the cross-sectional area of the wire. (ii) Calculate the length of wire required for the 0.12Ω resistor.	3
----	--	---

Source/editorial note: Official scheme rounds area to $5 \times 10^{-7} \text{ m}^2$ before calculating 3.33 m . Original “are” typo retained. No subpart marks printed. Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

Section D — 5-mark / case-based questions

12. [5 marks] Source Q34 • main

SECTION D

34. There are three resistors of 10Ω , 20Ω and 30Ω joined in parallel in a circuit. The potential difference across the electric circuit is 10 V .

- (a) Draw a circuit diagram for the above case.
(b) Find the total resistance of the combination of resistors.
(c) Calculate the electric current drawn from the same source.

5

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

13. [4 marks] Source Q39 iii • 2023-24


39	The diagram shows a 12V battery on the left. The positive terminal is at the top. A wire goes from the positive terminal to a switch labeled 'A'. The switch has three positions: 1 (top), 2 (middle), and 3 (bottom). Position 1 is currently selected. A wire from position 2 goes to the junction between the two 4.0 Ω lamps. A wire from position 3 goes to the junction between the two 12 Ω lamps. The negative terminal of the battery is connected to the bottom of all four lamps. Vinita and Ahmed demonstrated a circuit that operates the two headlights and the two sidelights of a car, in their school exhibition. Based on their demonstrated circuit, answer the following questions. - State what happens when switch A is connected to - Position 2 - Position 3 - Find the potential difference across each lamp when lit. - Calculate the current - in each $12\ \Omega$ lamp when lit. - In each $4\ \Omega$ lamp when lit.	1+1+2
----	---	-------

Source/editorial note: Includes common (i), (ii) and main (iii); 1+1+2 marks. Original scheme mislabels second line of (i) as (a). Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

14. [5 marks] Source Q39 B • 2025-26

B.

OR

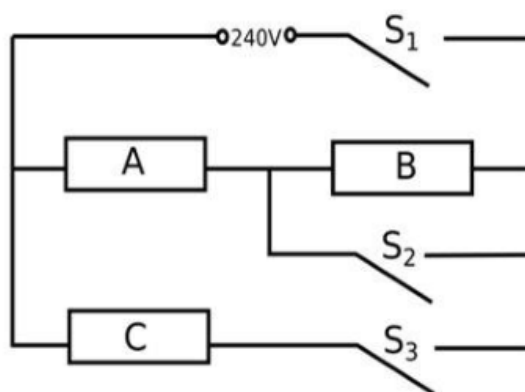

An electric heater consists of three similar heating elements A, B and C, connected as shown in the figure above. Each heating element is rated as 1.2 kW, 240 V and has constant resistance. S_1 , S_2 and S_3 are respective switches.

The circuit is connected to a 240 V supply.

- (i) Calculate the resistance of one heating element.
- (ii) Calculate the current in each resistor when only S_1 and S_3 are closed.
- (iii) Calculate the power dissipated across A when S_1 , S_2 and S_3 are closed.

Source/editorial note: Total 5 marks; MS provides no subpart allocation. Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

Solutions and verification status

Only explicitly verified solutions are printed. A missing solution is not a claim that the question is unsolvable.

Question 1 — pyq-2026-8f6db37837565412c602b458

Official answer unavailable/withheld: No independently verified official answer supplied.

Original marking scheme (see limitation above): https://www.cbse.gov.in/cbsenew/marketing-scheme/2026/X/086_SCIENCE.zip

Question 2 — pyq-2025-1aee07c91b9869601a83c309

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 3 — cbse_sqp_2019-20_electricity_q6

ii) $40\ \Omega$. $V = IR$; $V = 4\text{ V}$; $I = 100\text{ mA} = 0.1\text{ A}$. $R = V/I = 4/0.1\ \Omega = 40\ \Omega$.

6	ii) $= 40\ \Omega$. $V=IR$, $V = 4\text{ V}$, $I = 100\text{ mA} = 0.1\text{ A}$ Hence $R = V/I = 4/0.1\ \Omega = 40\ \Omega$.	1 mark
---	--	--------

Marking-scheme PDF page(s): [1]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_MS.pdf

Question 4 — sqp_2022-23_q15

(b) diameter d of the wire

15.	(b) diameter d of the wire	1
-----	------------------------------	---

Marking-scheme PDF page(s): [1]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-MS.pdf

Question 5 — cbse_sqp_2017-18_electricity_q26

Official answer unavailable/withheld: Official slope solution captured, but required plotted graph absent from official MS; not a complete publishable model answer.

Original marking scheme (see limitation above): https://cbseacademic.nic.in/web_material/SQP/CLASS_X_2017_18/Science_MS.pdf

Question 6 — cbse_sqp_2018-19_electricity_q26

LC of ammeter $= 0.2/10\text{ A} = 0.02\text{ A}$. LC of Voltmeter $= 1/10 = 0.1\text{ V}$. Current $= 15 \times 0.02\text{ A} = 0.3\text{ A}$. Potential difference $= 21 \times 0.1\text{ V} = 2.1\text{ V}$.

26. LC of ammeter $= \frac{0.2}{10}\text{ A} = 0.02\text{ A}$ LC of Voltmeter $= \frac{1}{10} = 0.1\text{ V}$ Current $= 15 \times 0.02\text{ A} = 0.3\text{ A}$ Potential difference $= 21 \times 0.1\text{ V} = 2.1\text{ V}$	2
--	---

Marking-scheme PDF page(s): [7]

https://cbseacademic.nic.in/web_material/SQP/CLASS_X_2018_19/X_Science_MS_2018-19.pdf

Question 7 — SQP_2024-25_q25_B

B. For series total resistance is $R+2R = 3R$ (0.5)

$$P_1 = V^2/(3R). \text{ (0.5)}$$

For parallel total Resistance is $2R/3$. (0.5)

$$P_2 = V^2/(2R/3) = 3V^2/(2R).$$

$$P_1/P_2 = 2/9. \text{ (0.5)}$$

	B. For series total resistance is $R+2R = 3R$	(0.5)
	$P_1 = \frac{V^2}{3R}.$	(0.5)
	For parallel total Resistance is $\frac{2R}{3}.$	(0.5)
	$P_2 = \frac{V^2}{2R/3} = \frac{3V^2}{2R}.$	
	$\frac{P_1}{P_2} = \frac{2}{9}.$	(0.5)

Marking-scheme PDF page(s): [3]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-MS.pdf

Question 8 — sqp_2020-21_q26

The overall current needed = 9 A and the voltage is 12 V. By Ohm's law, $R = 12/9 = 4/3 \Omega$. R_1 and R_2 are in parallel, so $R = R_1 R_2 / (R_1 + R_2) = 4R_2 / (4 + R_2) = 4/3$. Hence $R_2 = 2 \Omega$.

26	The overall current needed = 9A. The voltage is 12V Hence by Ohm's Law $V=IR$, The resistance for the entire circuit = $12/9 = 4/3 \Omega$. = R R_1 and R_2 are in parallel. Hence, $R=(R_1 R_2)/(R_1 + R_2) = 4R_2/(4+R_2) = 4/3$ $R_2 = 2\Omega$	2
----	--	---

Marking-scheme PDF page(s): [4]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2020_21/Science-MS.pdf

Question 9 — pyq-2018-910a1f81e814c508e7ea459d

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 10 — pyq-2022-9fe4ca3895577ede74461fc1

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 11 — SQP_2025-26_q36

(i) Show that the cross-sectional area of the wire is about $5 \times 10^{-7} \text{ m}^2$.

The cross-sectional area A of a wire with diameter d is given by:

$$A = \pi d^2/4$$

Substitute, $d = 0.80 \times 10^{-3} \text{ m}$:

$$A = \pi(0.80 \times 10^{-3})^2/4$$

$$A = \pi(0.64 \times 10^{-6})/4$$

$$A = (2.01 \times 10^{-6})/4 \approx 5 \times 10^{-7} \text{ m}^2$$

Thus, the cross-sectional area A is approximately $5 \times 10^{-7} \text{ m}^2$.

(ii) To find the length l of the wire, we can use the formula of resistance:

$$R = \rho l/A$$

Rearrange to solve for l :

$$l = RA/\rho$$

Substitute the values:

$$l = (0.12 \times 5 \times 10^{-7})/(1.8 \times 10^{-8})$$

$$l = (6 \times 10^{-8})/(1.8 \times 10^{-8})$$

$$l = 6/1.8 \approx 3.33 \text{ m}$$

The student needs a length of approximately 3.33 m of given copper wire to make a 0.12Ω resistor.

36	(i) Show that the cross-sectional area of the wire is about $5 \times 10^{-7} \text{ m}^2$. The cross-sectional area A of a wire with diameter d is given by: $A = \pi \left(\frac{d}{2} \right)^2$ Substitute, $d = 0.80 \times 10^{-3} \text{ m}$: $A = \pi \left(\frac{0.80 \times 10^{-3}}{2} \right)^2$ $A = \pi (0.40 \times 10^{-3})^2$ $A = \pi \times (0.16 \times 10^{-6}) \text{ m}^2$ $A \approx 3.14 \times 0.16 \times 10^{-6} \text{ m}^2$ $A \approx 5.024 \times 10^{-7} \text{ m}^2$ Thus, the cross-sectional area A is approximately $5 \times 10^{-7} \text{ m}^2$. (ii) To find the length l of the wire, we can use the formula of resistance: $R = \frac{\rho \cdot l}{A}$ Rearrange to solve for l : $l = \frac{R \cdot A}{\rho}$ Substitute the values: $l = \frac{0.12 \cdot 5 \times 10^{-7}}{1.8 \times 10^{-8}}$ $l = \frac{6 \times 10^{-8}}{1.8 \times 10^{-8}}$ $l = \frac{6}{1.8} \text{ m}$ $l = 3.33 \text{ m}$ The student needs a length of approximately 3.33 m of given copper wire to make a 0.12Ω resistor.	3
----	---	---

Marking-scheme PDF page(s): [9]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-MS.pdf

Question 12 — pyq-2023-84af9d4edc02297aecab4a0f

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 13 — SQP_2023-24_q39_iii

(i) 12 Ω lamps (only) on.

(a) 4 Ω lamps (only) on [0.5+0.5]

(ii) 12 V for both sets of lamps and all of them are in parallel. [1]

(iii) 12 Ω lamps are on when the wire is connected to position 2. Voltage across both 12 Ω lamps = 12 V. $V=IR$ (Ohm's law). $I = V/R = 12/12 = 1\text{A}$. [1]

4 Ω lamps are on when the wire is connected to position 3. Voltage across both 4 Ω lamps = 12 V. $V=IR$ (Ohm's law). $I = V/R = 12/4 = 3\text{A}$. [1]

39	(i) 12 Ω lamps (only) on. (a) 4 Ω lamps (only) on [0.5+0.5] (ii) 12 V for both sets of lamps and all of them are in parallel. [1] (iii) 12 Ω lamps are on when the wire is connected to position 2. Voltage across both 12 Ω lamps = 12 V. $V=IR$ (Ohm's law). $I = \frac{V}{R} = \frac{12}{12} = 1A.$ [1] 4 Ω lamps are on when the wire is connected to position 3. Voltage across both 4 Ω lamps = 12 V. $V=IR$ (Ohm's law). $I = \frac{V}{R} = \frac{12}{4} = 3A.$ [1]	4
----	---	---

Marking-scheme PDF page(s): [6]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-MS.pdf

Question 14 — SQP_2025-26_q39_B

B.

(i) $P = V^2/R$

$\therefore R = V^2/P = (240 \times 240)/1200 = 48 \Omega$

(ii) For S_1 and S_3 closed

– Current in C

$V = IR$ (Ohm's Law)

$\therefore I = V/R = 240 \text{ V}/48 \Omega = 5 \text{ A}$

– Current in A and B

$V = IR$ (Ohm's Law)

$\therefore I = V/R = 240 \text{ V}/96 \Omega = 2.5 \text{ A}$

(iii) Power across A for S_1, S_2, S_3 closed

$P_A = I^2 R = 5^2 \times 48 = 1200 \text{ W} = 1.2 \text{ KW}$

B. (i) $P = \frac{V^2}{R}$ $\therefore R = \frac{V^2}{P} = \frac{240 \times 240}{1200} = 48 \Omega$ (ii) For S_1 and S_3 closed – Current in C $V = IR$ (Ohm's Law) $\therefore I = \frac{V}{R} = \frac{240 \text{ V}}{48 \Omega} = 5 \text{ A}$ – Current in A and B $V = IR$ (Ohm's Law) $\therefore I = \frac{V}{R} = \frac{240 \text{ V}}{96 \Omega} = 2.5 \text{ A}$ (iii) Power across A for S_1, S_2, S_3 closed $P_A = I^2 R = 5^2 \times 48 = 1200 \text{ W} = 1.2 \text{ KW}$	
---	--

Marking-scheme PDF page(s): [13]

Per-question source appendix

Original CBSE questions/images remain attributed to their source. Compilation selection and numbering are editorial. The full Science source PDFs may include unrelated chapters; only selected Electricity crops form this worksheet.

1. pyq-2026-8f6db37837565412c602b458

CBSE Class X Science 2026 First Board 31-3-1 | PYQ | Year/session: 2026 / 2026 First Board | Paper code: 31/3/1 | Source question: 30 | Original section: Section C (Physics) | Selected marks: 1 | PDF pages (one-based): 23

<https://www.cbse.gov.in/cbsenew/question-paper/2026/X/Science.zip>

Also used in: official-07

2. pyq-2025-1aee07c91b9869601a83c309

CBSE — Class X Science — 2025 — main — 31/2/1 | PYQ | Year/session: 2025 / main | Paper code: 31/2/1 | Source question: 19 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 13, 11

https://www.cbse.gov.in/cbsenew/question-paper/2025/X/086_Science.zip

Also used in: official-01, official-07

3. cbse_sqp_2019-20_electricity_q6

Class-X Science-086 SAMPLE QUESTION PAPER 2019-20 | SQP | Year/session: 2019-20 / 2019-20 | Paper code: Not recorded | Source question: 6 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 4

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_SQP.pdf

Also used in: official-01, official-06, official-07, official-15

4. sqp_2022-23_q15

CBSE Class X Science (086) Sample Question Paper 2022-23 | SQP | Year/session: 2022-23 / 2022-23 | Paper code: Not recorded | Source question: 15 | Original section: Section A | Selected marks: 1 | PDF pages (one-based): 5

https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-SQP.pdf

Also used in: official-02, official-04, official-08, official-12, official-14

5. cbse_sqp_2017-18_electricity_q26

Sample Question Paper 2017-18 — Science — Class - X | SQP | Year/session: 2017-18 / 2017-18 | Paper code: Not recorded | Source question: 26 | Original section: SECTION - B | Selected marks: 2 | PDF pages (one-based): 3, 4

https://cbseacademic.nic.in/web_material/SQP/CLASS_X_2017_18/Science_SQP.pdf

Also used in: official-04, official-15

6. cbse_sqp_2018-19_electricity_q26

Class-X Science-086 SAMPLE QUESTION PAPER-19 | SQP | Year/session: 2018-19 / 2018-19 | Paper code: Not recorded | Source question: 26 | Original section: SECTION E | Selected marks: 2 | PDF pages (one-based): 5

https://cbseacademic.nic.in/web_material/SQP/CLASS_X_2018_19/X_Science_SQP_2018-19.pdf

Also used in: official-02, official-15

7. SQP_2024-25_q25_B

CBSE Class X Science (086) Sample Question Paper 2024-25 (English) | SQP | Year/session: 2024-25 / 2024-25 | Paper code: Not recorded | Source question: 25 B | Original section: Section-B | Selected marks: 2 | PDF pages (one-based): 6, 7

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-SQP.pdf

Also used in: official-01, official-13

8. sqp_2020-21_q26

CBSE Class X Science (086) Sample Question Paper 2020-21 | SQP | Year/session: 2020-21 / 2020-21 | Paper code: Not recorded | Source question: 26 | Original section: Section B | Selected marks: 2 | PDF pages (one-based): 12

https://cbseacademic.nic.in/web_material/SQP/ClassX_2020_21/Science-SQP.pdf

Also used in: official-01

9. pyq-2018-910a1f81e814c508e7ea459d

CBSE — Class X Science — 2018 — 31/1 — main | PYQ | Year/session: 2018 / main | Paper code: 31/1 | Source question: 13 | Original section: Section – A | Selected marks: 3 | PDF pages (one-based): 6

https://www.cbse.gov.in/curric~1/qpms2018/qp_10/Science.zip

Also used in: official-01, official-06

10. pyq-2022-9fe4ca3895577ede74461fc1

CBSE — Class X Science — 2022 — main — 31/1/1 | PYQ | Year/session: 2022 / main | Paper code: 31/1/1 | Source question: 11 | Original section: SECTION B | Selected marks: 3 | PDF pages (one-based): 7

<https://www.cbse.gov.in/cbsenew/question-paper/2022/X/Scince.zip>

Also used in: official-04, official-07

11. SQP_2025-26_q36

CBSE Class X Science (086) Sample Question Paper 2025-26 (English) | SQP | Year/session: 2025-26 / 2025-26 | Paper code: Not recorded | Source question: 36 | Original section: Section – C | Selected marks: 3 | PDF pages (one-based): 13

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-SQP.pdf

Also used in: official-14

12. pyq-2023-84af9d4edc02297aecab4a0f

CBSE — Class X Science — 2023 — main — 31/5/2 | PYQ | Year/session: 2023 / main | Paper code: 31/5/2 | Source question: 34 | Original section: SECTION D | Selected marks: 5 | PDF pages (one-based): 19

<https://www.cbse.gov.in/cbsenew/question-paper/2023/X/SCIENCE.zip>

Also used in: official-01, official-05, official-09, official-13

13. SQP_2023-24_q39_iii

CBSE Class X Science (086) Sample Question Paper 2023-24 (English) | SQP | Year/session: 2023-24 / 2023-24 | Paper code: Not recorded | Source question: 39 iii | Original section: Section-E | Selected marks: 4 | PDF pages (one-based): 8

https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-SQP.pdf

Also used in: official-02, official-07, official-14

14. SQP_2025-26_q39_B

CBSE Class X Science (086) Sample Question Paper 2025-26 (English) | SQP | Year/session: 2025-26 / 2025-26 | Paper code: Not recorded | Source question: 39 B | Original section: Section – C | Selected marks: 5 | PDF pages (one-based): 15

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-SQP.pdf

No cross-paper reuse.