

# Official-source Electricity compilation 11

Mixed-source chapter worksheet • cross-paper reuse disclosed

Total: 33 marks • Suggested time: 66 minutes

## Instructions and reuse disclosure

Curated compilation of official CBSE source questions, not a CBSE-issued chapter paper. Original source labels and exact source images are retained.

Answer every selected question. Only one selected source-slot alternative appears in this paper; do not answer or count excluded alternatives.

Questions recur across this 15-paper collection. Reuse is disclosed per question in the source appendix; these are not 15 disjoint official papers.

Sections use available source marks: A MCQ; B 2 marks; C 3 marks; D 5 marks or source-marked case questions. Case marks are not inflated to five.

## Section A — MCQ

Compilation questions 1-4; 4 marks. Exact source labels remain attached to each question.

## Section B — 2-mark questions

Compilation questions 5-8; 8 marks. Exact source labels remain attached to each question.

## Section C — 3-mark questions

Compilation questions 9-12; 12 marks. Exact source labels remain attached to each question.

## Section D — 5-mark / case-based questions

Compilation questions 13-14; 9 marks. Exact source labels remain attached to each question.

## Section A — MCQ

1. [1 marks] Source Q30 • 2026 First Board

**30.** Work done in displacing an electron between two points having potential difference of 1 V, is : 1

- |                                      |                                      |
|--------------------------------------|--------------------------------------|
| (A) $-1.6 \times 10^{-19} \text{ C}$ | (B) $-1.6 \times 10^{-19} \text{ J}$ |
| (C) $+1.6 \times 10^{-19} \text{ J}$ | (D) $-1.6 \times 10^{-19} \text{ V}$ |

Source/editorial note: Visually confirmed complete replacement crop: question number, wording, all options/table values, mathematical symbols and printed marks. Whitespace normalized; mathematical glyphs represented in Unicode and stacked fractions as  $\frac{1}{4}$  and  $\frac{V}{4}$ . Page/QR/footer debris removed from text; marks retained in marks field. No supplied diagram; table retained in text and evidence. Answers not reviewed. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

## 2. [1 marks] Source Q14 • 2019-20

14      **Assertion:** A fuse wire is always connected in parallel with the mainline.      1

**Reason:** If a current larger than the specified value flows through the circuit, fuse wire melts.

**For question numbers 13 and 14, two statements are given- one labeled *Assertion* (A) and the other labeled *Reason* (R). Select the correct answer to these questions from the codes (i), (ii), (iii) and (iv) as given below**

- i) Both A and R are true and R is correct explanation of the assertion.
- ii) Both A and R are true but R is not the correct explanation of the assertion.
- iii) A is true but R is false.
- iv) A is false but R is true.

13      **Assertion:** Following are the structural isomers of butane.      1

Source/editorial note: Fuse series placement and melting from excess current are explicitly NCERT Electricity section 11.7.1 (printed p190, PDF p20). Included after independent audit overturned the batch reviewer's domestic-circuit exclusion. Shared assertion-reason choices occur on preceding PDF page 5.

## 3. [1 marks] Source Q31 • 2026-27

|    |                                                                                                                                       |   |
|----|---------------------------------------------------------------------------------------------------------------------------------------|---|
| 31 | An electrical appliance rated 1000 W is operated at 250 V. What current does it draw?<br>A. 0.25 A<br>B. 2.5 A<br>C. 4.0 A<br>D. 10 A | 1 |
|----|---------------------------------------------------------------------------------------------------------------------------------------|---|

Source/editorial note: Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

## 4. [1 marks] Source Q15 • compartment

**15.** The resistance of a wire does ***not*** depend on its :

- (a) Length
- (b) Area of cross-section
- (c) Shape
- (d) Material


Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

## Section B — 2-mark questions

5. [2 marks] Source Q25 • main

- 25.**  $V - I$  graph for two conducting wires A and B are as shown. If both wires are of the same length and same diameter, which of the two is made of a material of high resistivity? Give reasons to justify your answer.

2

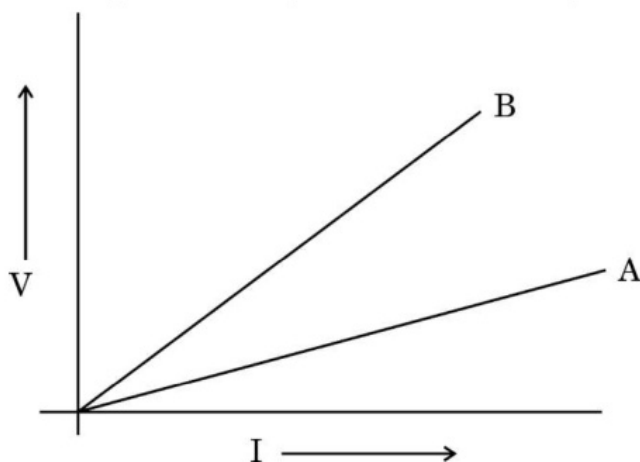

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

6. [2 marks] Source Q26 • main

- 26.** Two wires A and B of same material, having same lengths and diameters 0.2 mm and 0.3 mm respectively, are connected one by one in a circuit. Which one of these two wires will offer more resistance to the flow of current in the circuit? Justify your answer.

2

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

7. [2 marks] Source Q26 • main

- 26.** An electric kettle is rated 230 V; 1000 W. Calculate the resistance of its heating element when in operation.

2

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

8. [2 marks] Source Q34 VI A • 2025-26

For visually impaired students

- A. You are given four resistors each having resistance of  $R$  ohm. Find the maximum and minimum resistance that can be made with these four resistors.

Source/editorial note: Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

## Section C — 3-mark questions

### 9. [3 marks] Source Q11 • 2021-22

|    |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                |   |
|----|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|
| 11 | <p>a. It would cost a man Rs. 3.50 to buy 1.0 kW h of electrical energy from the Main Electricity Board. His generator has a maximum power of 2.0 kW. The generator produces energy at this maximum power for 3 hours. Calculate how much it would cost to buy the same amount of energy from the Main Electricity Board.(1 Mark)</p> <p>b. A student boils water in an electric kettle for 20 minutes. Using the same mains supply he wants to reduce the boiling time of water. To do so should he increase or decrease the length of the heating element? Justify your answer.(2 Marks)</p> | 3 |
|----|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|

Source/editorial note: Both compulsory subparts retained in one three-mark record. MS answer spans pp.3–4.

### 10. [3 marks] Source Q32 • 2024-25

|    |                                                                                                                                                                                                                                                                                       |   |
|----|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|
| 32 | <p>A. State the relationship between the resistance <math>R</math> of a wire to its length <math>l</math> and cross sectional area <math>A</math>. Use the mathematical symbols to arrive at the final formula.</p> <p>B. Using the formula define the resistivity of a material.</p> | 3 |
|----|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|

Source/editorial note: The intermediate MS proportionality is printed  $R \propto l/A$ ; retained rather than silently changing it to  $R \propto 1/A$ . Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

### 11. [3 marks] Source Q31 • compartment

- 31.** (a) Write mathematical expression for Joule's law of heating.
- (b) Calculate the amount of heat generated while transferring 72000 coulomb of charge in two hours through a potential difference of 220 V. 1+2

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

12. [3 marks] Source Q35 • 2026 First Board



- 35.** (a) Name a device which is used to :
- (i) Maintain a constant potential difference in a circuit.
  - (ii) Change the electric current in an electric circuit.
- (b) When the potential difference between the terminals of an electric heater is 110 V, a current of 5 A flows through it. What will be the value of current flowing through it when the potential difference is increased to 220 V ?


3

Source/editorial note: Question text, numbering, printed marks, subparts/internal choices, diagram labels and complete crop boundaries visually checked against saved original-PDF replacement crops, using JPEG quality 80 and maximum dimension 900 px. Whitespace normalized; original wording retained. No MCQ options in this question. Page furniture is not question text. Answer and marking scheme not verified. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

## Section D — 5-mark / case-based questions

13. [5 marks] Source Q36 • 2022-23

|    |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                       |   |
|----|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|
| 36 | <div data-bbox="491 297 1018 701" data-label="Diagram"> </div> <p>The diagram above is a schematic diagram of a household circuit. The house shown in the above diagram has 5 usable spaces where electrical connections are made. For this house, the mains have a voltage of 220 V and the net current coming from the mains is 22A.</p> <ol style="list-style-type: none"> <li>What is the mode of connection to all the spaces in the house from the mains?</li> <li>The spaces 5 and 4 have the same resistance and spaces 3 and 2 have respective resistances of <math>20\Omega</math> and <math>30\Omega</math>. Space 1 has a resistance double that of space 5. What is the net resistance for space 5.</li> <li>What is the current in space 3?</li> <li>What should be placed between the main connection and the rest of the house's electrical appliances to save them from accidental high electric current?</li> </ol> | 5 |
|----|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|

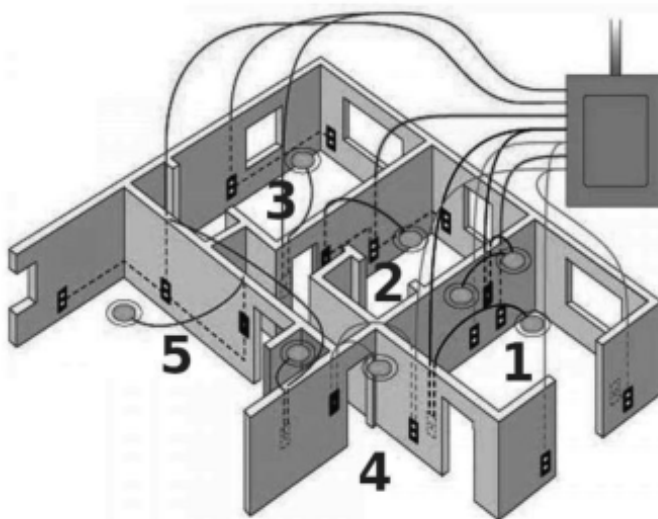

Source/editorial note: Full Q36(a-d) retained after NCERT-based chapter audit: parallel circuits and resistances are Electricity, and protective fuse function is explicitly NCERT Electricity section 11.7.1 (printed p190). Printed parent total = 5 marks. Official MS p6 supplies (a) and (b), but omits (c) and (d). Do not infer subpart mark allocations for those omissions. Answer (c)=11 A is independently derived, not an official MS answer. Answer (d) is not supplied here as an official answer. Official answer unavailable/withheld for an identified error, omission or incomplete verification: Official MS omits c,d; independent c derivation labelled; complete answer not verified. Consult the linked original marking scheme with this limitation in mind.

14. [4 marks] Source Q39 OR iv • 2023-24

|    |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                        |       |
|----|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-------|
| 39 | <div data-bbox="494 201 1085 470" data-label="Diagram"> <p>The diagram shows a 12V battery on the left. The positive terminal is at the top. A wire goes from the positive terminal to a junction. From this junction, a wire goes to the top of the first 4.0 Ω lamp. Another wire goes from the junction to a switch labeled 'A'. The switch has three positions: 1 (top), 2 (middle), and 3 (bottom). Position 1 is connected to the top of the second 4.0 Ω lamp. Position 2 is connected to the top of the first 12 Ω lamp. Position 3 is connected to the top of the second 12 Ω lamp. All four lamps are connected to a common bottom wire that returns to the negative terminal of the battery.</p> </div> <p>Vinita and Ahmed demonstrated a circuit that operates the two headlights and the two sidelights of a car, in their school exhibition. Based on their demonstrated circuit, answer the following questions.</p> <p>(i) State what happens when switch A is connected to</p> <ol style="list-style-type: none"> <li>Position 2</li> <li>Position 3</li> </ol> <p>(ii) Find the potential difference across each lamp when lit.</p> | 1+1+2 |
|    | <p style="text-align: center;"><b>OR</b></p> <p>(iv) Show, with calculations, which type of lamp, <math>4.0\ \Omega</math> or <math>12\ \Omega</math>, has the higher power.</p>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                       |       |

Source/editorial note: Includes common (i), (ii) and OR (iv); 1+1+2 marks. Original scheme mislabels second line of (i) as (a). Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

# Solutions and verification status

Only explicitly verified solutions are printed. A missing solution is not a claim that the question is unsolvable.

## Question 1 — pyq-2026-2857cf20146cab1a7997ae98

Official answer unavailable/withheld: No independently verified official answer supplied.

Original marking scheme (see limitation above): [https://www.cbse.gov.in/cbsenew/marketing-scheme/2026/X/086\\_SCIENCE.zip](https://www.cbse.gov.in/cbsenew/marketing-scheme/2026/X/086_SCIENCE.zip)

## Question 2 — SQP-2019-20-Q14

iv) Assertion is false but reason is true.

|    |                                            |        |
|----|--------------------------------------------|--------|
| 14 | iv) Assertion is false but reason is true. | 1 mark |
|----|--------------------------------------------|--------|

Marking-scheme PDF page(s): [2]

[https://cbseacademic.nic.in/web\\_material/SQP/ClassX\\_2019\\_20/Science\\_MS.pdf](https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_MS.pdf)

## Question 3 — SQP\_2026-27\_q31

C. 4.0 A

|    |          |   |
|----|----------|---|
| 31 | C. 4.0 A | 1 |
|----|----------|---|

Marking-scheme PDF page(s): [7]

[https://cbseacademic.nic.in/web\\_material/SQP/ClassX\\_2026\\_27/Science-MS.pdf](https://cbseacademic.nic.in/web_material/SQP/ClassX_2026_27/Science-MS.pdf)

## Question 4 — pyq-2023-dc74f0e84e53633b06097022

Official answer unavailable/withheld: No independently verified official answer supplied.

## Question 5 — pyq-2023-246eac3017f0793c27bba6a6

Official answer unavailable/withheld: No independently verified official answer supplied.

## Question 6 — pyq-2024-1e2d386b35acad1e9e07f369

Official answer unavailable/withheld: No independently verified official answer supplied.

## Question 7 — pyq-2025-50a1900d91ebeada79f31c34

Official answer unavailable/withheld: No independently verified official answer supplied.

## Question 8 — SQP\_2025-26\_q34\_VI\_A

(i) Maximum Resistance:

To get the maximum resistance, connect all four resistors in series.

The total resistance  $R_{\max}$  in series is the sum of the individual resistance:

$$R_{\max} = R + R + R + R = 4R$$

(ii) Minimum Resistance:

To get the minimum resistance, connect all four resistors in parallel.

The total resistance  $R_{\min}$  in parallel is given by:

$$1/R_{\min} = 1/R + 1/R + 1/R + 1/R = 4/R \Rightarrow R_{\min} = R/4$$



For visually impaired students

A.

(i) Maximum Resistance:

- To get the maximum resistance, connect all four resistors in series.
- The total resistance  $R_{max}$  in series is the sum of the individual resistance:

$$R_{max} = R + R + R + R = 4R$$

(ii) Minimum Resistance:

- To get the minimum resistance, connect all four resistors in parallel.

- The total resistance  $R_{min}$  in parallel is given by:

$$\frac{1}{R_{min}} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \frac{1}{R} = \frac{4}{R}$$

$$R_{min} = \frac{R}{4}$$

Marking-scheme PDF page(s): [7, 8]

[https://cbseacademic.nic.in/web\\_material/SQP/ClassX\\_2025\\_26/Science-MS.pdf](https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-MS.pdf)

Question 9 — sqp\_2021-22\_term2\_q11

(a)  $E = P \times T = 3 \times 2 = 6$  kWh. Cost =  $6 \times 3.50 = \text{Rs. } 21.0$ . (b) To reduce the boiling time, the rate of heat production should be large.  $P = V^2/R$ ;  $V$  is constant, so  $R$  should be decreased. Since  $R$  is directly proportional to length  $l$ , the length should be decreased.

|    |                                                                                                                                                                                                                                                                                                                          |           |   |
|----|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------|---|
| 11 | <p>a. <math>E = P \times T</math><br/> SO, <math>E = 3 \times 2 = 6</math> kWh<br/> Cost of buying electricity from the main electricity board = <math>6 \times 3.50 = \text{Rs. } 21.0</math></p>                                                                                                                       | (1 mark)  | 3 |
|    | <p>b. To reduce the boiling time using the same mains supply, the rate of heat production should be large. We know that <math>P = V^2/R</math>. Since <math>V</math> is constant, <math>R</math> should be decreased. Since <math>R</math> is directly proportional to <math>l</math> so length should be decreased.</p> | (2 marks) |   |

Marking-scheme PDF page(s): [3, 4]

[https://cbseacademic.nic.in/web\\_material/SQP/ClassX\\_2021\\_22/Science-MS\\_Term2.pdf](https://cbseacademic.nic.in/web_material/SQP/ClassX_2021_22/Science-MS_Term2.pdf)

Question 10 — SQP\_2024-25\_q32

A.  $R \propto l$

$R \propto l/A$

$R = \rho l/A$ . (1.5)

B.  $R = \rho l/A$

$\rho = R A/l$  for  $A = 1\text{m}^2$  and  $l = 1\text{m}$ , we have

$\rho = R$

Hence resistivity is the resistance offered by a wire of length 1 m having a cross sectional area of  $1\text{ m}^2$ . (1.5)

|    |                                                                                                                                                                                                                                                                                                                                                           |   |
|----|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|
| 32 | <p>A.</p> $R \propto l$ $R \propto \frac{l}{A}$ $R = \rho \frac{l}{A} \quad (1.5)$ <p>B.</p> $R = \rho \frac{l}{A}$ $\rho = R \frac{A}{l} \text{ for } A = 1\text{m}^2 \text{ and } l = 1\text{m, we have}$ $\rho = R$ <p>Hence resistivity is the resistance offered by a wire of length 1 m having a cross sectional area of 1 m<sup>2</sup>. (1.5)</p> | 3 |
|----|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|

Marking-scheme PDF page(s): [5]

[https://cbseacademic.nic.in/web\\_material/SQP/ClassX\\_2024\\_25/Science-MS.pdf](https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-MS.pdf)

### Question 11 — pyq-2025-179b945e5fe9505f3715ef55

Official answer unavailable/withheld: No independently verified official answer supplied.

### Question 12 — pyq-2026-b2053a5342a24ba0adc2e791

Official answer unavailable/withheld: No independently verified official answer supplied.

Original marking scheme (see limitation above): [https://www.cbse.gov.in/cbsenew/marketing-scheme/2026/X/086\\_SCIENCE.zip](https://www.cbse.gov.in/cbsenew/marketing-scheme/2026/X/086_SCIENCE.zip)

### Question 13 — sqp\_2022-23\_q36

Official answer unavailable/withheld: Official MS omits c,d; independent c derivation labelled; complete answer not verified.

Original marking scheme (see limitation above): [https://cbseacademic.nic.in/web\\_material/SQP/ClassX\\_2022\\_23/Science-M S.pdf](https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-M S.pdf)

### Question 14 — SQP\_2023-24\_q39\_OR\_iv

(i) 12 Ω lamps (only) on.

(a) 4 Ω lamps (only) on [0.5+0.5]

(ii) 12 V for both sets of lamps and all of them are in parallel. [1]

OR

$$P = V^2/R$$

All lamps are in parallel and hence same V for all lamps.

For 4 Ω lamps →  $P = (12 \times 12)/4 = 36 \text{ W}$

For 12 Ω lamps →  $P = (12 \times 12)/12 = 12 \text{ W}$

Hence 4 Ω lamps will have higher power. [0.5 x 4]

|    |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                             |   |
|----|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|
| 39 | <p>(i) 12 Ω lamps (only) on.</p> <p>(a) 4 Ω lamps (only) on [0.5+0.5]</p> <p>(ii) 12 V for both sets of lamps and all of them are in parallel. [1]</p> <p style="text-align: center;"><b>OR</b></p> <p><math>P = V^2 / R</math></p> <p>All lamps are in parallel and hence same V for all lamps.</p> <p>For 4 Ω lamps → <math>P = \frac{12 \times 12}{4} = 36 \text{ W}</math></p> <p>For 12 Ω lamps → <math>P = \frac{12 \times 12}{12} = 12 \text{ W}</math></p> <p>Hence 4 Ω lamps will have higher power. [0.5 x 4]</p> | 4 |
|----|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|

Marking-scheme PDF page(s): [6]

[https://cbseacademic.nic.in/web\\_material/SQP/ClassX\\_2023\\_24/Science-MS.pdf](https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-MS.pdf)

# Per-question source appendix

Original CBSE questions/images remain attributed to their source. Compilation selection and numbering are editorial. The full Science source PDFs may include unrelated chapters; only selected Electricity crops form this worksheet.

## 1. pyq-2026-2857cf20146cab1a7997ae98

CBSE Class X Science 2026 First Board 31(B)-Science for V.I. | PYQ | Year/session: 2026 / 2026 First Board | Paper code: 31/B | Source question: 30 | Original section: Section C (Physics) | Selected marks: 1 | PDF pages (one-based): 21

<https://www.cbse.gov.in/cbsenew/question-paper/2026/X/Science.zip>

Also used in: official-01

## 2. SQP-2019-20-Q14

Science-086 Sample Question Paper 2019-20 Class-X | SQP | Year/session: 2019-20 / 2019-20 | Paper code: Not recorded | Source question: 14 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 5, 6

[https://cbseacademic.nic.in/web\\_material/SQP/ClassX\\_2019\\_20/Science\\_SQP.pdf](https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_SQP.pdf)

Also used in: official-03, official-05, official-09, official-13

## 3. SQP\_2026-27\_q31

CBSE Class X Science (086) Sample Question Paper 2026-27 (English) | SQP | Year/session: 2026-27 / 2026-27 | Paper code: Not recorded | Source question: 31 | Original section: Section – C | Selected marks: 1 | PDF pages (one-based): 11

[https://cbseacademic.nic.in/web\\_material/SQP/ClassX\\_2026\\_27/Science-SQP.pdf](https://cbseacademic.nic.in/web_material/SQP/ClassX_2026_27/Science-SQP.pdf)

Also used in: official-01, official-05, official-08, official-12, official-15

## 4. pyq-2023-dc74f0e84e53633b06097022

CBSE — Class X Science — 2023 — compartment | PYQ | Year/session: 2023 / compartment | Paper code: Not recorded | Source question: 15 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 11

<https://www.cbse.gov.in/cbsenew/question-paper/2023-COMPTT/X/Science.zip>

Also used in: official-02, official-03, official-06, official-09, official-14

## 5. pyq-2023-246eac3017f0793c27bba6a6

CBSE — Class X Science — 2023 — main — 31/2/1 | PYQ | Year/session: 2023 / main | Paper code: 31/2/1 | Source question: 25 | Original section: SECTION B | Selected marks: 2 | PDF pages (one-based): 15

<https://www.cbse.gov.in/cbsenew/question-paper/2023/X/SCIENCE.zip>

Also used in: official-04, official-07, official-08, official-14

## 6. pyq-2024-1e2d386b35acad1e9e07f369

CBSE — Class X Science — 2024 — main — 31/4/1 | PYQ | Year/session: 2024 / main | Paper code: 31/4/1 | Source question: 26 | Original section: SECTION B | Selected marks: 2 | PDF pages (one-based): 13

<https://www.cbse.gov.in/cbsenew/question-paper/2024/X/SCIENCE.zip>

Also used in: official-05, official-08, official-14

## 7. pyq-2025-50a1900d91ebeada79f31c34

CBSE — Class X Science — 2025 — main — 31/3/1 | PYQ | Year/session: 2025 / main | Paper code: 31/3/1 | Source question: 26 | Original section: SECTION B | Selected marks: 2 | PDF pages (one-based): 13

[https://www.cbse.gov.in/cbsenew/question-paper/2025/X/086\\_Science.zip](https://www.cbse.gov.in/cbsenew/question-paper/2025/X/086_Science.zip)

Also used in: official-02, official-12

## 8. SQP\_2025-26\_q34\_VI\_A

CBSE Class X Science (086) Sample Question Paper 2025-26 (English) | SQP | Year/session: 2025-26 / 2025-26 | Paper code: Not recorded | Source question: 34 VI A | Original section: Section – C | Selected marks: 2 | PDF pages (one-based): 12

[https://cbseacademic.nic.in/web\\_material/SQP/ClassX\\_2025\\_26/Science-SQP.pdf](https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-SQP.pdf)

Also used in: official-03, official-06

## 9. sqp\_2021-22\_term2\_q11

CBSE Class X Science (086) Sample Question Paper 2021-22 — Term 2 | SQP | Year/session: 2021-22 / 2021-22 | Paper code: Not recorded | Source question: 11 | Original section: Section B | Selected marks: 3 | PDF pages (one-based): 4

[https://cbseacademic.nic.in/web\\_material/SQP/ClassX\\_2021\\_22/Science-SQP\\_Term2.pdf](https://cbseacademic.nic.in/web_material/SQP/ClassX_2021_22/Science-SQP_Term2.pdf)

Also used in: official-03

## 10. SQP\_2024-25\_q32

CBSE Class X Science (086) Sample Question Paper 2024-25 (English) | SQP | Year/session: 2024-25 / 2024-25 | Paper code: Not recorded | Source question: 32 | Original section: Section-C | Selected marks: 3 | PDF pages (one-based): 9

[https://cbseacademic.nic.in/web\\_material/SQP/ClassX\\_2024\\_25/Science-SQP.pdf](https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-SQP.pdf)

Also used in: official-06, official-15

## 11. pyq-2025-179b945e5fe9505f3715ef55

CBSE — Class X Science — 2025 — compartment — 31/S/3 | PYQ | Year/session: 2025 / compartment | Paper code: 31/S/3 | Source question: 31 | Original section: SECTION C | Selected marks: 3 | PDF pages (one-based): 15

<https://www.cbse.gov.in/cbsenew/question-paper/2025-COMPTT/X/Science.zip>

Also used in: official-02, official-05

## 12. pyq-2026-b2053a5342a24ba0adc2e791

CBSE Class X Science 2026 First Board 31-3-2 | PYQ | Year/session: 2026 / 2026 First Board | Paper code: 31/3/2 | Source question: 35 | Original section: Section C (Physics) | Selected marks: 3 | PDF pages (one-based): 27

<https://www.cbse.gov.in/cbsenew/question-paper/2026/X/Science.zip>

No cross-paper reuse.

## 13. sqp\_2022-23\_q36

CBSE Class X Science (086) Sample Question Paper 2022-23 | SQP | Year/session: 2022-23 / 2022-23 | Paper code: Not recorded | Source question: 36 | Original section: Section D | Selected marks: 5 | PDF pages (one-based): 9

[https://cbseacademic.nic.in/web\\_material/SQP/ClassX\\_2022\\_23/Science-SQP.pdf](https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-SQP.pdf)

Also used in: official-02

## 14. SQP\_2023-24\_q39\_OR\_iv

CBSE Class X Science (086) Sample Question Paper 2023-24 (English) | SQP | Year/session: 2023-24 / 2023-24 | Paper code: Not recorded | Source question: 39 OR iv | Original section: Section-E | Selected marks: 4 | PDF pages (one-based): 8

[https://cbseacademic.nic.in/web\\_material/SQP/ClassX\\_2023\\_24/Science-SQP.pdf](https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-SQP.pdf)

Also used in: official-01, official-08, official-12, official-15