

Official-source Electricity compilation 12

Mixed-source chapter worksheet • cross-paper reuse disclosed

Total: 35 marks • Suggested time: 70 minutes

Instructions and reuse disclosure

Curated compilation of official CBSE source questions, not a CBSE-issued chapter paper. Original source labels and exact source images are retained.

Answer every selected question. Only one selected source-slot alternative appears in this paper; do not answer or count excluded alternatives.

Questions recur across this 15-paper collection. Reuse is disclosed per question in the source appendix; these are not 15 disjoint official papers.

Sections use available source marks: A MCQ; B 2 marks; C 3 marks; D 5 marks or source-marked case questions. Case marks are not inflated to five.

Section A — MCQ

Compilation questions 1-4; 4 marks. Exact source labels remain attached to each question.

Section B — 2-mark questions

Compilation questions 5-8; 8 marks. Exact source labels remain attached to each question.

Section C — 3-mark questions

Compilation questions 9-11; 9 marks. Exact source labels remain attached to each question.

Section D — 5-mark / case-based questions

Compilation questions 12-14; 14 marks. Exact source labels remain attached to each question.

Section A — MCQ

1. [1 marks] Source Q7 • 2019-20

- | | | |
|---|--|---|
| 7 | Unit of electric power may also be expressed as: | 1 |
| | i) volt-ampere | |
| | ii) kilowatt-hour | |
| | iii) watt-second | |
| | iv) joule-second | |



2. [1 marks] Source Q14 • main

14. An electric iron of resistance $20\ \Omega$ draws a current of 5 A . The heat developed in the iron in 30 seconds is :

- (A) 15000 J (B) 6000 J
(C) 1500 J (D) 3000 J

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

3. [1 marks] Source Q15 • 2022-23

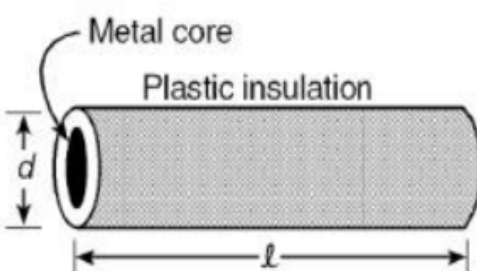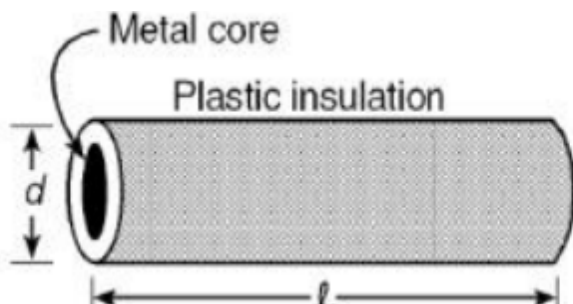15	 Plastic insulation surrounds a wire having diameter d and length l as shown above. A decrease in the resistance of the wire would be produced by an increase in the (a) length l of the wire (b) diameter d of the wire (c) temperature of the wire (d) thickness of the plastic insulation 	1
----	---	---

4. [1 marks] Source Q31 • 2026-27

31	An electrical appliance rated 1000 W is operated at 250 V. What current does it draw? A. 0.25 A B. 2.5 A C. 4.0 A D. 10 A	1
----	---	---

Source/editorial note: Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

Section B — 2-mark questions

5. [2 marks] Source Q26 • main

- 26.** An electric kettle is rated 230 V; 1000 W. Calculate the resistance of its heating element when in operation.

2


Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

6. [2 marks] Source Q27 • main

The range of a milliammeter is 0-500 mA. There are 20 divisions between 0 and 100 mA mark on its scale. During an experiment a student observes ammeter's pointer at 3rd graduation mark after zero mark when the key is off and the pointer at 15th graduation mark after 300 mA mark when the key is inserted into the plug. Find (i) the least count, (ii) the zero error with proper sign and (iii) the value of current drawn from the battery.

Source/editorial note: Occurrence mappings retained verbatim; only primary PDF/question evidence is accepted and counted. Other occurrences require their own evidence validation. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

7. [2 marks] Source Q34 A • 2025-26

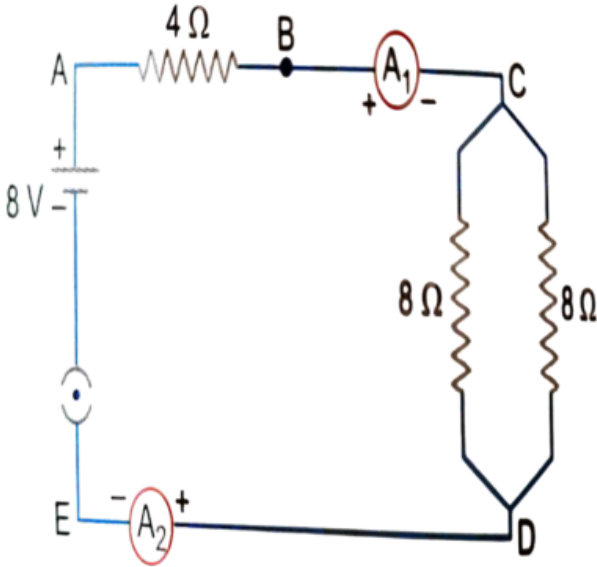34	<u>Attempt either option A or B.</u> A.  Find out the following in the electric circuit given in the figure- (i) Effective resistance of two 8 ohm resistors in the combination. (ii) Current flowing through the 4-ohm resistor	2
----	---	---

Source/editorial note: Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

8. [2 marks] Source Q25 VI A • 2024-25

	<u>For visually impaired students</u> A. We have four resistors A, B, C and D of resistance 3 Ω, 6 Ω, 9 Ω and 12 Ω respectively. Find out the lowest resistance which can be obtained by combining these four resistors.	
--	--	--

Source/editorial note: Official MS arithmetic error retained: $1/12 = 3/36$, not $2/36$. Independently calculated correct minimum = $36/25 = 1.44 \Omega$; this correction is not substituted into the official answer. Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence. Official answer unavailable/withheld for an identified error, omission or incomplete verification: Official arithmetic answer 1.5 ohm is erroneous; correct 1.44 ohm documented separately. Consult the linked original marking scheme with this limitation in mind.

Section C — 3-mark questions

9. [3 marks] Source Q37 • 2026 First Board

37. The values of current I flowing in a given resistor for the corresponding values of potential difference V applied across the ends of resistor are given below in the table :


I (Amperes)	0.4	0.8	1.2	1.6	2.0
V (Volts)	1.2	2.4	3.6	4.8	6.0

Plot a graph between V and I and calculate the resistance of that resistor. 3

Source/editorial note: Visually confirmed complete replacement crop: question number, wording, all options/table values, mathematical symbols and printed marks. Whitespace normalized; mathematical glyphs represented in Unicode and stacked fractions as $I/4$ and $V/4$. Page/QR/footer debris removed from text; marks retained in marks field. No supplied diagram; table retained in text and evidence. Answers not reviewed. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.


10. [3 marks] Source Q12 • 2021-22

12

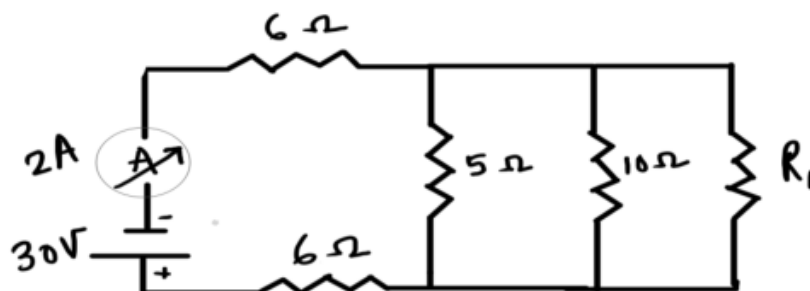

3

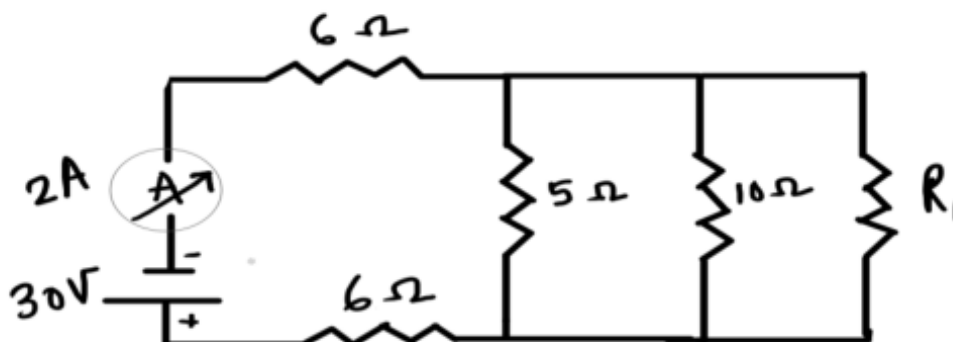In the above circuit, if the current reading in the ammeter A is 2A, what would be the value of R_1 ?



Source/editorial note: Main and OR are separate three-mark alternatives sharing a single three-mark exam slot. MS incorrectly calls the $5\ \Omega$, $10\ \Omega$ and R_1 block "in series", although its reciprocal formula and source circuit show parallel; MS also prints $R_{eq} = 15\ A$ instead of $15\ \Omega$. These source errors are explicitly corrected in answer.

11. [3 marks] Source Q10 • main

10. (a) Calculate the resistance of a metal wire of length 2 m and area of cross-section $1.55 \times 10^{-6} \text{ m}^2$.

(Resistivity of the metal is $2.8 \times 10^{-8} \Omega \text{ m}$)


- (b) Why are alloys preferred over pure metals to make the heating elements of electrical heating devices ?


2+1

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

Section D — 5-mark / case-based questions


12. [5 marks] Source Q36 • 2020-21

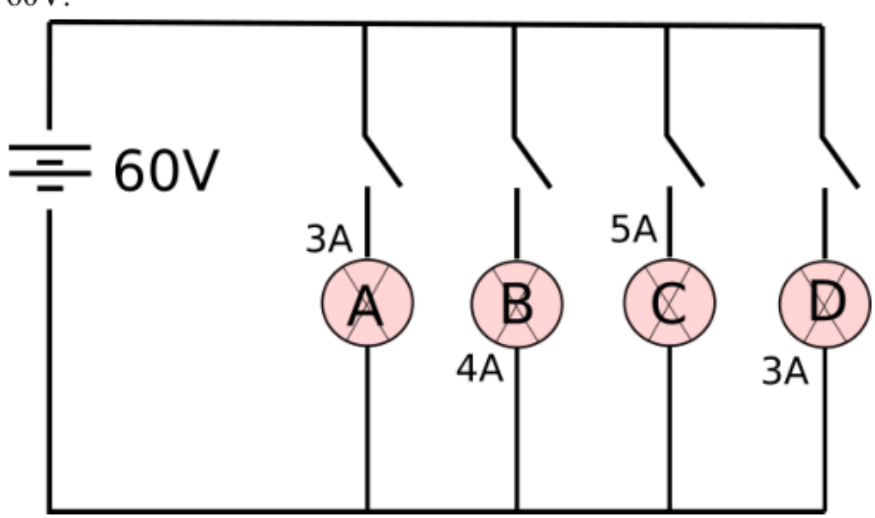36	In the given circuit, A, B, C and D are four lamps connected with a battery of 60V.  Analyse the circuit to answer the following questions. (i) What kind of combination are the lamps arranged in (series or parallel)? (ii) Explain with reference to your above answer, what are the advantages (any two) of this combination of lamps? (iii) Explain with proper calculations which lamp glows the brightest? (iv) Find out the total resistance of the circuit.	5
----	--	---

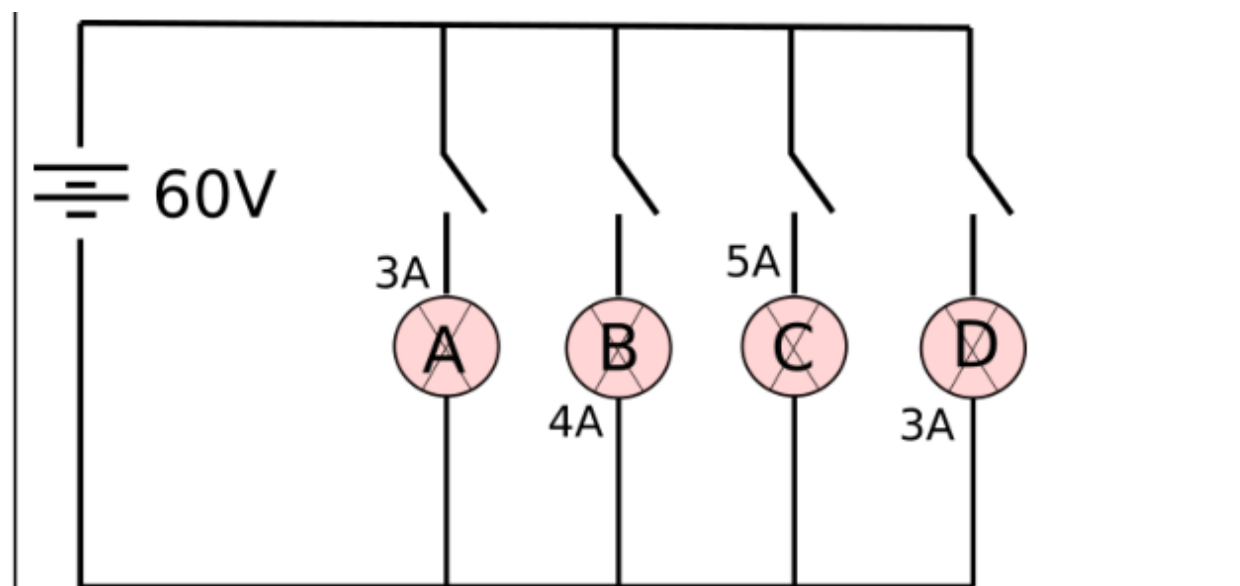


Source/editorial note: All four subparts retained. The OR alternative on pp.14-15 concerns magnetic fields and the right-hand thumb rule and is excluded. Source MS p.8 prints " $= 60/15 \text{ A} = 4\text{A}$ "; the resistance unit is corrected explicitly to Ω , not silently attributed to the source.

13. [4 marks] Source Q39 OR iv • 2023-24

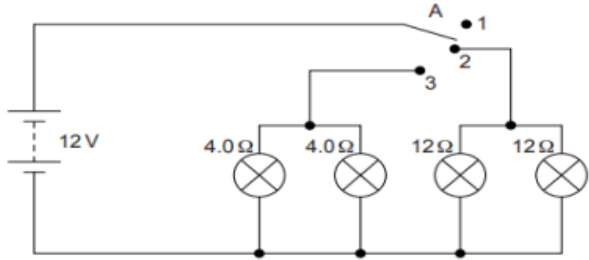39	 Vinita and Ahmed demonstrated a circuit that operates the two headlights and the two sidelights of a car, in their school exhibition. Based on their demonstrated circuit, answer the following questions. (i) State what happens when switch A is connected to - Position 2 - Position 3 (ii) Find the potential difference across each lamp when lit. OR (iv) Show, with calculations, which type of lamp, $4.0\ \Omega$ or $12\ \Omega$, has the higher power.	1+1+2
----	---	-------

Source/editorial note: Includes common (i), (ii) and OR (iv); 1+1+2 marks. Original scheme mislabels second line of (i) as (a). Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

14. [5 marks] Source Q36 A • 2024-25

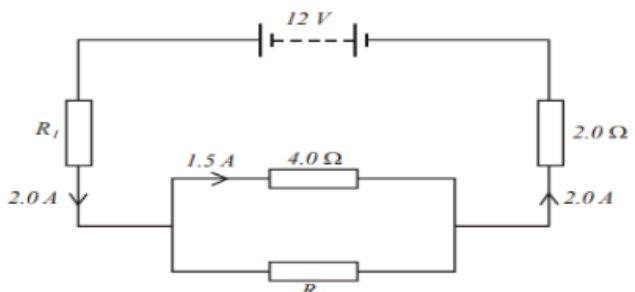36	<u>Attempt either option A or B.</u> A.  The above circuit is a part of an electrical device. Use the information given in the question to calculate the following. - Potential Difference across R_2. - Value of the resistance R_2. - Value of resistance R_1.	5
----	--	---

Source/editorial note: Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

Solutions and verification status

Only explicitly verified solutions are printed. A missing solution is not a claim that the question is unsolvable.

Question 1 — cbse_sqp_2019-20_electricity_q7

i) volt-ampere. Power = Voltage $\times$ Current.

7	i) volt-ampere Power = Voltage $\times$ Current.	1 mark
---	---	--------

Marking-scheme PDF page(s): [1]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_MS.pdf

Question 2 — pyq-2024-a415e02467405f8b9fbacfc3

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 3 — sqp_2022-23_q15

(b) diameter d of the wire

15.	(b) diameter d of the wire	1
-----	----------------------------	---

Marking-scheme PDF page(s): [1]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-MS.pdf

Question 4 — SQP_2026-27_q31

C. 4.0 A

31	C. 4.0 A	1
----	----------	---

Marking-scheme PDF page(s): [7]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2026_27/Science-MS.pdf

Question 5 — pyq-2025-50a1900d91ebeada79f31c34

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 6 — pyq-2018-7253f82c5332b612f2b92314

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 7 — SQP_2025-26_q34_A

A.

(i) $R = \frac{R_1 R_2}{R_1 + R_2} = \frac{(8 \times 8)}{(8 + 8)} = 4 \text{ ohms}$

(ii) $I = \frac{V}{R} = \frac{8}{(4 + 4)} = 1 \text{ A}$

34	<u>Student to attempt either A or B.</u> A. (i) $R = \frac{R_1 R_2}{R_1 + R_2} = \frac{8 \times 8}{8 + 8} = 4 \text{ ohms}$ (ii) $I = \frac{V}{R} = \frac{8}{(4 + 4)} = 1 \text{ A}$ OR	2
----	---	---

Marking-scheme PDF page(s): [7]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-MS.pdf

Question 8 — SQP_2024-25_q25_VI_A

Official answer unavailable/withheld: Official arithmetic answer 1.5 ohm is erroneous; correct 1.44 ohm documented separately.

Original marking scheme (see limitation above): https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-MS.pdf


Question 9 — pyq-2026-55a6ea37078fb0fe5e79e7be

Official answer unavailable/withheld: No independently verified official answer supplied.

Original marking scheme (see limitation above): https://www.cbse.gov.in/cbsenew/marketing-scheme/2026/X/086_SCIENCE.zip

Question 10 — sqp_2021-22_term2_q12_main

$R_1 = 30 \Omega$. The parallel block has $1/R_p = 1/5 + 1/10 + 1/R_1$, so $R_p = 10R_1/(3R_1 + 10)$. The two 6Ω resistors are in series with that block. $R_{eq} = 30/2 = 15 \Omega$, hence $12 + 10R_1/(3R_1 + 10) = 15$ and $R_1 = 30 \Omega$.

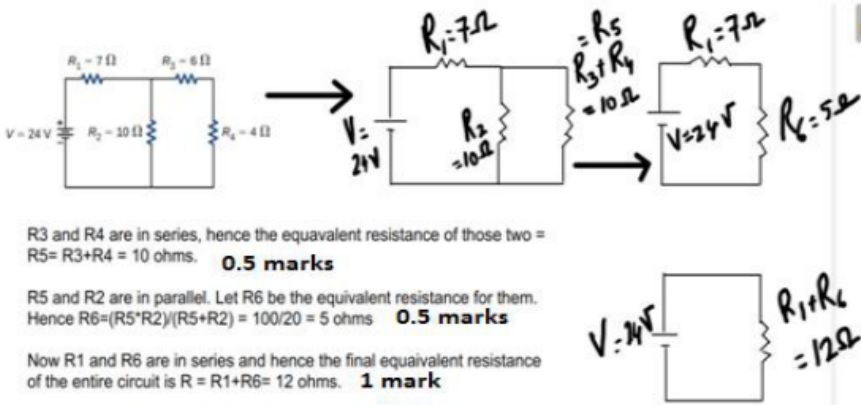12	5 ohm, 10 ohm and R_1 are in series $1/R_p = 1/5 + 1/10 + 1/R_1$ $1/R_p = (2+1)/10 + 1/R_1$ $= 3/10 + 1/R_1$ $1/R_p = (3R_1 + 10)/10R_1$ $R_p = 10R_1 / (3R_1 + 10)$ Now, 6 ohm, 6 ohm and R_p are in series Thus, $R_{eq} = 12 + 10R_1 / (3R_1 + 10) \text{ ----- (1)} \quad (1 \text{ mark})$ $V = I R_{eq}$ From the circuit $R_{eq} = 30/2 = 15 \text{ A ----- (2)} \quad (1 \text{ mark})$ Equating (1) and (2) $12 + 10R_1 / (3R_1 + 10) = 15$ $10R_1 / (3R_1 + 10) = 3$ $10R_1 = (9R_1 + 30)$ Thus, $R_1 = 30 \text{ ohm.}$ (1 mark) OR  R3 and R4 are in series, hence the equivalent resistance of those two = $R_5 = R_3 + R_4 = 10 \text{ ohms.}$ 0.5 marks R5 and R2 are in parallel. Let R_6 be the equivalent resistance for them. Hence $R_6 = (R_5 \cdot R_2) / (R_5 + R_2) = 100/20 = 5 \text{ ohms}$ 0.5 marks Now R_1 and R_6 are in series and hence the final equivalent resistance of the entire circuit is $R = R_1 + R_6 = 12 \text{ ohms.}$ 1 mark By Ohm's Law we know that $V = IR$, hence $I = V/R$. Hence the current in the circuit is $24/12 \text{ A} = 2 \text{ A}$ (Final Answer) 1 mark (0.5+0.5+1+1)	3
----	---	---

Marking-scheme PDF page(s): [4]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2021_22/Science-MS_Term2.pdf

Question 11 — pyq-2022-cfec2ef8067dd02793a5ebf2

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 12 — sqp_2020-21_q36_main

(i) The lamps are in parallel. (ii) A faulty lamp does not affect the working of the others; all lamps use the full potential of the battery. (iii) The lamp with the highest power glows brightest. All have the same voltage; C has the largest current. $PC = 5 \times 60 = 300 \text{ W}$, the maximum. (iv) Total current = $3 + 4 + 5 + 3 = 15 \text{ A}$; $R = V/I = 60/15 = 4 \Omega$. The MS prints the final unit incorrectly as A.

36	The lamps are in parallel.	1
	Advantages: If one lamp is faulty, it will not affect the working of the other lamps. They will also be using the full potential of the battery as they are connected in parallel.	1
	The lamp with the highest power will glow the brightest. $P=VI$	1
	In this case, all the bulbs have the same voltage. But lamp C has the highest current. Hence, for Lamp C $P=5 \times 60 \text{ Watt} = 300 \text{ W}$. (the maximum).	1
	The total current in the circuit $= 3+4+5+3 \text{ A} = 15\text{A}$ The Voltage $= 60\text{V}$ $V=IR$ and hence $R = V/I$ $= 60/15 \text{ A} = 4\text{A}$	1

Marking-scheme PDF page(s): [8]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2020_21/Science-MS.pdf

Question 13 — SQP_2023-24_q39_OR_iv

(i) 12 Ω lamps (only) on.

(a) 4 Ω lamps (only) on [0.5+0.5]

(ii) 12 V for both sets of lamps and all of them are in parallel. [1]

OR

$$P = V^2/R$$

All lamps are in parallel and hence same V for all lamps.

For 4 Ω lamps $\rightarrow P = (12 \times 12)/4 = 36 \text{ W}$

For 12 Ω lamps $\rightarrow P = (12 \times 12)/12 = 12 \text{ W}$

Hence 4 Ω lamps will have higher power. [0.5 x 4]

39	(i) 12 Ω lamps (only) on. (a) 4 Ω lamps (only) on [0.5+0.5] (ii) 12 V for both sets of lamps and all of them are in parallel. [1]	4
	OR	
	$P = V^2 / R$ All lamps are in parallel and hence same V for all lamps. For 4 Ω lamps $\rightarrow P = \frac{12 \times 12}{4} = 36 \text{ W}$ For 12 Ω lamps $\rightarrow P = \frac{12 \times 12}{12} = 12 \text{ W}$ Hence 4 Ω lamps will have higher power. [0.5 x 4]	

Marking-scheme PDF page(s): [6]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-MS.pdf

Question 14 — SQP_2024-25_q36_A

A.

(i) p.d. across 4 Ω resistor = p.d. Across R_2 as both are in parallel. (0.5)

$$1.5 \text{ (A)} \times 4 \text{ (}\Omega\text{)} = 6 \text{ V (0.5)}$$

(ii) Total Current through 4 Ω and $R_2 = 2.0 \text{ A}$ (given).

Current through 4 $\Omega = 1.5 \text{ A}$ (given) (0.5)

Hence current through $R_2 = 2 - 1.5 = 0.5 \text{ A}$

Using Ohm's law for R_2 we get (0.5)

$$6 \text{ V} = 0.5 \text{ A} \times R_2$$

Hence $R_2 = 6/0.5 = 12 \Omega$ (0.5)

(iii) p.d. across $R_1 = \text{Total p.d.} - (\text{p.d. across } R_2) - (\text{p.d. across } 2.0 \Omega)$ (0.5)

p.d. across 2.0 $\Omega = 2 \times 2 = 4 \text{ V}$

p.d. across $R_2 = 6 \text{ V}$ (calculated before) (0.5)

Hence p.d. across $R_1 = 12 - 6 - 4 = 2 \text{ V}$ (0.5)

Current through $R_1 = 2 \text{ A}$ (0.5)

Using Ohm's Law, we get

$$R_1 = 2\text{V}/2\text{A} = 1\Omega \text{ (0.5)}$$

Alternative method

Total Resistance = $R_1 + (4 \times 12)/(4+12) + 2 = 12\text{V}/2 \text{ A} = 6\Omega$ (0.5)

$$R_1 = 6 - (3 + 2) = 1 \Omega \text{ (0.5)}$$

36	<u>Students to attempt either option A or B.</u>	5
	A.	
	(i) p.d. across 4 Ω resistor = p.d. Across R_2 as both are in parallel.	(0.5)
	$1.5 \text{ (A)} \times 4 \text{ (}\Omega\text{)} = 6 \text{ V}$	(0.5)
	(ii) Total Current through 4 Ω and $R_2 = 2.0 \text{ A}$ (given).	
	Current through 4 $\Omega = 1.5 \text{ A}$ (given)	(0.5)
	Hence current through $R_2 = 2 - 1.5 = 0.5 \text{ A}$	
	Using Ohm's law for R_2 we get	(0.5)
	$6 \text{ V} = 0.5 \text{ A} \times R_2$	
	Hence $R_2 = 6/0.5 = 12 \Omega$	(0.5)
	(iii) p.d. across $R_1 = \text{Total p.d.} - (\text{p.d. across } R_2) - (\text{p.d. across } 2.0 \Omega)$	
	(0.5)	
	p.d. across 2.0 $\Omega = 2 \times 2 = 4 \text{ V}$	
	p.d. across $R_2 = 6 \text{ V}$ (calculated before)	(0.5)
	Hence p.d. across $R_1 = 12 - 6 - 4 = 2 \text{ V}$	(0.5)
	Current through $R_1 = 2 \text{ A}$	(0.5)
	Using Ohm's Law, we get	
	$R_1 = 2\text{V}/2\text{A} = 1\Omega$	(0.5)
	Alternative method	
	Total Resistance = $R_1 + \frac{(4 \times 12)}{(4+12)} + 2 = 12\text{V}/2 \text{ A} = 6\Omega$	(0.5)
	$R_1 = 6 - (3 + 2) = 1 \Omega$	(0.5)

Marking-scheme PDF page(s): [8, 9]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-MS.pdf

Per-question source appendix

Original CBSE questions/images remain attributed to their source. Compilation selection and numbering are editorial. The full Science source PDFs may include unrelated chapters; only selected Electricity crops form this worksheet.

1. cbse_sqp_2019-20_electricity_q7

Class-X Science-086 SAMPLE QUESTION PAPER 2019-20 | SQP | Year/session: 2019-20 / 2019-20 | Paper code: Not recorded | Source question: 7 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 4

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_SQP.pdf

Also used in: official-02, official-04, official-08, official-14

2. pyq-2024-a415e02467405f8b9fbacfc3

CBSE — Class X Science — 2024 — main — 31/4/1 | PYQ | Year/session: 2024 / main | Paper code: 31/4/1 | Source question: 14 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 7

<https://www.cbse.gov.in/cbsenew/question-paper/2024/X/SCIENCE.zip>

Also used in: official-02, official-06, official-07, official-09, official-15

3. sqp_2022-23_q15

CBSE Class X Science (086) Sample Question Paper 2022-23 | SQP | Year/session: 2022-23 / 2022-23 | Paper code: Not recorded | Source question: 15 | Original section: Section A | Selected marks: 1 | PDF pages (one-based): 5

https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-SQP.pdf

Also used in: official-02, official-04, official-08, official-10, official-14

4. SQP_2026-27_q31

CBSE Class X Science (086) Sample Question Paper 2026-27 (English) | SQP | Year/session: 2026-27 / 2026-27 | Paper code: Not recorded | Source question: 31 | Original section: Section - C | Selected marks: 1 | PDF pages (one-based): 11

https://cbseacademic.nic.in/web_material/SQP/ClassX_2026_27/Science-SQP.pdf

Also used in: official-01, official-05, official-08, official-11, official-15

5. pyq-2025-50a1900d91ebeada79f31c34

CBSE — Class X Science — 2025 — main — 31/3/1 | PYQ | Year/session: 2025 / main | Paper code: 31/3/1 | Source question: 26 | Original section: SECTION B | Selected marks: 2 | PDF pages (one-based): 13

https://www.cbse.gov.in/cbsenew/question-paper/2025/X/086_Science.zip

Also used in: official-02, official-11

6. pyq-2018-7253f82c5332b612f2b92314

CBSE — Class X Science — 2018 — 31/B — main | PYQ | Year/session: 2018 / main | Paper code: 31/B | Source question: 27 | Original section: SECTION-B | Selected marks: 2 | PDF pages (one-based): 15

https://www.cbse.gov.in/curric~1/qpms2018/qp_10/Science.zip

Also used in: official-04, official-07

7. SQP_2025-26_q34_A

CBSE Class X Science (086) Sample Question Paper 2025-26 (English) | SQP | Year/session: 2025-26 / 2025-26 | Paper code: Not recorded | Source question: 34 A | Original section: Section - C | Selected marks: 2 | PDF pages (one-based): 11

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-SQP.pdf

Also used in: official-05, official-08

8. SQP_2024-25_q25_VI_A

CBSE Class X Science (086) Sample Question Paper 2024-25 (English) | SQP | Year/session: 2024-25 / 2024-25 | Paper code: Not recorded | Source question: 25 VI A | Original section: Section-B | Selected marks: 2 | PDF pages (one-based): 7

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-SQP.pdf

Also used in: official-05, official-06

9. pyq-2026-55a6ea37078fb0fe5e79e7be

CBSE Class X Science 2026 First Board 31-2-1 | PYQ | Year/session: 2026 / 2026 First Board | Paper code: 31/2/1 | Source question: 37 | Original section: Section C (Physics) | Selected marks: 3 | PDF pages (one-based): 29

<https://www.cbse.gov.in/cbsenew/question-paper/2026/X/Science.zip>

No cross-paper reuse.

10. sqp_2021-22_term2_q12_main

CBSE Class X Science (086) Sample Question Paper 2021-22 — Term 2 | SQP | Year/session: 2021-22 / 2021-22 | Paper code: Not recorded | Source question: 12 | Original section: Section B | Selected marks: 3 | PDF pages (one-based): 4

https://cbseacademic.nic.in/web_material/SQP/ClassX_2021_22/Science-SQP_Term2.pdf

Also used in: official-02

11. pyq-2022-cfec2ef8067dd02793a5ebf2

CBSE — Class X Science — 2022 — main — 31/1/2 | PYQ | Year/session: 2022 / main | Paper code: 31/1/2 | Source question: 10 | Original section: SECTION B | Selected marks: 3 | PDF pages (one-based): 7

<https://www.cbse.gov.in/cbsenew/question-paper/2022/X/Scince.zip>

Also used in: official-04, official-06

12. sqp_2020-21_q36_main

CBSE Class X Science (086) Sample Question Paper 2020-21 | SQP | Year/session: 2020-21 / 2020-21 | Paper code: Not recorded | Source question: 36 | Original section: Section D | Selected marks: 5 | PDF pages (one-based): 14

https://cbseacademic.nic.in/web_material/SQP/ClassX_2020_21/Science-SQP.pdf

Also used in: official-03, official-05, official-08

13. SQP_2023-24_q39_OR_iv

CBSE Class X Science (086) Sample Question Paper 2023-24 (English) | SQP | Year/session: 2023-24 / 2023-24 | Paper code: Not recorded | Source question: 39 OR iv | Original section: Section-E | Selected marks: 4 | PDF pages (one-based): 8

https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-SQP.pdf

Also used in: official-01, official-08, official-11, official-15

14. SQP_2024-25_q36_A

CBSE Class X Science (086) Sample Question Paper 2024-25 (English) | SQP | Year/session: 2024-25 / 2024-25 | Paper code: Not recorded | Source question: 36 A | Original section: Section-D | Selected marks: 5 | PDF pages (one-based): 12, 13

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-SQP.pdf

No cross-paper reuse.