

Official-source Electricity compilation 13

Mixed-source chapter worksheet • cross-paper reuse disclosed

Total: 36 marks • Suggested time: 72 minutes

Instructions and reuse disclosure

Curated compilation of official CBSE source questions, not a CBSE-issued chapter paper. Original source labels and exact source images are retained.

Answer every selected question. Only one selected source-slot alternative appears in this paper; do not answer or count excluded alternatives.

Questions recur across this 15-paper collection. Reuse is disclosed per question in the source appendix; these are not 15 disjoint official papers.

Sections use available source marks: A MCQ; B 2 marks; C 3 marks; D 5 marks or source-marked case questions. Case marks are not inflated to five.

Section A — MCQ

Compilation questions 1-4; 4 marks. Exact source labels remain attached to each question.

Section B — 2-mark questions

Compilation questions 5-8; 8 marks. Exact source labels remain attached to each question.

Section C — 3-mark questions

Compilation questions 9-11; 9 marks. Exact source labels remain attached to each question.

Section D — 5-mark / case-based questions

Compilation questions 12-14; 15 marks. Exact source labels remain attached to each question.

Section A — MCQ

1. [1 marks] Source Q30 • 2026 First Board

- 30.** The correct way to connect an ammeter and a voltmeter in an electric circuit is : 1
- (A) Ammeter in parallel and voltmeter in series
 - (B) Ammeter and voltmeter both in parallel
 - (C) Ammeter in series and voltmeter in parallel
 - (D) Ammeter and voltmeter both in series

Source/editorial note: Visually confirmed complete replacement crop: question number, wording, all options/table values, mathematical symbols and printed marks. Whitespace normalized; mathematical glyphs represented in Unicode and stacked fractions as $\frac{1}{4}$ and $\frac{V}{4}$. Page/QR/footer debris removed from text; marks retained in marks field. No supplied diagram; table retained in text and evidence. Answers not reviewed. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

2. [1 marks] Source Q13 • main

- 13.** A wire of length ' l ' is gradually stretched so that its length increases to $3l$.
If its original resistance is R , then its new resistance will be :

- (A) $3R$ (B) $6R$
(C) $9R$ (D) $27R$

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

3. [1 marks] Source Q14 • 2019-20

- 14 **Assertion:** A fuse wire is always connected in parallel with the mainline. 1

Reason: If a current larger than the specified value flows through the circuit, fuse wire melts.

For question numbers 13 and 14, two statements are given- one labeled *Assertion* (A) and the other labeled *Reason* (R). Select the correct answer to these questions from the codes (i), (ii), (iii) and (iv) as given below

- i) Both A and R are true and R is correct explanation of the assertion.
- ii) Both A and R are true but R is not the correct explanation of the assertion.
- iii) A is true but R is false.
- iv) A is false but R is true.

- 13 **Assertion:** Following are the structural isomers of butane. 1

Source/editorial note: Fuse series placement and melting from excess current are explicitly NCERT Electricity section 11.7.1 (printed p190, PDF p20). Included after independent audit overturned the batch reviewer's domestic-circuit exclusion. Shared assertion-reason choices occur on preceding PDF page 5.

4. [1 marks] Source Q13 • 2022-23

13	A complete circuit is left on for several minutes, causing the connecting copper wire to become hot. As the temperature of the wire increases, the electrical resistance of the wire	1
	(a) decreases.	
	(b) remains the same.	
	(c) increases.	
	(d) increases for some time and then decreases .	

Section B — 2-mark questions

5. [2 marks] Source Q27 • main

The values of current (I) flowing through a given resistor of resistance (R), for the corresponding values of potential difference (V) across the resistor are as given below :

V (volts)	0.5	1.0	1.5	2.0	2.5	3.0	4.0	5.0
I (amperes)	0.1	0.2	0.3	0.4	0.5	0.6	0.8	1.0

Plot a graph between current (I) and potential difference (V) and determine the resistance (R) of the resistor.

Source/editorial note: Occurrence mappings retained verbatim; only primary PDF/question evidence is accepted and counted. Other occurrences require their own evidence validation. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

6. [2 marks] Source Q34 VI B • 2025-26


OR

B. A copper wire has a length $L=2$ m, a cross-sectional area $A=0.5$ mm², and resistivity $\rho=1.7\times10^{-8}$ Ω -m. Calculate the resistance of another wire made of the same material whose length is twice the length of the wire but has the same cross-sectional area.

Source/editorial note: Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

7. [2 marks] Source Q25 B • 2024-25

B.

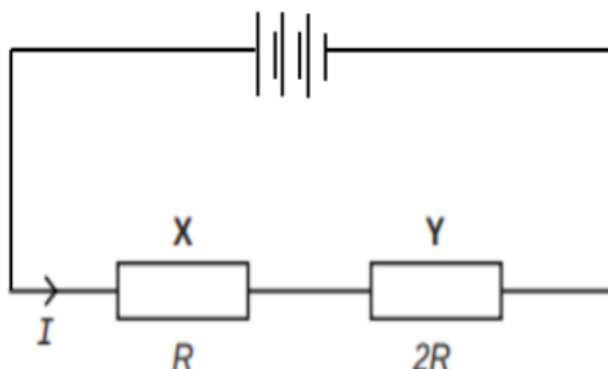

The above figure shows two resistors X and Y connected in series to a battery. The power dissipated for this combination is P_1 . When these resistors are connected in parallel to the same battery then the power dissipated is given by P_2 . Find out the ratio $\frac{P_1}{P_2}$.

Source/editorial note: Diagram supplies $X = R$ and $Y = 2R$; continuation on next page retained. Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

8. [2 marks] Source Q26 OR • 2017-18

OR

In a given ammeter, a student sees that needle indicates 17 divisions in ammeter while performing an experiment to verify Ohm's law. If ammeter has 10 divisions between 0 and 0.5A, then what is the value corresponding to 17 divisions?

Source/editorial note: Separate internal OR alternative to Q26; practical-skills question. The printed number 26 and 2-mark allocation occur on the previous page for the shared question slot.

Section C — 3-mark questions


9. [3 marks] Source Q12 • compartment

- 12.** Define the term electric power. An electric device of resistance R when connected across an electric source of voltage V draws a current I . Derive an expression for the power in terms of resistance R and voltage V . What is the power of a device of resistance $400\ \Omega$ operating at $200\ \text{V}$?

3

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

10. [3 marks] Source Q37 main • 2026-27

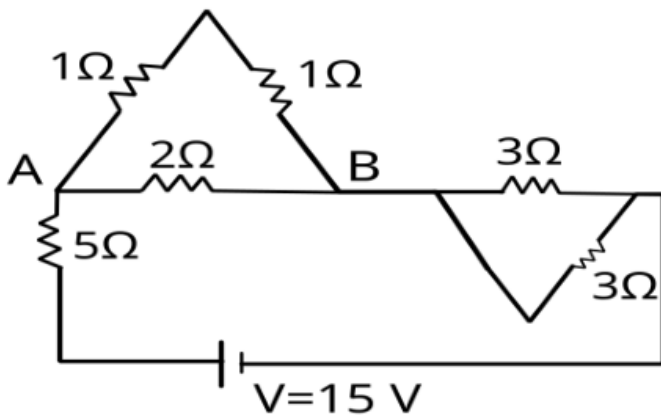37	 The figure shows a circuit with a 15 V battery connected to several resistors. Using the given circuit diagram: A. Find the total current supplied by the battery. B. Calculate the potential difference between points A and B.	3
----	--	---

Source/editorial note: Original and reduced circuit diagrams are preserved in answer evidence. Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

11. [3 marks] Source Q32 • 2023-24

32	(i) State the law that explains the heating effect of current with respect to the measurable properties in an electrical circuit. (ii) List the factors on which the resistance of a conductor depends.	2+1
----	---	-----

Source/editorial note: Official MS prints $H = I^2 R t$ (digit 1, visually verified), evidently a typo for $H = I^2 R t$. Printed typo preserved in answer. Marks 2+1. Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence. Official answer unavailable/withheld for an identified error, omission or incomplete verification: Official answer retains erroneous digit 1 in $H = I^2 R t$; correct formula explained in notes. Consult the linked original marking scheme with this limitation in mind.

Section D — 5-mark / case-based questions

12. [5 marks] Source Q34 • main

SECTION D

- 34.** There are three resistors of $10\ \Omega$, $20\ \Omega$ and $30\ \Omega$ joined in parallel in a circuit. The potential difference across the electric circuit is 10 V.
- Draw a circuit diagram for the above case.
 - Find the total resistance of the combination of resistors.
 - Calculate the electric current drawn from the same source.

5

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

13. [5 marks] Source Q36 • compartment

36. (a) (i) Write the relation between the electrical resistivity ' ρ ' and the resistance ' R ' of a cylindrical conductor of length ' l ' and area of cross-section ' A '. Use this relationship to determine the SI unit of ' ρ '.

(ii) Find the electrical resistivity of the material of a wire of length 120 cm and diameter 0.4 mm. The resistance of this wire is 3 Ω .

5

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

14. [5 marks] Source Q29 • 2019-20

29 (i) Consider a conductor of resistance ' R ', length ' L ', thickness ' d ' and resistivity ' ρ '. 5
Now this conductor is cut into four equal parts. What will be the new resistivity of each of these parts? Why?

(ii) Find the resistance if all of these parts are connected in:

(a) Parallel

(b) Series

(iii) Out of the combinations of resistors mentioned above in the previous part, for a given voltage which combination will consume more power and why?

Source/editorial note: All dependent subparts retained in one 5-mark record, including both (ii)(a) and (ii)(b). Marking-scheme answer spans PDF pages 6-7.

Solutions and verification status

Only explicitly verified solutions are printed. A missing solution is not a claim that the question is unsolvable.

Question 1 — pyq-2026-0c419e09ddf75b6dd3da937f

Official answer unavailable/withheld: No independently verified official answer supplied.

Original marking scheme (see limitation above): https://www.cbse.gov.in/cbsenew/marketing-scheme/2026/X/086_SCIENCE.zip

Question 2 — pyq-2025-89ec80e87c4adf229cc3e824

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 3 — SQP-2019-20-Q14

iv) Assertion is false but reason is true.

14	iv) Assertion is false but reason is true.	1 mark
----	--	--------

Marking-scheme PDF page(s): [2]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_MS.pdf

Question 4 — sqp_2022-23_q13

(c) increases

13.	(c) increases	1
-----	---------------	---

Marking-scheme PDF page(s): [1]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-MS.pdf

Question 5 — pyq-2018-ac2b7b28762938a4a2df67a3

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 6 — SQP_2025-26_q34_VI_B

Given:

Length of the wire, $l = 2 \text{ m}$

Cross-sectional area, $A = 0.5 \text{ mm}^2 = 0.5 \times 10^{-6} \text{ m}^2$

Resistivity of copper, $\rho = 1.7 \times 10^{-8} \Omega\text{-m}$

The resistance R of a wire is given by the formula:

$$R = \rho l / A$$

Step 1: Calculate the initial resistance R_1 and $l = 2 \text{ m}$

$$R_1 = (1.7 \times 10^{-8} \times 2) / (0.5 \times 10^{-6}) = 0.068 \Omega$$

Step 2: Calculate the new resistance R_2 and $l = 4 \text{ m}$ (double length)

$$R_2 = (1.7 \times 10^{-8} \times 4) / (0.5 \times 10^{-6}) = 0.136 \Omega$$

The resistance of the wire when the length is double is 0.136Ω

OR

B.

$$R = \frac{\rho \cdot l}{A}$$

Given:

- Initial length, $l = 2 \text{ m}$
- Cross-sectional area, $A = 0.5 \text{ mm}^2 = 0.5 \times 10^{-6} \text{ m}^2$
- Resistivity of copper, $\rho = 1.7 \times 10^{-8} \Omega \cdot \text{m}$

Step 1: Calculate the initial resistance R_1 and $l = 2 \text{ m}$

$$R_1 = \frac{\rho \cdot l}{A} = \frac{1.7 \times 10^{-8} \Omega \cdot \text{m} \times 2 \text{ m}}{0.5 \times 10^{-6} \text{ m}^2}$$
$$R_1 = \frac{3.4 \times 10^{-8}}{0.5 \times 10^{-6}} \Omega = 0.068 \Omega$$

Step 2: Calculate the new resistance R_2 and $l = 4 \text{ m}$ (double length)

$$R_2 = \frac{\rho \cdot (2l)}{A} = 2 \times R_1 = 2 \times 0.068 \Omega = 0.136 \Omega$$

The resistance of the wire when the length is double is 0.136Ω

Marking-scheme PDF page(s): [8]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-MS.pdf

Question 7 — SQP_2024-25_q25_B

B. For series total resistance is $R+2R = 3R$ (0.5)

$$P_1 = V^2/(3R). \text{ (0.5)}$$

For parallel total Resistance is $2R/3$. (0.5)

$$P_2 = V^2/(2R/3) = 3V^2/(2R).$$

$$P_1/P_2 = 2/9. \text{ (0.5)}$$

B. For series total resistance is $R+2R = 3R$

(0.5)

$$P_1 = \frac{V^2}{3R}.$$

(0.5)

For parallel total Resistance is $\frac{2R}{3}$.

(0.5)

$$P_2 = \frac{V^2}{2R/3} = \frac{3V^2}{2R}.$$

$$\frac{P_1}{P_2} = \frac{2}{9}.$$

(0.5)

Marking-scheme PDF page(s): [3]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-MS.pdf

Question 8 — cbse_sqp_2017-18_electricity_q26_OR

1 Division = $0.5 \text{ A} / 10$. 17 divisions = $17/20 = 0.85 \text{ A}$.

OR

An ammeter has 10 divisions between 0 to 0.5A. So,

$$1 \text{ Division} = 0.5\text{A} / 10$$

$$17 \text{ divisions} = 17/20 = 0.85\text{A}$$

Marking-scheme PDF page(s): [7]

https://cbseacademic.nic.in/web_material/SQP/CLASS_X_2017_18/Science_MS.pdf

Question 9 — pyq-2022-4f106d54aeecf637b6b663fc

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 10 — SQP_2026-27_q37_main

A.

1 Ω and 1 Ω are in series and the combination is in parallel with 2 Ω

$$1/R = 1/2 + 1/2 \quad R_{AB} = 1 \Omega$$

$$1/R = 1/3 + 1/3 \quad R = 1.5 \Omega$$

5 Ω , 1 Ω and 1.5 Ω are in series: $R_s = 5 + 1 + 1.5$

$$R_s = 7.5 \Omega$$

$$V = IR$$


$$15 \text{ V} = I \times 7.5$$

$$I = 2 \text{ A (2)}$$


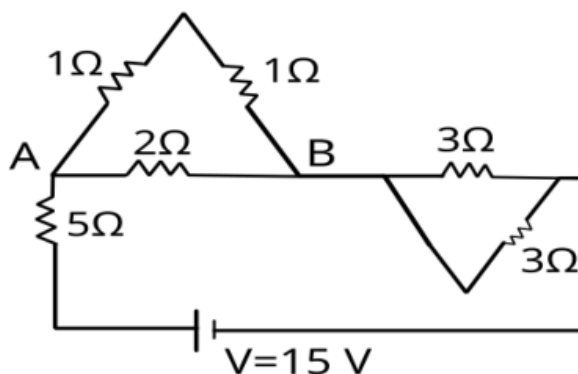
B. $R_{AB} = 1 \Omega$, net current between points A and B is 2A

$$V_{AB} = I_{AB} \times R_{AB}$$


$$V_{AB} = 2 \times 1 = 2 \text{ V (1)}$$



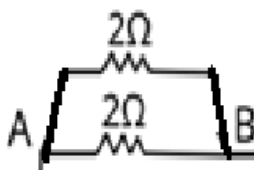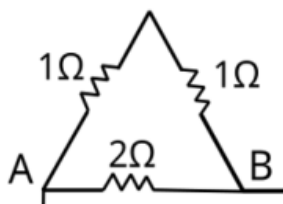1 Ω and 1 Ω are in series and the combination is in parallel with 2 Ω


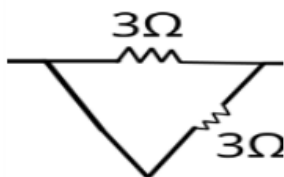
$$\frac{1}{R} = \frac{1}{2} + \frac{1}{2} \quad R_{AB} = 1 \Omega$$



$$\frac{1}{R} = \frac{1}{3} + \frac{1}{3} \quad R = 1.5 \Omega$$

5 Ω , 1 Ω and 1.5 Ω are in series: $R_s = 5 + 1 + 1.5$
 $R_s = 7.5 \Omega$

$$V = I R$$

$$15 \text{ V} = I \times 7.5$$

$$I = 2 \text{ A}$$

(2)

B. $R_{AB} = 1 \Omega$, net current between points A and B is 2A

$$V_{AB} = I_{AB} \times R_{AB}$$

$$V_{AB} = 2 \times 1 = 2 \text{ V}$$

(1)

Marking-scheme PDF page(s): [9]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2026_27/Science-MS.pdf

Question 11 — SQP_2023-24_q32

Official answer unavailable/withheld: Official answer retains erroneous digit 1 in $H=1^2Rt$; correct formula explained in notes.

Original marking scheme (see limitation above): https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-M S.pdf

Question 12 — pyq-2023-84af9d4edc02297aecab4a0f

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 13 — pyq-2024-17a293a3889e84f2b1aa8c67

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 14 — cbse_sqp_2019-20_electricity_q29

(i) Resistivity will not change as it depends on the nature of the material of the conductor. (ii) Each part has length $L/4$; ρ and A are constant. $R = \rho L/A$; resistance of each part = $R/4$. (a) In parallel, equivalent resistance = $R/16 \Omega$. (b) In series, equivalent resistance = $R \Omega$. (iii) $P = V^2/R$. At a given voltage, the parallel combination has smaller equivalent resistance and therefore consumes more power.

29	(i) Resistivity will not change as it depends on the nature of the material of the conductor. (ii) The length of each part becomes $L/4$. ρ, A constant. $R = \rho L/A$. Resistance of each part = $R_{\text{part}} = (\rho L/4)/A = R/4$.	1 mark 0.5 mark
	(a) In parallel the $\frac{1}{R_{\text{eq}}} = \frac{1}{R_{\text{part}}} + \frac{1}{R_{\text{part}}} + \frac{1}{R_{\text{part}}} + \frac{1}{R_{\text{part}}} = \frac{4}{R_{\text{part}}} = \frac{4}{R/4} \rightarrow R_{\text{eq}} = R/16 \Omega$ (b) In series the $R_{\text{eq}} = R/4 + R/4 + R/4 + R/4 = R \Omega$ (iii) $P = V^2/R$. If R_{eq} is less, power consumed will be more. In the given case, R_{eq} is lesser in the parallel and power consumed will be more.	0.5 mark 1 mark 1 mark 0.5 mark 0.5 mark

Marking-scheme PDF page(s): [6, 7]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_MS.pdf

Per-question source appendix

Original CBSE questions/images remain attributed to their source. Compilation selection and numbering are editorial. The full Science source PDFs may include unrelated chapters; only selected Electricity crops form this worksheet.

1. pyq-2026-0c419e09ddf75b6dd3da937f

CBSE Class X Science 2026 First Board 31-3-3 | PYQ | Year/session: 2026 / 2026 First Board | Paper code: 31/3/3 | Source question: 30 | Original section: Section C (Physics) | Selected marks: 1 | PDF pages (one-based): 23

<https://www.cbse.gov.in/cbsenew/question-paper/2026/X/Science.zip>

Also used in: official-05

2. pyq-2025-89ec80e87c4adf229cc3e824

CBSE — Class X Science — 2025 — main — 31/3/1 | PYQ | Year/session: 2025 / main | Paper code: 31/3/1 | Source question: 13 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 9

https://www.cbse.gov.in/cbsenew/question-paper/2025/X/086_Science.zip

Also used in: official-03, official-04

3. SQP-2019-20-Q14

Science-086 Sample Question Paper 2019-20 Class-X | SQP | Year/session: 2019-20 / 2019-20 | Paper code: Not recorded | Source question: 14 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 5, 6

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_SQP.pdf

Also used in: official-03, official-05, official-09, official-11

4. sqp_2022-23_q13

CBSE Class X Science (086) Sample Question Paper 2022-23 | SQP | Year/session: 2022-23 / 2022-23 | Paper code: Not recorded | Source question: 13 | Original section: Section A | Selected marks: 1 | PDF pages (one-based): 4

https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-SQP.pdf

Also used in: official-03, official-05, official-06, official-09, official-15

5. pyq-2018-ac2b7b28762938a4a2df67a3

CBSE — Class X Science — 2018 — 31/1 — main | PYQ | Year/session: 2018 / main | Paper code: 31/1 | Source question: 27 | Original section: Section – B | Selected marks: 2 | PDF pages (one-based): 12

https://www.cbse.gov.in/curric~1/qpms2018/qp_10/Science.zip

Also used in: official-03, official-09, official-15

6. SQP_2025-26_q34_VI_B

CBSE Class X Science (086) Sample Question Paper 2025-26 (English) | SQP | Year/session: 2025-26 / 2025-26 | Paper code: Not recorded | Source question: 34 VI B | Original section: Section – C | Selected marks: 2 | PDF pages (one-based): 12

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-SQP.pdf

Also used in: official-01, official-09

7. SQP_2024-25_q25_B

CBSE Class X Science (086) Sample Question Paper 2024-25 (English) | SQP | Year/session: 2024-25 / 2024-25 | Paper code: Not recorded | Source question: 25 B | Original section: Section-B | Selected marks: 2 | PDF pages (one-based): 6, 7

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-SQP.pdf

Also used in: official-01, official-10

8. cbse_sqp_2017-18_electricity_q26_OR

Sample Question Paper 2017-18 — Science — Class - X | SQP | Year/session: 2017-18 / 2017-18 | Paper code: Not recorded | Source question: 26 OR | Original section: SECTION - B | Selected marks: 2 | PDF pages (one-based): 4

https://cbseacademic.nic.in/web_material/SQP/CLASS_X_2017_18/Science_SQP.pdf

Also used in: official-01, official-09

9. pyq-2022-4f106d54aeecf637b6b663fc

CBSE — Class X Science — 2022 — compartment — 31/6/1 | PYQ | Year/session: 2022 / compartment | Paper code: 31/6/1 | Source question: 12 | Original section: SECTION B | Selected marks: 3 | PDF pages (one-based): 11

<https://www.cbse.gov.in/cbsenew/question-paper/2022-COMPTT/X/SCIENCE.zip>

Also used in: official-01, official-07

10. SQP_2026-27_q37_main

CBSE Class X Science (086) Sample Question Paper 2026-27 (English) | SQP | Year/session: 2026-27 / 2026-27 | Paper code: Not recorded | Source question: 37 main | Original section: Section - C | Selected marks: 3 | PDF pages (one-based): 13

https://cbseacademic.nic.in/web_material/SQP/ClassX_2026_27/Science-SQP.pdf

Also used in: official-09

11. SQP_2023-24_q32

CBSE Class X Science (086) Sample Question Paper 2023-24 (English) | SQP | Year/session: 2023-24 / 2023-24 | Paper code: Not recorded | Source question: 32 | Original section: Section-C | Selected marks: 3 | PDF pages (one-based): 5

https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-SQP.pdf

Also used in: official-04, official-09

12. pyq-2023-84af9d4edc02297aecab4a0f

CBSE — Class X Science — 2023 — main — 31/5/2 | PYQ | Year/session: 2023 / main | Paper code: 31/5/2 | Source question: 34 | Original section: SECTION D | Selected marks: 5 | PDF pages (one-based): 19

<https://www.cbse.gov.in/cbsenew/question-paper/2023/X/SCIENCE.zip>

Also used in: official-01, official-05, official-09, official-10

13. pyq-2024-17a293a3889e84f2b1aa8c67

CBSE — Class X Science — 2024 — compartment — 31/5/1 | PYQ | Year/session: 2024 / compartment | Paper code: 31/5/1 | Source question: 36 | Original section: SECTION D | Selected marks: 5 | PDF pages (one-based): 23

<https://www.cbse.gov.in/cbsenew/question-paper/2024-COMPTT/X/SCIENCE.zip>

Also used in: official-03, official-04, official-06, official-15

14. cbse_sqp_2019-20_electricity_q29

Class-X Science-086 SAMPLE QUESTION PAPER 2019-20 | SQP | Year/session: 2019-20 / 2019-20 | Paper code: Not recorded | Source question: 29 | Original section: SECTION C | Selected marks: 5 | PDF pages (one-based): 9

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_SQP.pdf

No cross-paper reuse.