

Official-source Electricity compilation 14

Mixed-source chapter worksheet • cross-paper reuse disclosed

Total: 34 marks • Suggested time: 68 minutes

Instructions and reuse disclosure

Curated compilation of official CBSE source questions, not a CBSE-issued chapter paper. Original source labels and exact source images are retained.

Answer every selected question. Only one selected source-slot alternative appears in this paper; do not answer or count excluded alternatives.

Questions recur across this 15-paper collection. Reuse is disclosed per question in the source appendix; these are not 15 disjoint official papers.

Sections use available source marks: A MCQ; B 2 marks; C 3 marks; D 5 marks or source-marked case questions. Case marks are not inflated to five.

Section A — MCQ

Compilation questions 1-4; 4 marks. Exact source labels remain attached to each question.

Section B — 2-mark questions

Compilation questions 5-8; 8 marks. Exact source labels remain attached to each question.

Section C — 3-mark questions

Compilation questions 9-11; 9 marks. Exact source labels remain attached to each question.

Section D — 5-mark / case-based questions

Compilation questions 12-14; 13 marks. Exact source labels remain attached to each question.

Section A — MCQ

1. [1 marks] Source Q31 • 2026 First Board

- 31.** In an electric circuit carrying current I , a $2\ \Omega$ resistor is replaced by an $8\ \Omega$ resistor without changing the connected (ideal) battery. Then : 1
- (A) current becomes $\frac{I}{4}$ and potential difference $\frac{V}{4}$
- (B) current becomes $\frac{I}{4}$ and potential difference remains V
- (C) current becomes $4I$ and potential difference remains V
- (D) current becomes $4I$ and potential difference $\frac{V}{4}$

31/3/2

Page 23 of 31

P.T.O.

Source/editorial note: Visually confirmed complete replacement crop: question number, wording, all options/table values, mathematical symbols and printed marks. Whitespace normalized; mathematical glyphs represented in Unicode and stacked fractions as $I/4$ and $V/4$. Page/QR/footer debris removed from text; marks retained in marks field. No supplied diagram; table retained in text and evidence. Answers not reviewed. Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.


2. [1 marks] Source Q7 • 2019-20

- 7 Unit of electric power may also be expressed as: 1
- i) volt-ampere
- ii) kilowatt-hour
- iii) watt-second
- iv) joule-second

3. [1 marks] Source Q15 • 2022-23


15

1

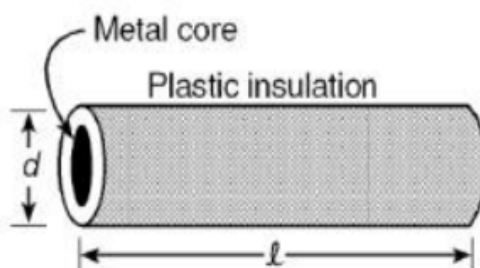

Plastic insulation surrounds a wire having diameter d and length l as shown above. A decrease in the resistance of the wire would be produced by an increase in the

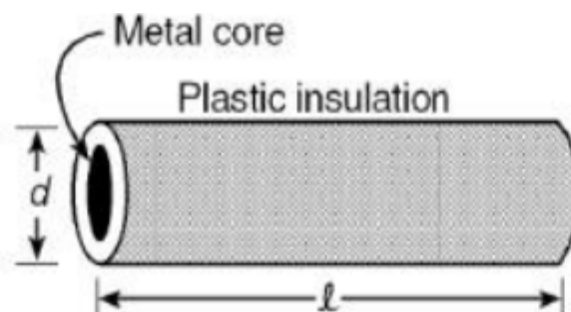- (a) length l of the wire
- (b) diameter d of the wire
- (c) temperature of the wire
- (d) thickness of the plastic insulation



4. [1 marks] Source Q15 • compartment

15. The resistance of a wire does **not** depend on its :

- (a) Length
- (b) Area of cross-section
- (c) Shape
- (d) Material


Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

Section B — 2-mark questions

5. [2 marks] Source Q25 • main

- 25.** $V - I$ graph for two conducting wires A and B are as shown. If both wires are of the same length and same diameter, which of the two is made of a material of high resistivity? Give reasons to justify your answer.

2

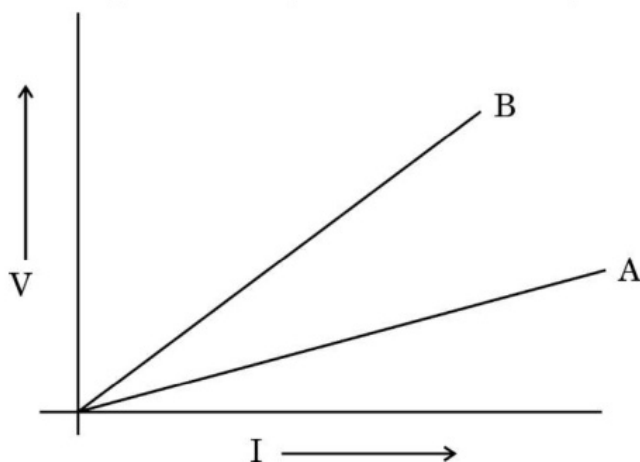

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

6. [2 marks] Source Q26 • main

- 26.** Two wires A and B of same material, having same lengths and diameters 0.2 mm and 0.3 mm respectively, are connected one by one in a circuit. Which one of these two wires will offer more resistance to the flow of current in the circuit? Justify your answer.

2

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

7. [2 marks] Source Q34 B • 2026-27

Or

B.

I. Define resistivity.

II. Justify with an example why resistivity is an intrinsic property of a material.


Source/editorial note: Original MS “thick-nesses” retained; comparison implicitly at fixed temperature. Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

8. [2 marks] Source Q25 A • 2024-25

25

Attempt either option A or B.

A.

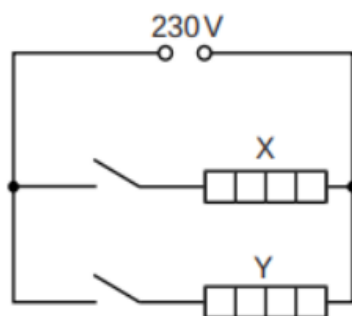

The electric circuit (above figure) in a clothes dryer contains two heaters X and Y in parallel. The above figure shows the circuit connected to a 230 V power supply. When both switches are closed, the current in X is 3.5 A.

Analyse the circuit given above and answer the following questions.

- Calculate the power developed in heater X.
- If the resistance of X is double that of Y calculate the current in heater Y.

2

Source/editorial note: Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

Section C — 3-mark questions

9. [3 marks] Source Q36 • 2025-26

36

A student needs to make a $0.12\ \Omega$ resistor. She has some copper wire of 0.80 mm diameter. Resistivity of copper is $1.8 \times 10^{-8}\ \Omega\text{m}$


- Determine the cross-sectional area of the wire.
- Calculate the length of wire required for the $0.12\ \Omega$ resistor.

3


Source/editorial note: Official scheme rounds area to $5 \times 10^{-7}\ \text{m}^2$ before calculating 3.33 m. Original “are” typo retained. No subpart marks printed. Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

10. [3 marks] Source Q12 • 2021-22

OR

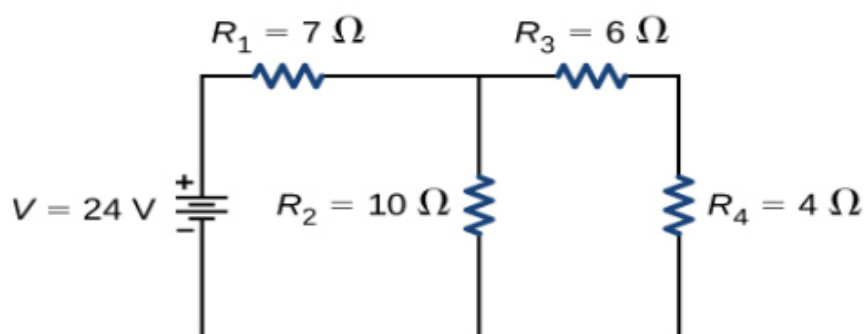

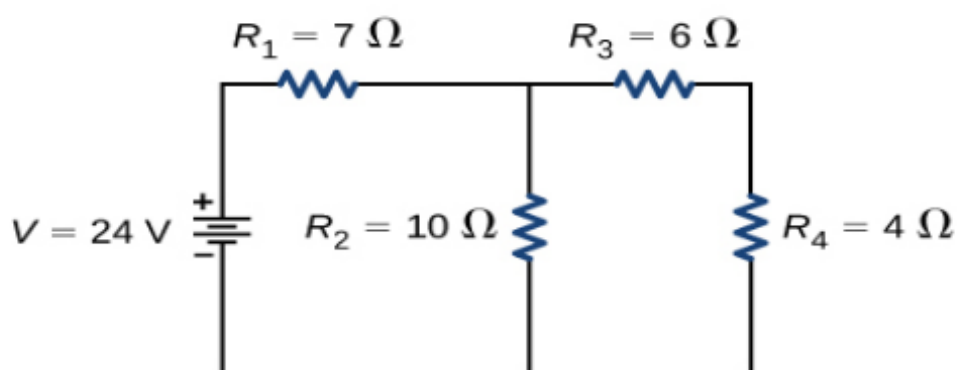
Calculate the total resistance of the circuit and find the total current in the circuit.



Source/editorial note: OR alternative with its own complete circuit and stem. Official solution is an embedded image on MS p.4 and was visually transcribed. Main and OR share three exam marks.

11. [3 marks] Source Q13 • 2018-19

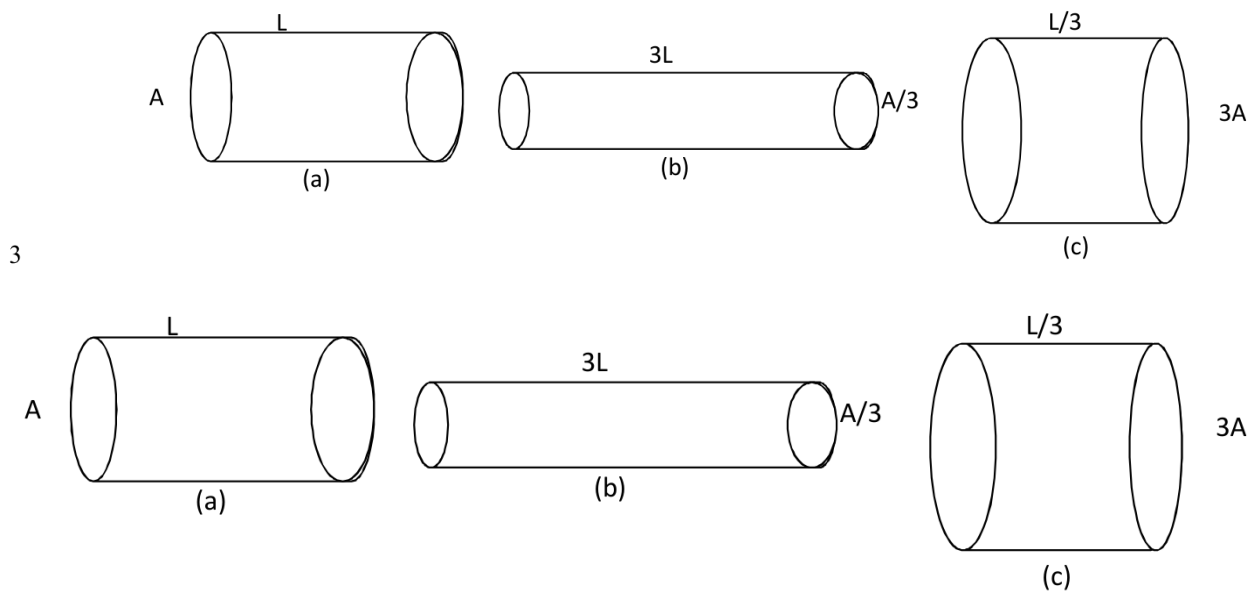13. The figure below shows three cylindrical copper conductors along with their face areas and lengths. Compare the resistance and the resistivity of the three conductors. Justify your answer.



Source/editorial note: Diagram labels verified visually: (a) L and A ; (b) $3L$ and $A/3$; (c) $L/3$ and $3A$. The full question crop preserves a stray printed "3" below the figures as present in the source.

Section D — 5-mark / case-based questions

12. [4 marks] Source Q39 • main


- 39.** As shown in the diagram, an electric circuit consisting of an ammeter, a voltmeter, 4 cells of 1.5 V each, a plug key with a gap XY was set up. Voltmeter and ammeter readings were recorded in the observation table for four arrangements as given below :

Arrangement No. 1 – only resistor R_1 in gap XY


Arrangement No. 2 – only resistor R_2 in gap XY

Arrangement No. 3 – Resistors R_1 and R_2 in series in gap XY

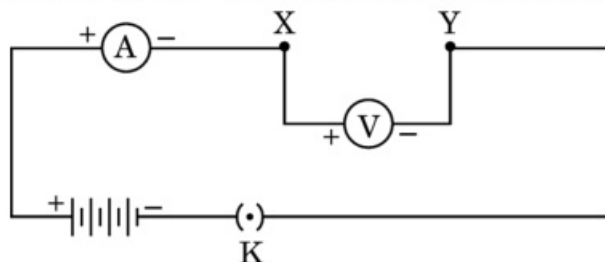Arrangement No. 4 – Resistors R_1 and R_2 in parallel in gap XY



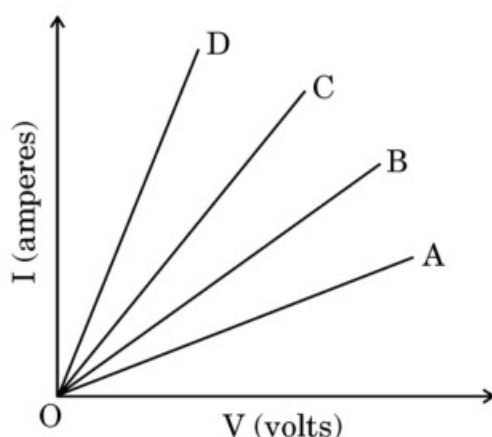
Based on the observations, four V – I graphs A, B, C and D as shown in figure were drawn. Study these graphs.



- (a) Which one of the graphs represents the series combination of R_1 and R_2 ? 1
- (b) Which one of these graphs represents the parallel combination of R_1 and R_2 ? 1
- (c) (i) Show an arrangement of three resistors, each of resistance $10\ \Omega$, so that the combination has a resistance of $15\ \Omega$. Give justification for your answer. 2

Source/editorial note: Official answer unavailable/withheld for an identified error, omission or incomplete verification: No independently verified official answer supplied. Consult the linked original marking scheme with this limitation in mind.

13. [4 marks] Source Q39 iii • 2023-24

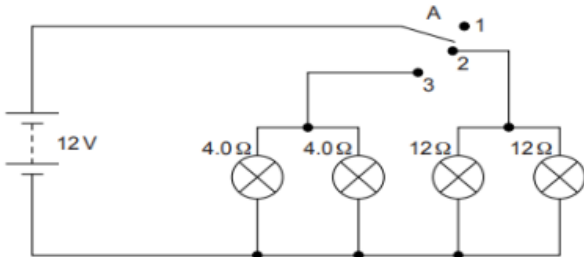39	 Vinita and Ahmed demonstrated a circuit that operates the two headlights and the two sidelights of a car, in their school exhibition. Based on their demonstrated circuit, answer the following questions. - State what happens when switch A is connected to - Position 2 - Position 3 - Find the potential difference across each lamp when lit. - Calculate the current - in each $12\ \Omega$ lamp when lit. - In each $4\ \Omega$ lamp when lit.	1+1+2
----	---	-------

Source/editorial note: Includes common (i), (ii) and main (iii); 1+1+2 marks. Original scheme mislabels second line of (i) as (a). Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence.

14. [5 marks] Source Q36 VI A • 2024-25

For visually impaired students

A.

- State the law and write the formula connecting the electric current flowing through a conductor and voltage applied across it.
- In a household five fans each of 100W are used for 4 hours and an electric press of 500W for 2 hours every day. Calculate the cost of using the fans and electric press for 60 days if the cost of 1 unit of electrical energy is Rs. 6.5.

Source/editorial note: Official MS omits the factor of five fans. Its Rs. 546.00 answer is retained. Correct calculation from SQP: $(5 \times 0.1 \times 4 + 0.5 \times 2) \times 60 = 180\text{ kWh}$; cost Rs.1170. MS marks 2+3=5. Source-verified against complete local text/coordinates and question crops; diagram-dependent and image-only formula evidence visually checked. Layout whitespace and mathematical glyphs normalized; wording/known source errors retained. Answer text is a source-faithful linear transcription; original layout is in answer evidence. Official answer unavailable/withheld for an identified error, omission or incomplete verification: Official energy cost omits four fans; correct Rs1170 documented separately. Consult the linked original marking scheme with this limitation in mind.

Solutions and verification status

Only explicitly verified solutions are printed. A missing solution is not a claim that the question is unsolvable.

Question 1 — pyq-2026-a53ce36a0fd993043d965609

Official answer unavailable/withheld: No independently verified official answer supplied.

Original marking scheme (see limitation above): https://www.cbse.gov.in/cbsenew/marketing-scheme/2026/X/086_SCIENCE.zip

Question 2 — cbse_sqp_2019-20_electricity_q7

i) volt-ampere. Power = Voltage $\times$ Current.

7	i) volt-ampere Power = Voltage $\times$ Current.	1 mark
---	---	--------

Marking-scheme PDF page(s): [1]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_MS.pdf

Question 3 — sqp_2022-23_q15

(b) diameter d of the wire

15.	(b) diameter d of the wire	1
-----	----------------------------	---

Marking-scheme PDF page(s): [1]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-MS.pdf

Question 4 — pyq-2023-dc74f0e84e53633b06097022

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 5 — pyq-2023-246eac3017f0793c27bba6a6

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 6 — pyq-2024-1e2d386b35acad1e9e07f369

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 7 — SQP_2026-27_q34_B

B.

I. Definition: The resistivity (ρ) of a material is defined as the resistance of a wire having unit cross-sectional area and unit length

$R = \rho L/A$, where R is resistance of a wire of length L and cross-sectional area A (1)

II. Intrinsic property justification: Resistivity depends only on material (not on dimensions).

Example: Two copper wires of different lengths and thick-nesses yield the same ρ when computed using $R \cdot A/L$. (1)

B.

I. Definition: The resistivity (ρ) of a material is defined as the resistance of a wire having unit cross-sectional area and unit length $R = \frac{\rho L}{A}$, where R is resistance of a wire of length L and cross-sectional area A (1)

II. Intrinsic property justification: Resistivity depends only on material (not on dimensions). Example: Two copper wires of different lengths and thick-nesses yield the same ρ when computed using $R \cdot A/L$. (1)

Marking-scheme PDF page(s): [7]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2026_27/Science-MS.pdf

Question 8 — SQP_2024-25_q25_A

A. $P = VI$ (1)

$$= 230 \times 3.5 = 805 \text{ W}$$

$I \propto 1/R$, so half the resistance means double the current.

Therefore, current in Y = 7.0 A. (1)

25

Student to attempt either A or B.

A. $P = VI$

$$= 230 \times 3.5 = 805 \text{ W}$$

$I \propto \frac{1}{R}$, so half the resistance means double the current.

Therefore, current in Y = 7.0 A.

(1)

(1)

2

Marking-scheme PDF page(s): [3]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-MS.pdf

Question 9 — SQP_2025-26_q36

(i) Show that the cross-sectional area of the wire is about $5 \times 10^{-7} \text{ m}^2$.

The cross-sectional area A of a wire with diameter d is given by:

$$A = \pi d^2/4$$

Substitute, $d = 0.80 \times 10^{-3} \text{ m}$:

$$A = \pi(0.80 \times 10^{-3})^2/4$$

$$A = \pi(0.64 \times 10^{-6})/4$$

$$A = (2.01 \times 10^{-6})/4 \approx 5 \times 10^{-7} \text{ m}^2$$

Thus, the cross-sectional area A is approximately $5 \times 10^{-7} \text{ m}^2$.

(ii) To find the length l of the wire, we can use the formula of resistance:

$$R = \rho l/A$$

Rearrange to solve for l :

$$l = RA/\rho$$

Substitute the values:

$$l = (0.12 \times 5 \times 10^{-7})/(1.8 \times 10^{-8})$$

$$l = (6 \times 10^{-8})/(1.8 \times 10^{-8})$$

$$l = 6/1.8 \approx 3.33 \text{ m}$$

The student needs a length of approximately 3.33 m of given copper wire to make a 0.12Ω resistor.

36	(i) Show that the cross-sectional area of the wire is about $5 \times 10^{-7} \text{ m}^2$. The cross-sectional area A of a wire with diameter d is given by: $A = \pi \left(\frac{d}{2} \right)^2$ Substitute, $d = 0.80 \times 10^{-3} \text{ m}$: $A = \pi \left(\frac{0.80 \times 10^{-3}}{2} \right)^2$ $A = \pi (0.40 \times 10^{-3})^2$ $A = \pi \times (0.16 \times 10^{-6}) \text{ m}^2$ $A \approx 3.14 \times 0.16 \times 10^{-6} \text{ m}^2$ $A \approx 5.024 \times 10^{-7} \text{ m}^2$ Thus, the cross-sectional area A is approximately $5 \times 10^{-7} \text{ m}^2$. (ii) To find the length l of the wire, we can use the formula of resistance: $R = \frac{\rho \cdot l}{A}$ Rearrange to solve for l : $l = \frac{R \cdot A}{\rho}$ Substitute the values: $l = \frac{0.12 \cdot 5 \times 10^{-7}}{1.8 \times 10^{-8}}$ $l = \frac{6 \times 10^{-8}}{1.8 \times 10^{-8}}$ $l = \frac{6}{1.8} \text{ m}$ $l = 3.33 \text{ m}$ The student needs a length of approximately 3.33 m of given copper wire to make a 0.12Ω resistor.	3
----	---	---

Marking-scheme PDF page(s): [9]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-MS.pdf

Question 10 — sqp_2021-22_term2_q12_OR

R3 and R4 are in series: $R_5 = 6 + 4 = 10 \Omega$. R5 and R2 are in parallel: $R_6 = (10 \times 10)/(10 + 10) = 5 \Omega$. R1 and R6 are in series: total resistance = $7 + 5 = 12 \Omega$. With $V = 24 \text{ V}$, $I = V/R = 24/12 = 2 \text{ A}$.

12

5 ohm, 10 ohm and R_1 are in series

$$1/R_p = 1/5 + 1/10 + 1/R_1$$

$$1/R_p = (2+1)/10 + 1/R_1$$

$$= 3/10 + 1/R_1$$

$$1/R_p = (3R_1 + 10)/10R_1$$

$$R_p = 10R_1 / (3R_1 + 10)$$

Now, 6 ohm, 6 ohm and R_p are in series

Thus,

$$R_{eq} = 12 + 10R_1 / (3R_1 + 10) \text{ ----- (1)} \quad (1 \text{ mark})$$

$$V = I R_{eq}$$

From the circuit

$$R_{eq} = 30/2 = 15 \text{ A ----- (2)} \quad (1 \text{ mark})$$


Equating (1) and (2)

$$12 + 10R_1 / (3R_1 + 10) = 15$$

$$10R_1 / (3R_1 + 10) = 3$$

$$10R_1 = (9R_1 + 30)$$

$$\text{Thus, } R_1 = 30 \text{ ohm.} \quad (1 \text{ mark})$$

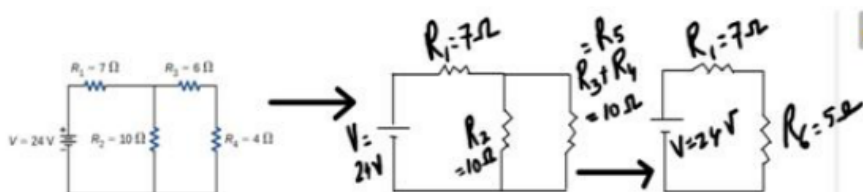OR


R_3 and R_4 are in series, hence the equivalent resistance of those two = $R_5 = R_3 + R_4 = 10 \text{ ohms}$. **0.5 marks**

R_5 and R_2 are in parallel. Let R_6 be the equivalent resistance for them. Hence $R_6 = (R_5 \cdot R_2) / (R_5 + R_2) = 100/20 = 5 \text{ ohms}$. **0.5 marks**

Now R_1 and R_6 are in series and hence the final equivalent resistance of the entire circuit is $R = R_1 + R_6 = 12 \text{ ohms}$. **1 mark**

By Ohm's Law we know that $V = IR$, hence $I = V/R$.

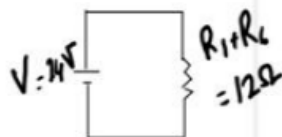Hence the current in the circuit is $24/12 \text{ A} = 2 \text{ A}$ (Final Answer) **1 mark**



(0.5+0.5+1+1)

3

Marking-scheme PDF page(s): [4]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2021_22/Science-MS_Term2.pdf

Question 11 — cbse_sqp_2018-19_electricity_q13

$R_a = \rho L/A$; $R_b = \rho(3L)/(A/3) = 9\rho L/A = 9R_a$; $R_c = \rho(L/3)/(3A) = (1/9)\rho L/A = (1/9)R_a$. Hence $R_b > R_a > R_c$. $\rho_a = \rho_b = \rho_c$ because all three conductors are of the same material.

$$13. R_a = \rho \frac{L}{A}$$

$$R_b = \rho \left(\frac{3L}{A/3} \right) = 9 \frac{\rho L}{A} = 9 R_a$$

$$R_c = \rho \frac{L/3}{3A} = \frac{1}{9} \frac{\rho L}{A} = \frac{1}{9} R_a$$

Hence $R_b > R_a > R_c$

$\rho_a = \rho_b = \rho_c$ because all the three conductors are of same material.

Marking-scheme PDF page(s): [4]

https://cbseacademic.nic.in/web_material/SQP/CLASS_X_2018_19/X_Science_MS_2018-19.pdf

Question 12 — pyq-2025-3c907fffc20ec05c468bbbea

Official answer unavailable/withheld: No independently verified official answer supplied.

Question 13 — SQP_2023-24_q39_iii

(i) 12 Ω lamps (only) on.

(a) 4 Ω lamps (only) on [0.5+0.5]

(ii) 12 V for both sets of lamps and all of them are in parallel. [1]

(iii) 12 Ω lamps are on when the wire is connected to position 2. Voltage across both 12 Ω lamps = 12 V. $V=IR$ (Ohm's law). $I = V/R = 12/12 = 1A$. [1]

4 Ω lamps are on when the wire is connected to position 3. Voltage across both 4 Ω lamps = 12 V. $V=IR$ (Ohm's law). $I = V/R = 12/4 = 3A$. [1]

39	(i) 12 Ω lamps (only) on. (a) 4 Ω lamps (only) on [0.5+0.5] (ii) 12 V for both sets of lamps and all of them are in parallel. [1] (iii) 12 Ω lamps are on when the wire is connected to position 2. Voltage across both 12 Ω lamps = 12 V. $V=IR$ (Ohm's law). $I = \frac{V}{R} = \frac{12}{12} = 1A$. [1] 4 Ω lamps are on when the wire is connected to position 3. Voltage across both 4 Ω lamps = 12 V. $V=IR$ (Ohm's law). $I = \frac{V}{R} = \frac{12}{4} = 3A$. [1]	4
----	---	---

Marking-scheme PDF page(s): [6]

https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-MS.pdf

Question 14 — SQP_2024-25_q36_VI_A

Official answer unavailable/withheld: Official energy cost omits four fans; correct Rs1170 documented separately.

Original marking scheme (see limitation above): https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-MS.pdf

Per-question source appendix

Original CBSE questions/images remain attributed to their source. Compilation selection and numbering are editorial. The full Science source PDFs may include unrelated chapters; only selected Electricity crops form this worksheet.

1. pyq-2026-a53ce36a0fd993043d965609

CBSE Class X Science 2026 First Board 31-3-2 | PYQ | Year/session: 2026 / 2026 First Board | Paper code: 31/3/2 | Source question: 31 | Original section: Section C (Physics) | Selected marks: 1 | PDF pages (one-based): 23

<https://www.cbse.gov.in/cbsenew/question-paper/2026/X/Science.zip>

Also used in: official-04, official-08

2. cbse_sqp_2019-20_electricity_q7

Class-X Science-086 SAMPLE QUESTION PAPER 2019-20 | SQP | Year/session: 2019-20 / 2019-20 | Paper code: Not recorded | Source question: 7 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 4

https://cbseacademic.nic.in/web_material/SQP/ClassX_2019_20/Science_SQP.pdf

Also used in: official-02, official-04, official-08, official-12

3. sqp_2022-23_q15

CBSE Class X Science (086) Sample Question Paper 2022-23 | SQP | Year/session: 2022-23 / 2022-23 | Paper code: Not recorded | Source question: 15 | Original section: Section A | Selected marks: 1 | PDF pages (one-based): 5

https://cbseacademic.nic.in/web_material/SQP/ClassX_2022_23/Science-SQP.pdf

Also used in: official-02, official-04, official-08, official-10, official-12

4. pyq-2023-dc74f0e84e53633b06097022

CBSE — Class X Science — 2023 — compartment | PYQ | Year/session: 2023 / compartment | Paper code: Not recorded | Source question: 15 | Original section: SECTION A | Selected marks: 1 | PDF pages (one-based): 11

<https://www.cbse.gov.in/cbsenew/question-paper/2023-COMPTT/X/Science.zip>

Also used in: official-02, official-03, official-06, official-09, official-11

5. pyq-2023-246eac3017f0793c27bba6a6

CBSE — Class X Science — 2023 — main — 31/2/1 | PYQ | Year/session: 2023 / main | Paper code: 31/2/1 | Source question: 25 | Original section: SECTION B | Selected marks: 2 | PDF pages (one-based): 15

<https://www.cbse.gov.in/cbsenew/question-paper/2023/X/SCIENCE.zip>

Also used in: official-04, official-07, official-08, official-11

6. pyq-2024-1e2d386b35acad1e9e07f369

CBSE — Class X Science — 2024 — main — 31/4/1 | PYQ | Year/session: 2024 / main | Paper code: 31/4/1 | Source question: 26 | Original section: SECTION B | Selected marks: 2 | PDF pages (one-based): 13

<https://www.cbse.gov.in/cbsenew/question-paper/2024/X/SCIENCE.zip>

Also used in: official-05, official-08, official-11

7. SQP_2026-27_q34_B

CBSE Class X Science (086) Sample Question Paper 2026-27 (English) | SQP | Year/session: 2026-27 / 2026-27 | Paper code: Not recorded | Source question: 34 B | Original section: Section - C | Selected marks: 2 | PDF pages (one-based): 12

https://cbseacademic.nic.in/web_material/SQP/ClassX_2026_27/Science-SQP.pdf

Also used in: official-02, official-06

8. SQP_2024-25_q25_A

CBSE Class X Science (086) Sample Question Paper 2024-25 (English) | SQP | Year/session: 2024-25 / 2024-25 | Paper code: Not recorded | Source question: 25 A | Original section: Section-B | Selected marks: 2 | PDF pages (one-based): 6

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-SQP.pdf

Also used in: official-04, official-09

9. SQP_2025-26_q36

CBSE Class X Science (086) Sample Question Paper 2025-26 (English) | SQP | Year/session: 2025-26 / 2025-26 | Paper code: Not recorded | Source question: 36 | Original section: Section – C | Selected marks: 3 | PDF pages (one-based): 13

https://cbseacademic.nic.in/web_material/SQP/ClassX_2025_26/Science-SQP.pdf

Also used in: official-10

10. sqp_2021-22_term2_q12_OR

CBSE Class X Science (086) Sample Question Paper 2021-22 — Term 2 | SQP | Year/session: 2021-22 / 2021-22 | Paper code: Not recorded | Source question: 12 | Original section: Section B | Selected marks: 3 | PDF pages (one-based): 4

https://cbseacademic.nic.in/web_material/SQP/ClassX_2021_22/Science-SQP_Term2.pdf

Also used in: official-04, official-07

11. cbse_sqp_2018-19_electricity_q13

Class-X Science-086 SAMPLE QUESTION PAPER-19 | SQP | Year/session: 2018-19 / 2018-19 | Paper code: Not recorded | Source question: 13 | Original section: SECTION C | Selected marks: 3 | PDF pages (one-based): 3

https://cbseacademic.nic.in/web_material/SQP/CLASS_X_2018_19/X_Science_SQP_2018-19.pdf

Also used in: official-03, official-08

12. pyq-2025-3c907fffc20ec05c468bbbea

CBSE — Class X Science — 2025 — main — 31/3/1 | PYQ | Year/session: 2025 / main | Paper code: 31/3/1 | Source question: 39 | Original section: SECTION E | Selected marks: 4 | PDF pages (one-based): 25, 27

https://www.cbse.gov.in/cbsenew/question-paper/2025/X/086_Science.zip

Also used in: official-06, official-09

13. SQP_2023-24_q39_iii

CBSE Class X Science (086) Sample Question Paper 2023-24 (English) | SQP | Year/session: 2023-24 / 2023-24 | Paper code: Not recorded | Source question: 39 iii | Original section: Section-E | Selected marks: 4 | PDF pages (one-based): 8

https://cbseacademic.nic.in/web_material/SQP/ClassX_2023_24/Science-SQP.pdf

Also used in: official-02, official-07, official-10

14. SQP_2024-25_q36_VI_A

CBSE Class X Science (086) Sample Question Paper 2024-25 (English) | SQP | Year/session: 2024-25 / 2024-25 | Paper code: Not recorded | Source question: 36 VI A | Original section: Section-D | Selected marks: 5 | PDF pages (one-based): 13

https://cbseacademic.nic.in/web_material/SQP/ClassX_2024_25/Science-SQP.pdf

No cross-paper reuse.